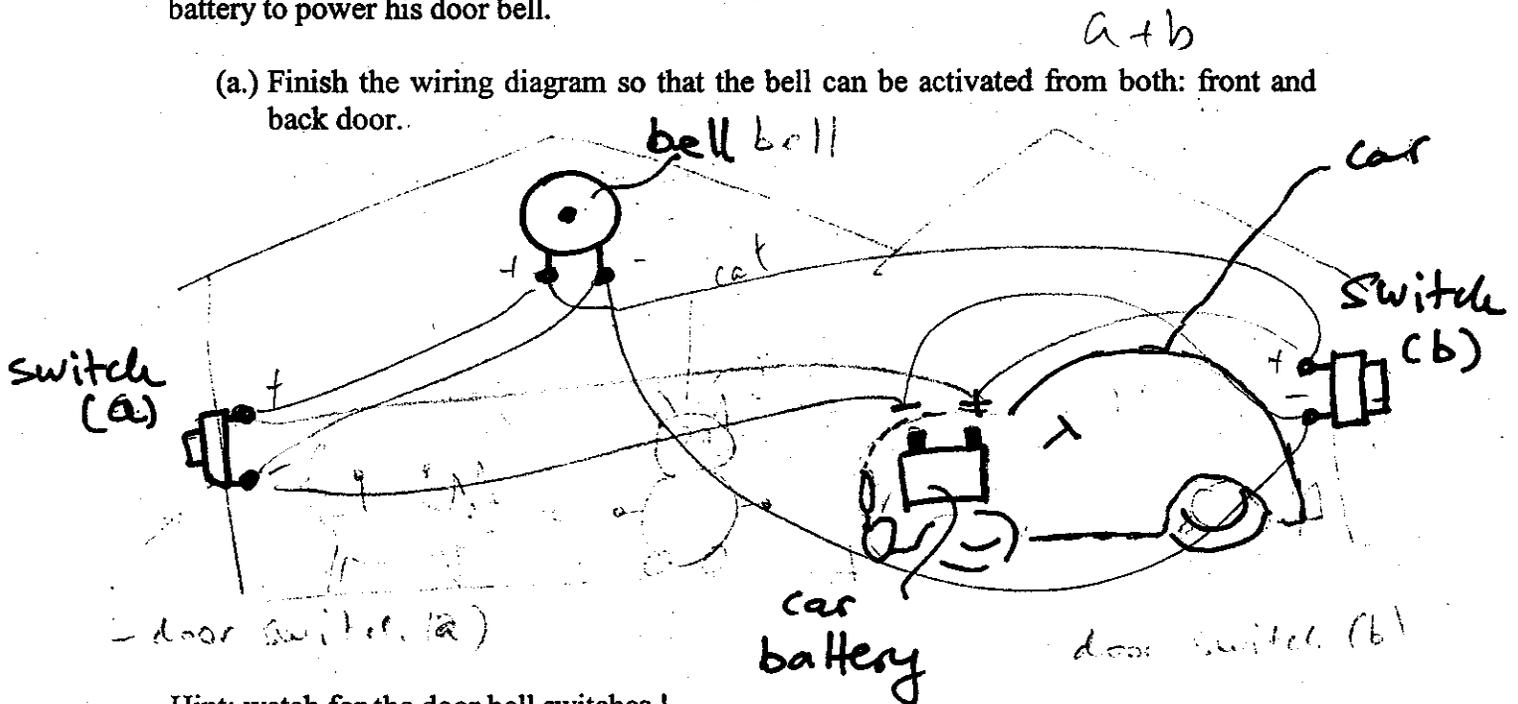


Your Name: _____

Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = ab' + ba'$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

Yes


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No

Your Name: 24-10

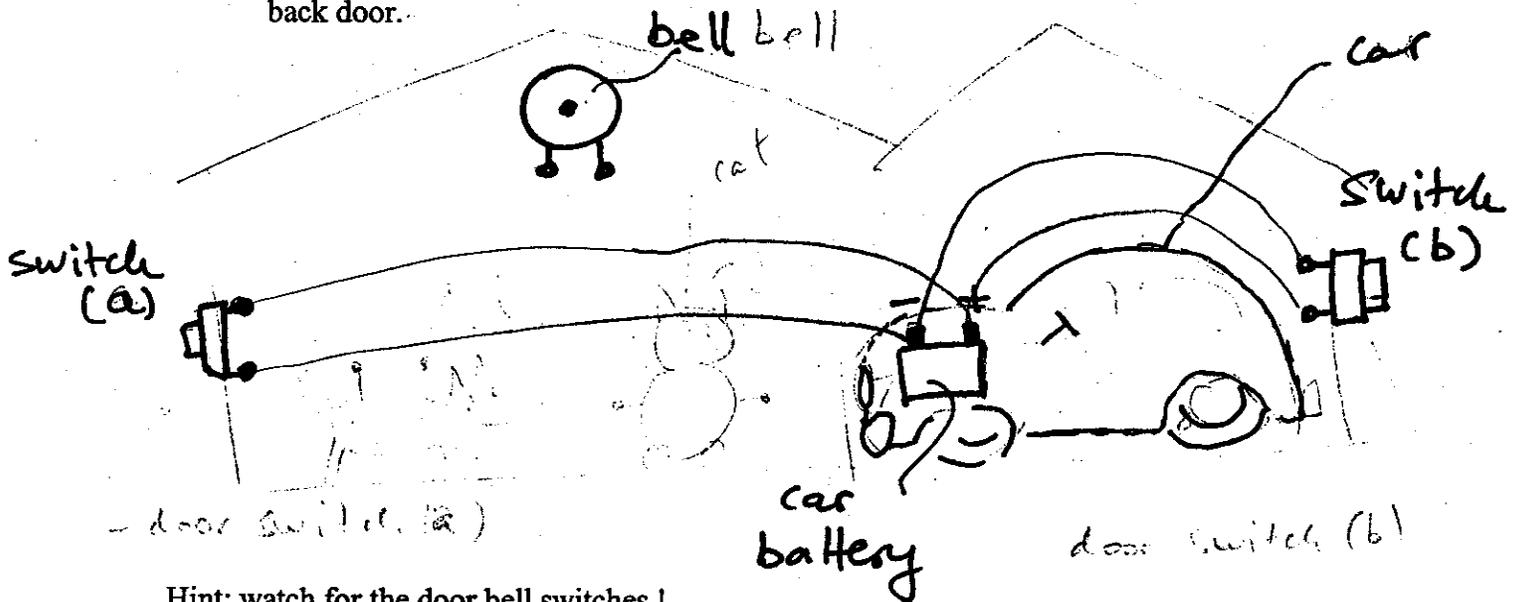Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

a	b	f
0	1	1
1	0	1
0	0	0
1	1	1

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$) $(\bar{a} + b) + (a + \bar{b}) + (a + b)$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

Yes


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No

Your Name: _____

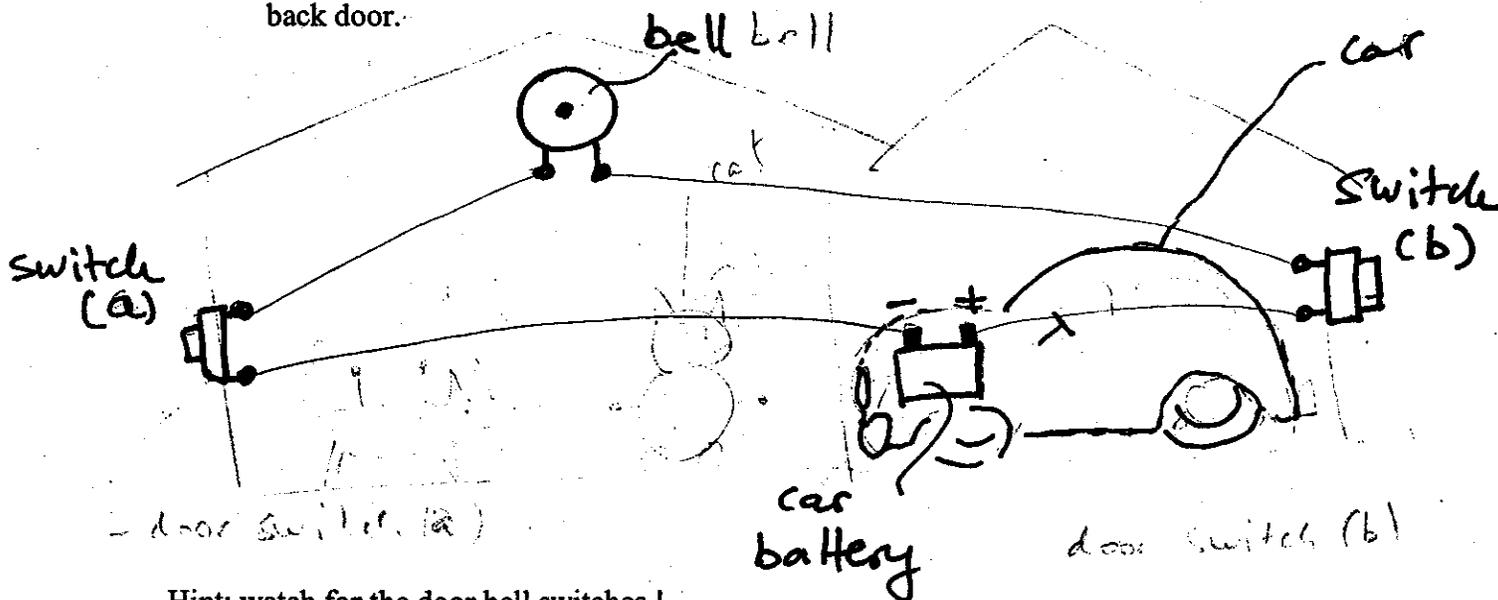Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = \bar{a}b + \bar{b}a$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

Yes


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No

Your Name: _____

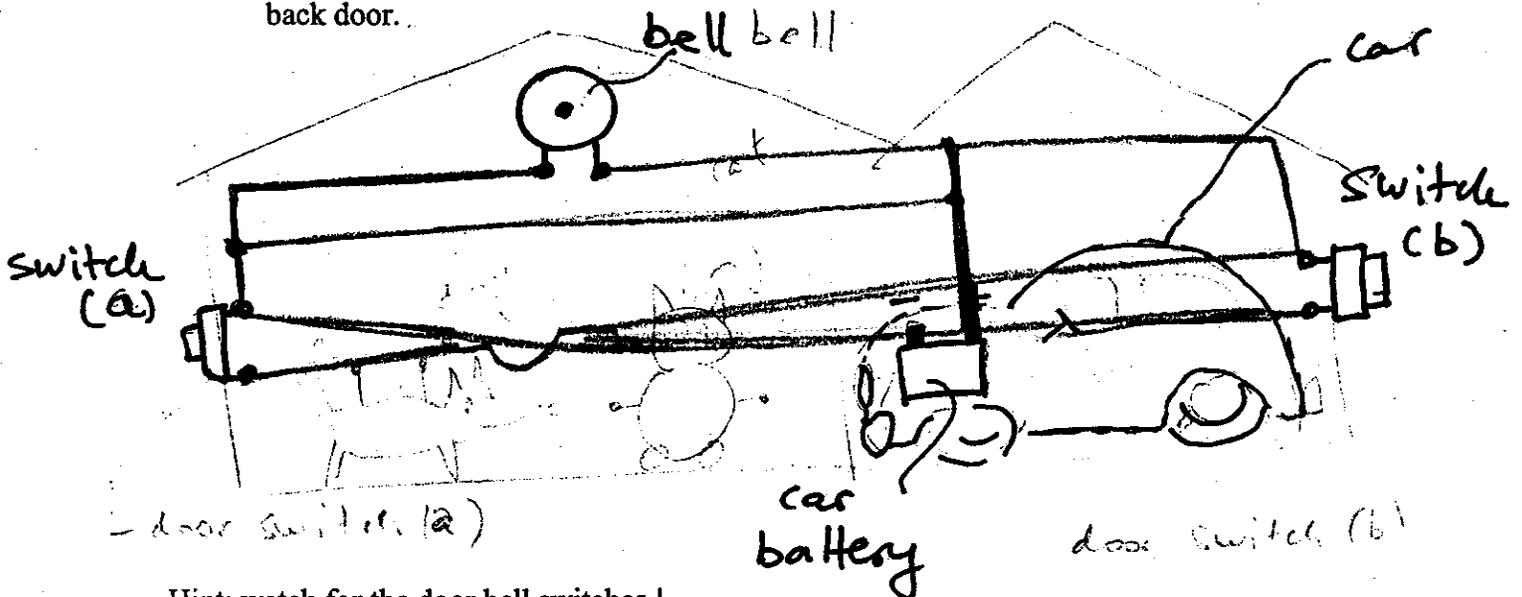Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

- (a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

- (b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

- (c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No, because there is no battery to activate the switches


- (d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No,

Your Name: _____

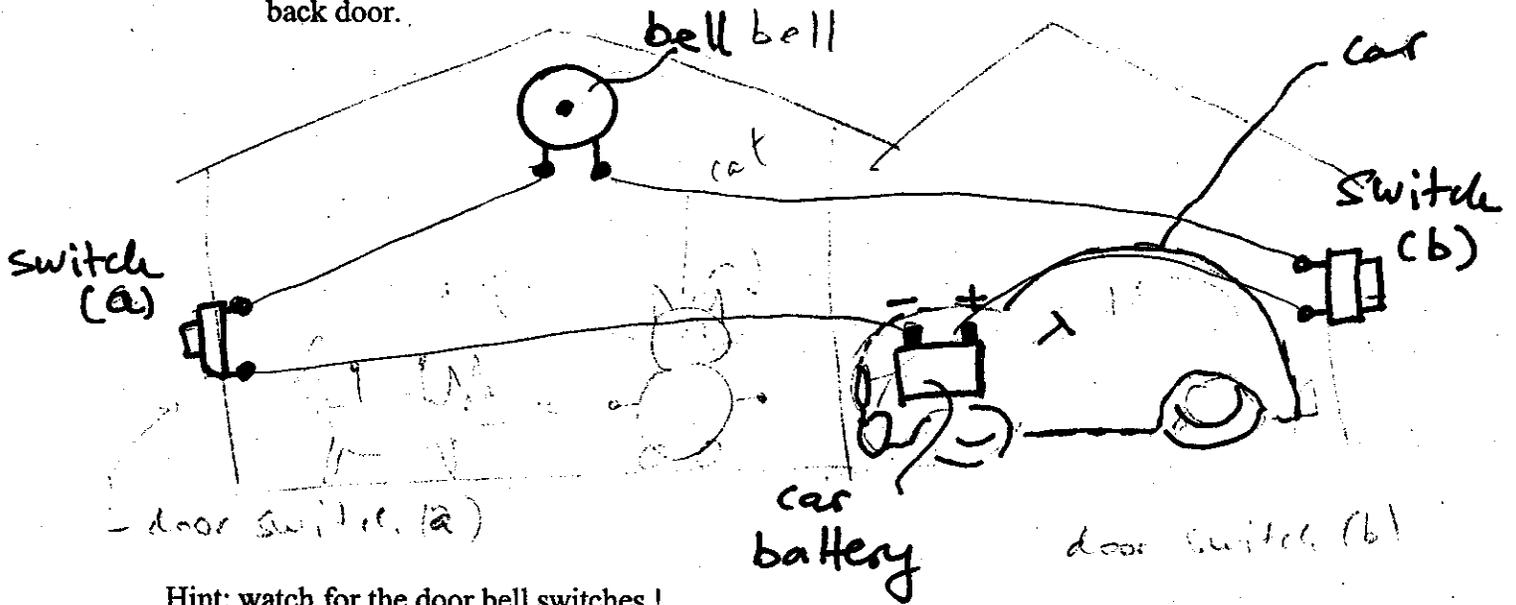Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

no

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?


?

yes

Your Name: _____

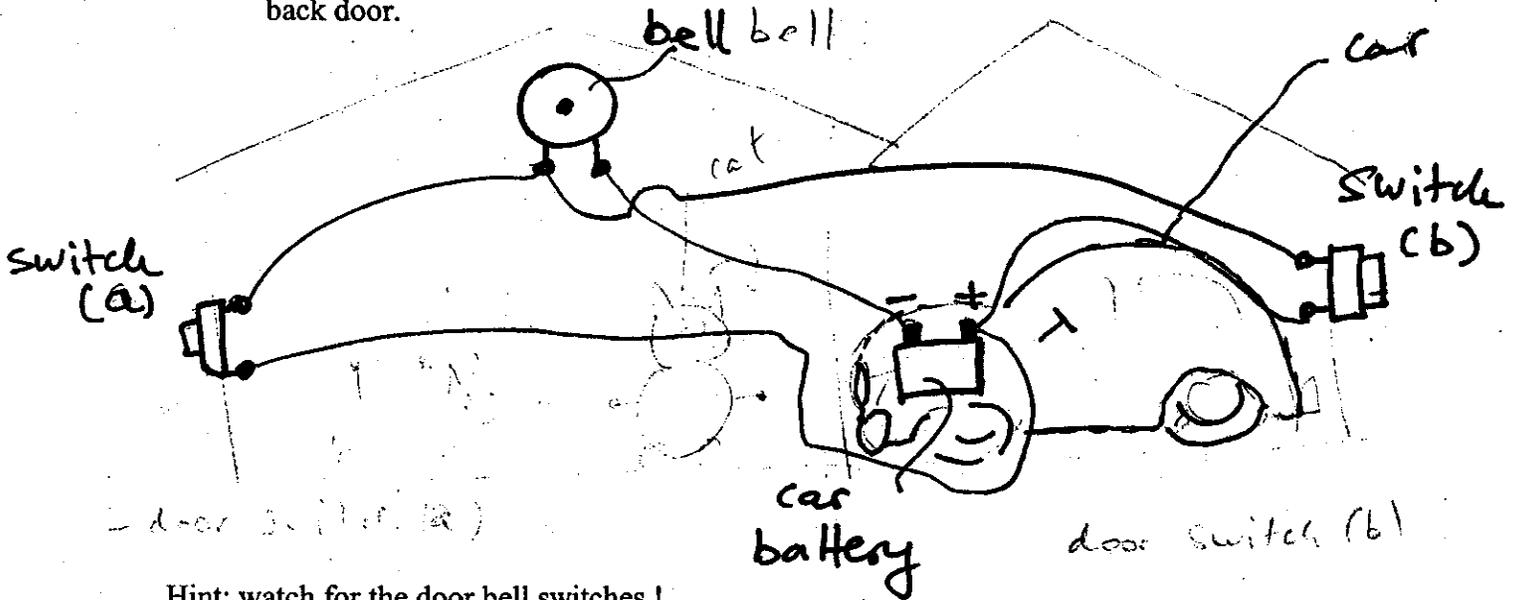Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No!


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No!

Your Name: _____

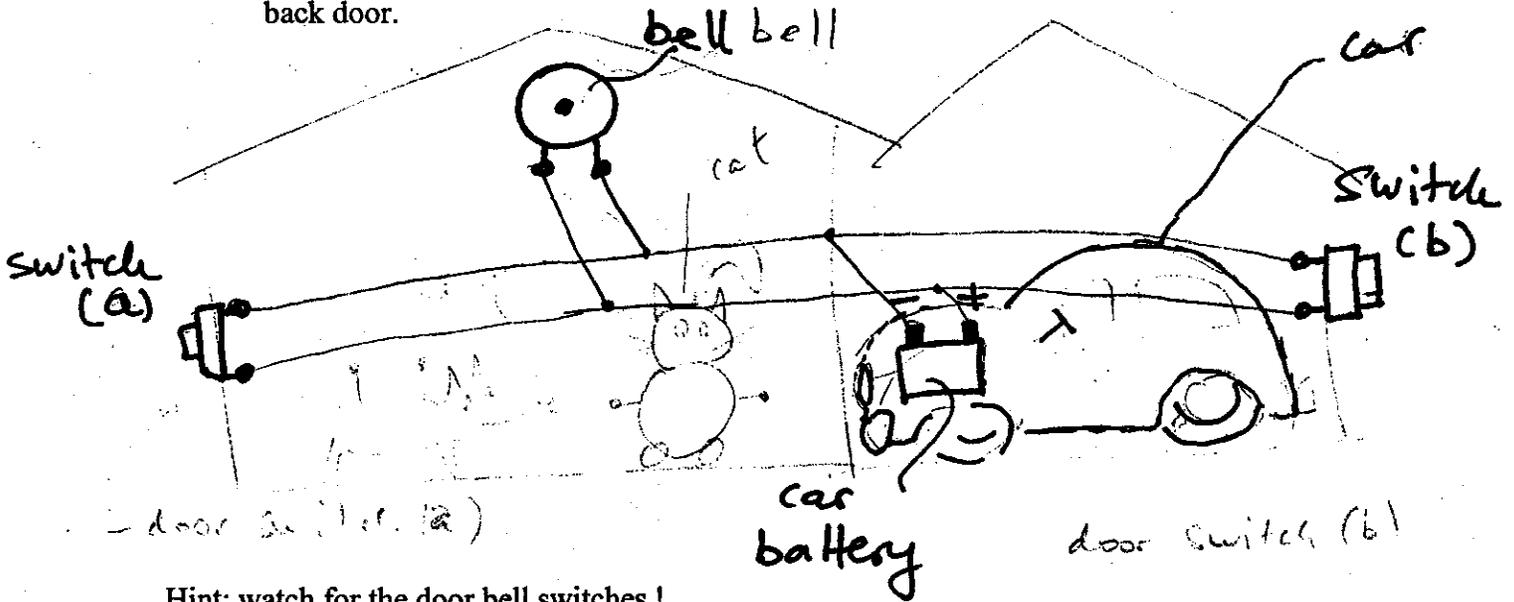Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = ab + a\bar{b} + \bar{a}b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No, because the battery is not there.


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No, because the bell ring when pressed the contact. , alarm is off does not mean there is contact.

Your Name: _____

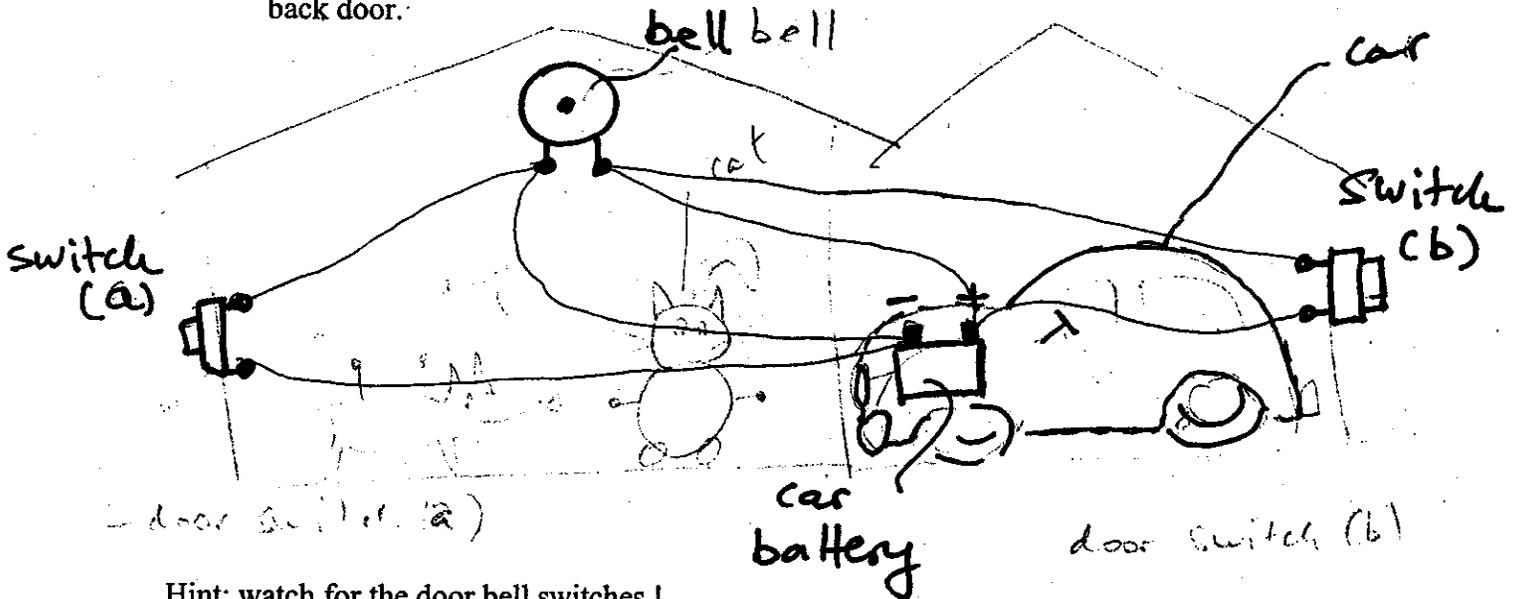Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring?
 No unless the wires are still connected.

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring?
 Not unless the switches are ON.

Your Name:

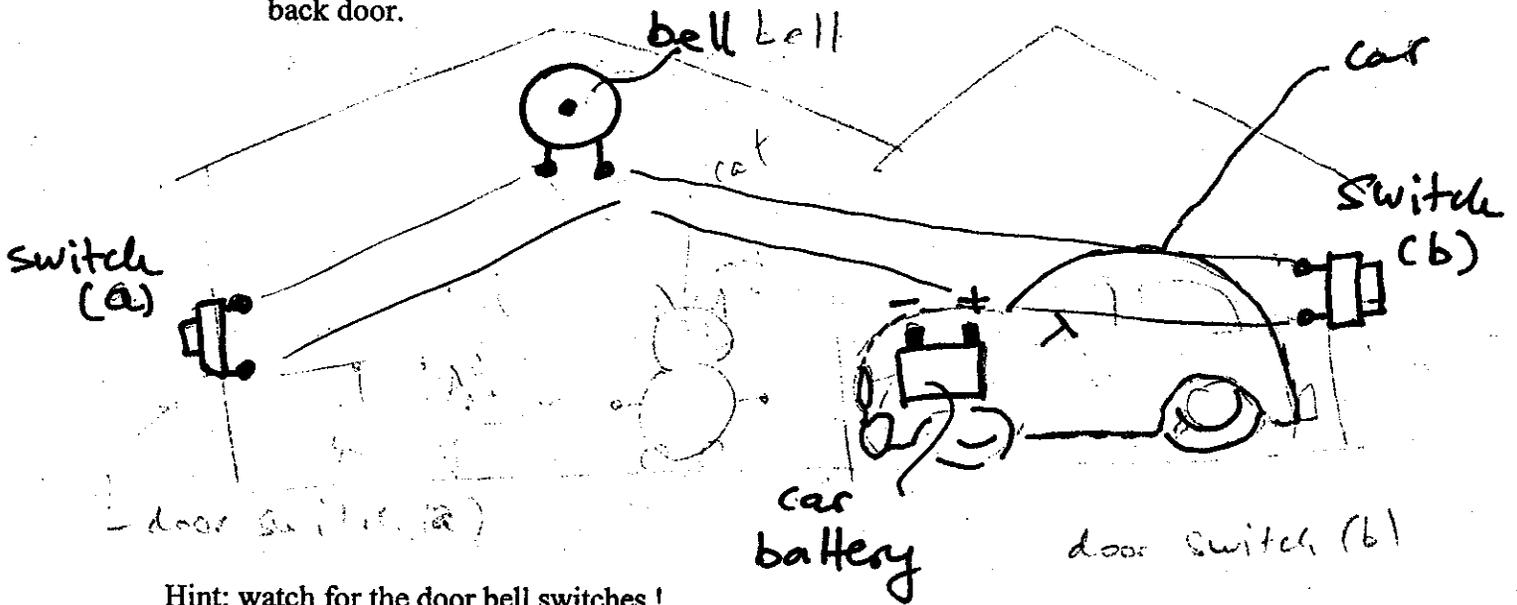Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$a \cdot \bar{b} + \bar{a} \cdot b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

$$b=1 \quad a=0 \quad 0 \cdot 0 + 1 \cdot 1 = 1 \quad \text{yes}$$


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No.

Your Name: _____

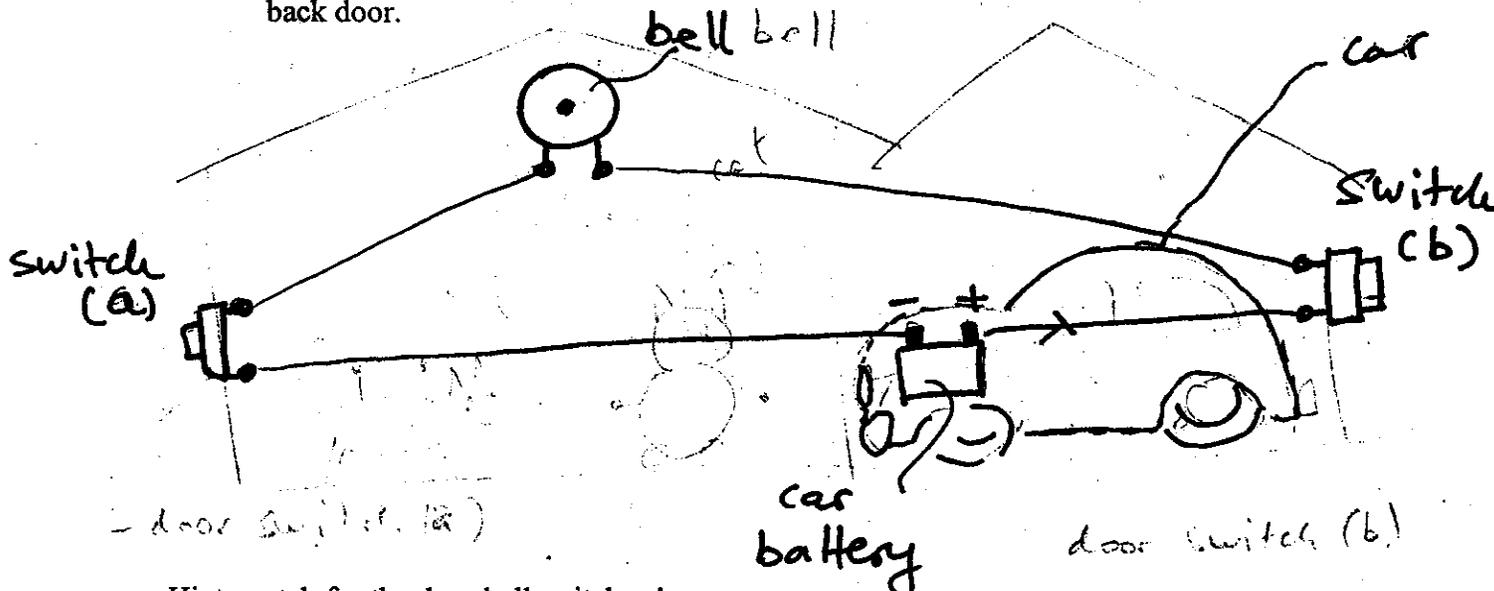Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.




Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

$f=1$ true

a	b	f
0	0	0
0	1	0
1	0	0
1	1	1

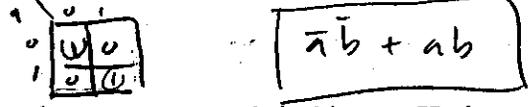i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)



(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

YES, BECAUSE WHEN DOOR BELL IS PRESSED IS ON.


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

NO, BECAUSE THE DOORBELL WAS NOT PRESSED.

Your Name: _____

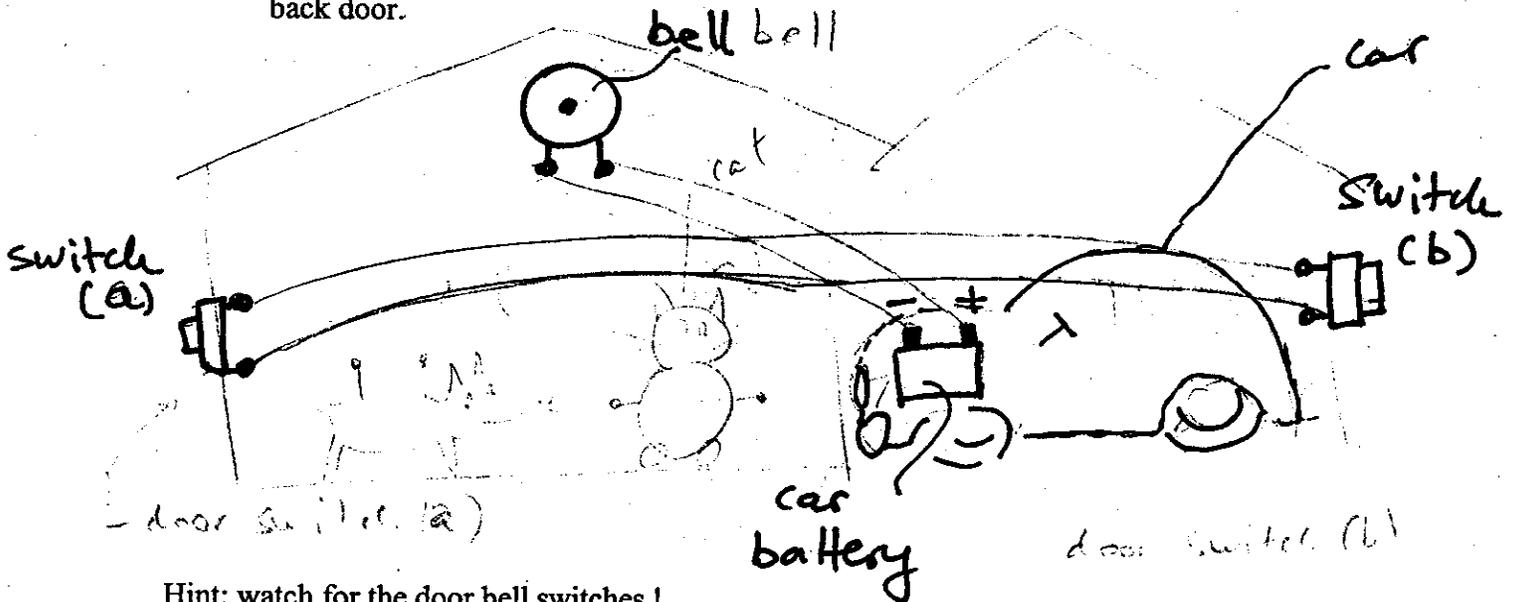Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = ab + \bar{a}b + a\bar{b}$$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring? *No*

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring? *No*

Your Name: _____

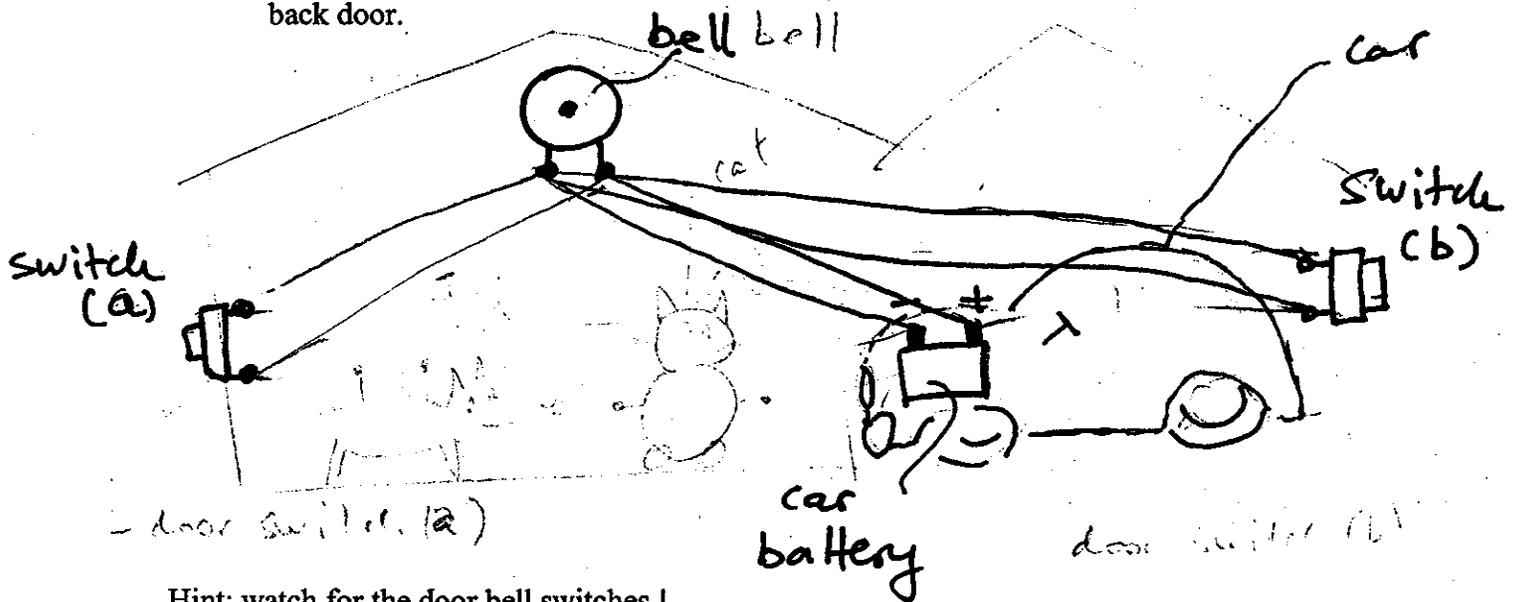Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a\bar{b} + \bar{a}b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No, the car battery is hooked up to the bell


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

Yes

Your Name: _____

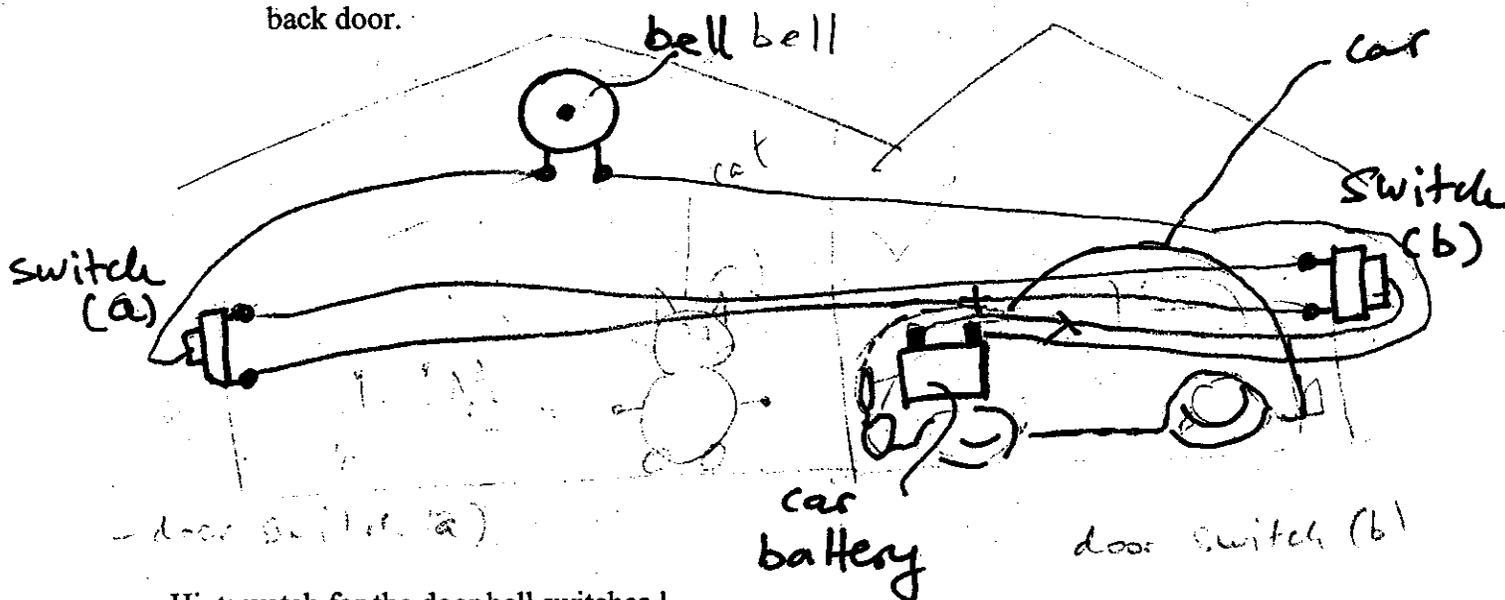Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f = ab + \bar{a}\bar{b} + \bar{a}b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No, There is no power,


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

Only if someone pushed the bell, since in parallel the bell should ring if either switch is pushed,

Your Name: _____ 21

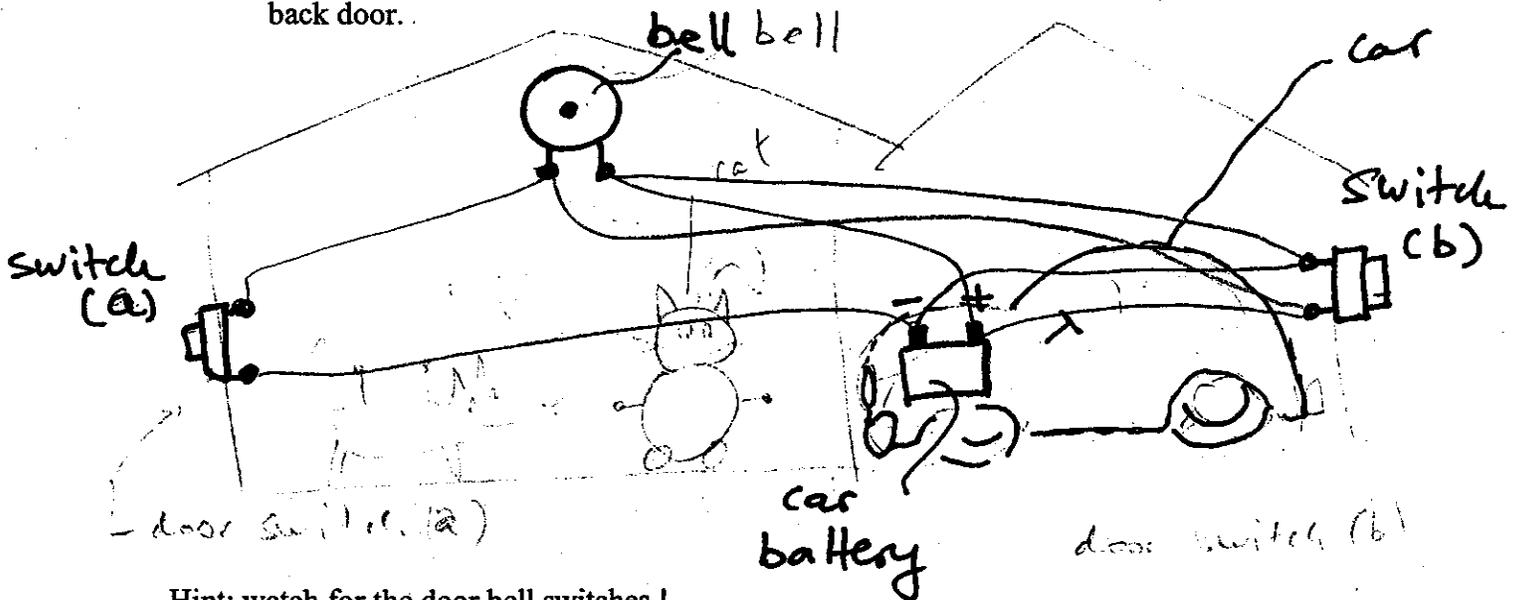Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy conscientious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

Yes


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No

Your Name: _____

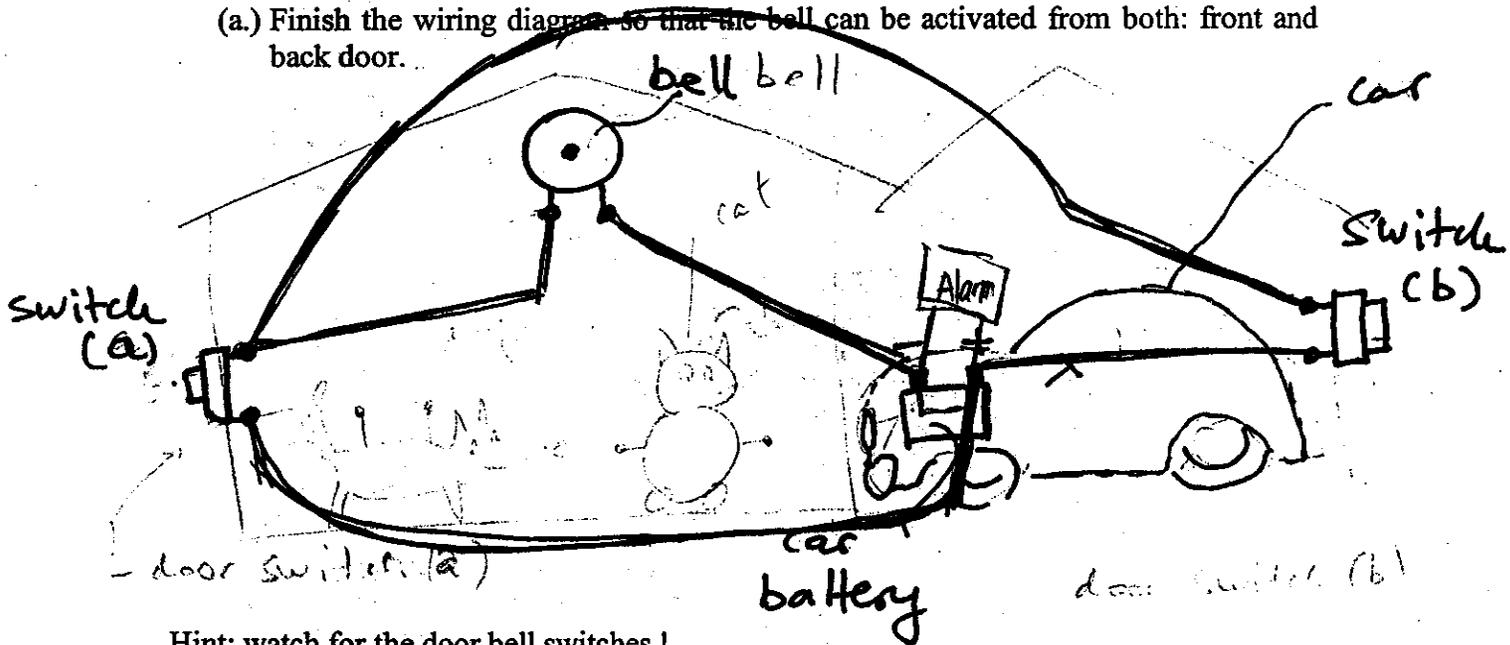Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = (a + b)$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

no


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

no

Your Name: _____

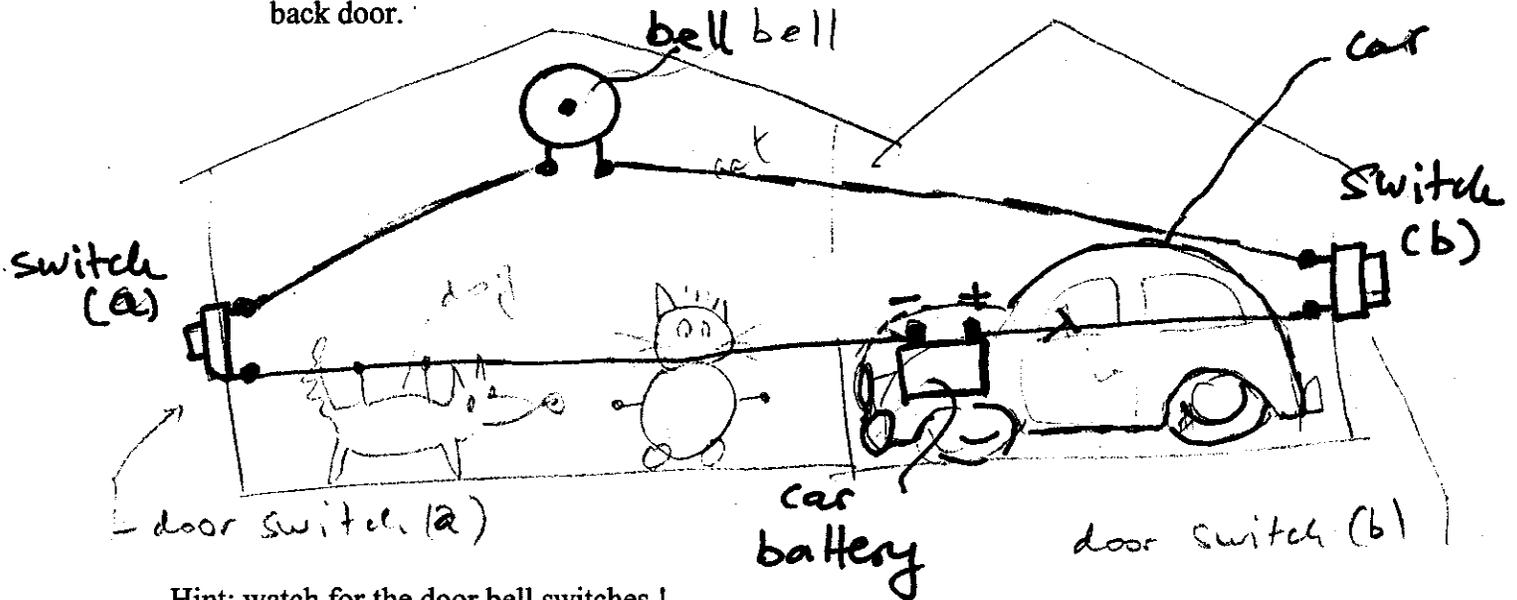Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f = a\bar{b} + \bar{a}b$$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring? It depends on how recently he left, since the switch acts as a capacitance which holds a charge for a short amount of time.

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring? no the car alarm uses the battery, but the switch must complete the circuit

Your Name: _____

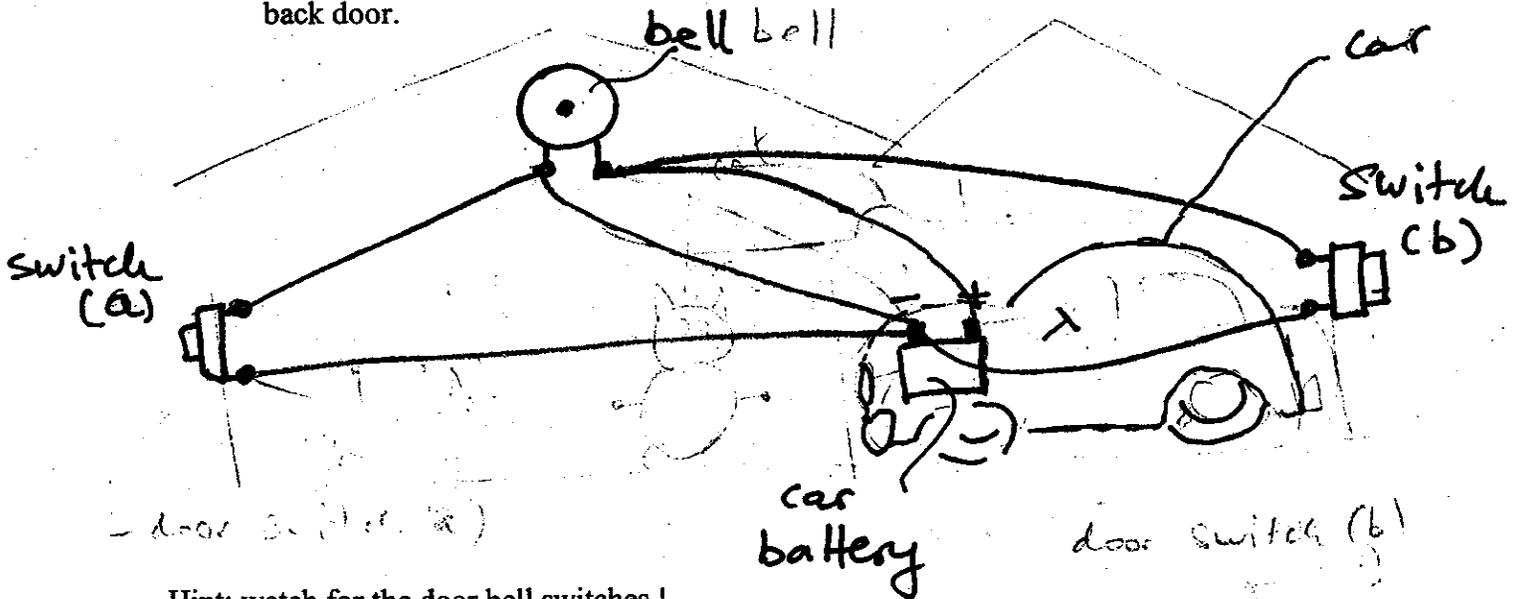Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No, it doesn't.


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No. it doesn't

Your Name: _____

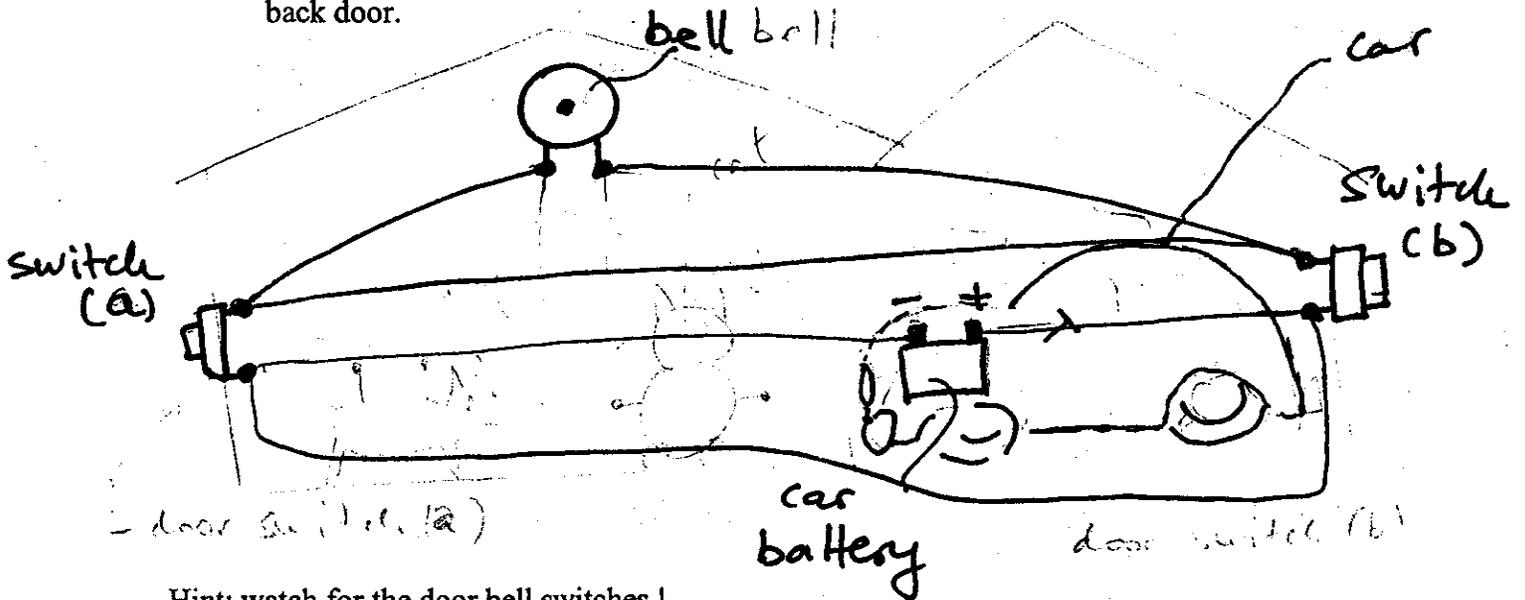Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f = \bar{a}b + \bar{b}a + ab$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

NO

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?


NO, The switches have to be connected

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

Your Name: _____

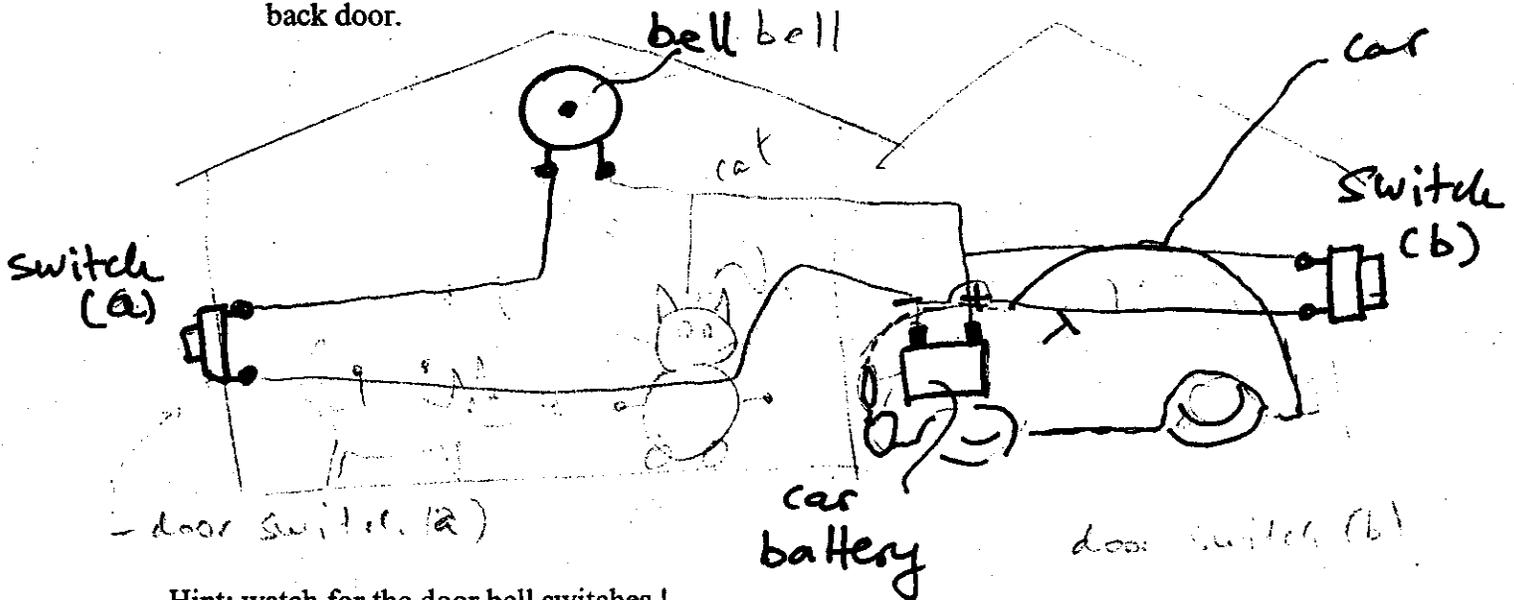Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.




Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)
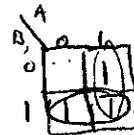
$$\begin{aligned} & \bar{A}\bar{B} + \bar{A}B + A\bar{B} \\ & = A + B \end{aligned}$$




(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

Not if the doorbell is connected to the car battery source.

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

Not unless the button is pushed to close the circuit.


a)

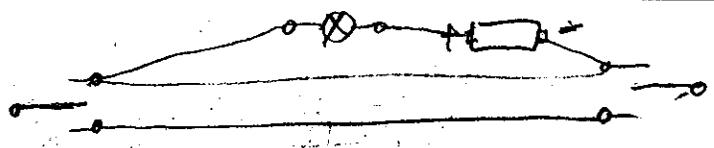

Your Name: _____

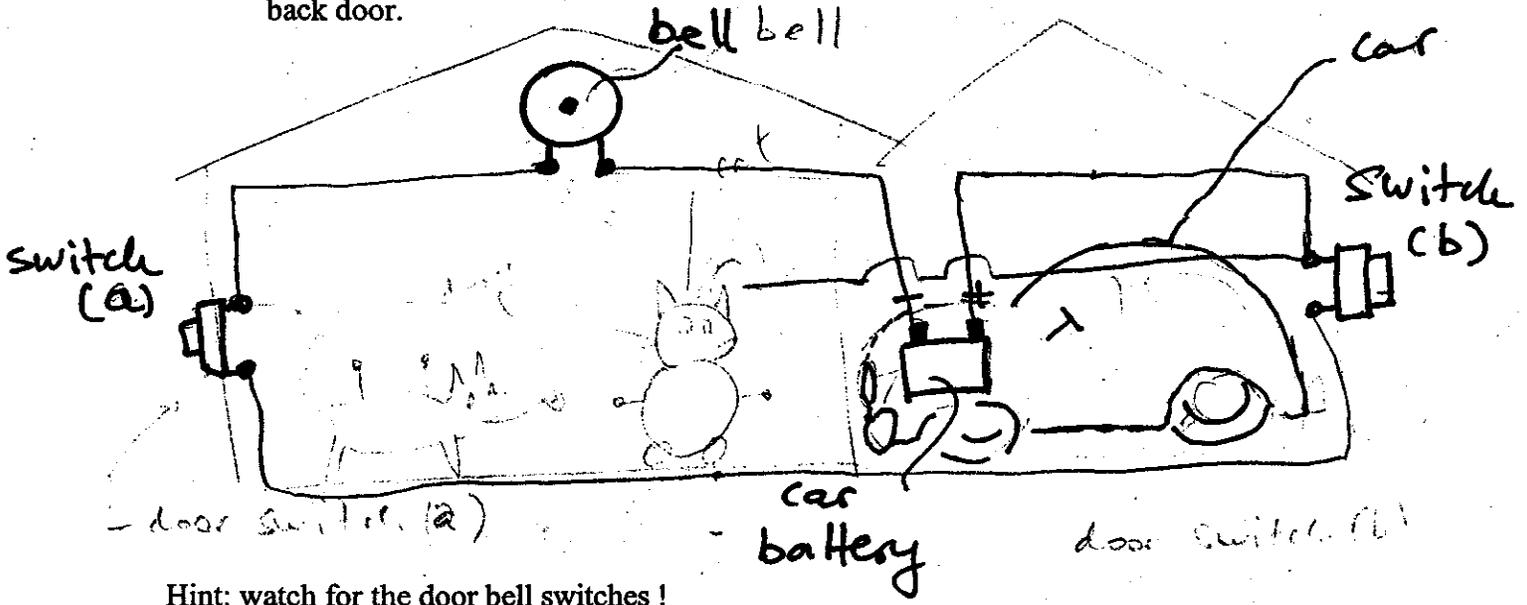Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

✓ (a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

✓ (b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No voltage, no ring.


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

No

Your Name: _____

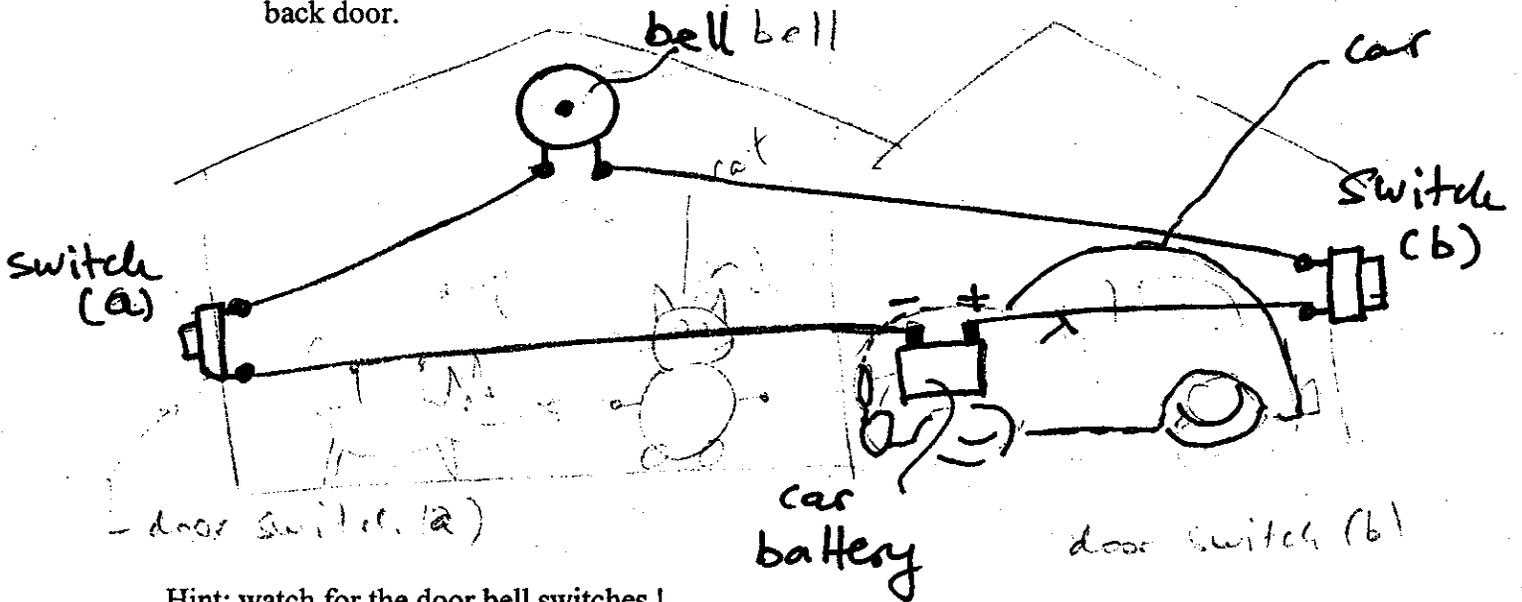Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

There's no voltage \rightarrow The bell would not ring.


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

The doorbell would ring, \rightarrow have voltage

Your Name: _____

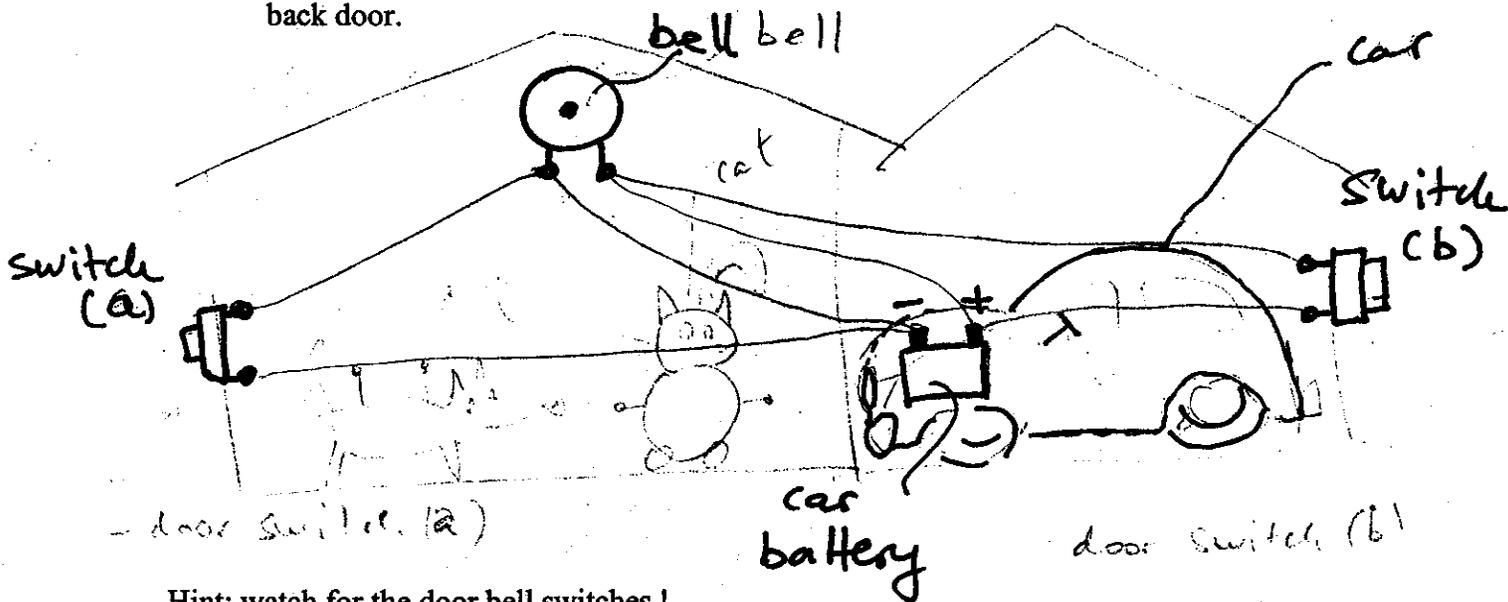Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)


$$f(a,b) = a + b$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

no, the battery go with the car

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?


no.

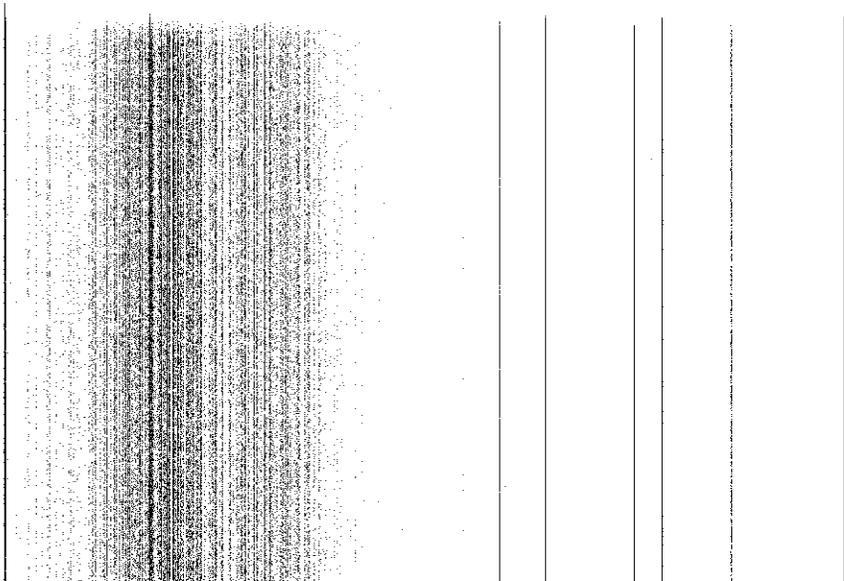

Your Name: _____

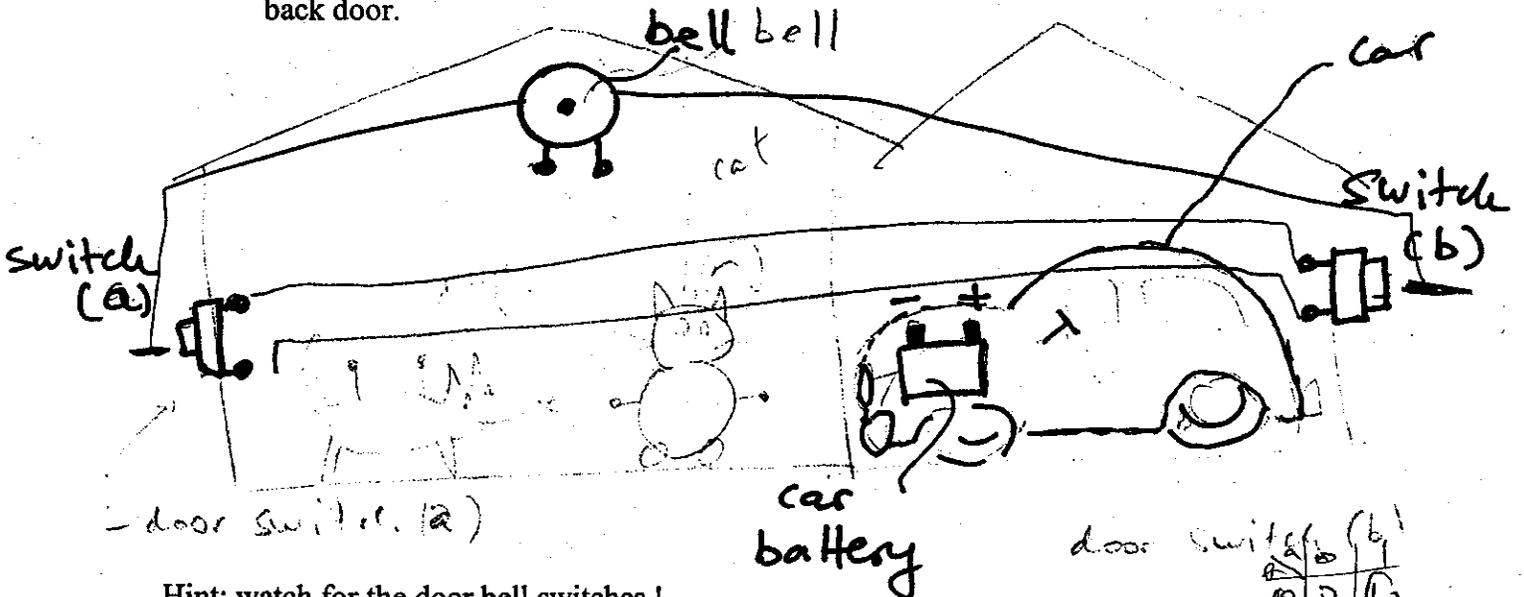Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

$f(a,b) =$

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$f(a,b) = a + b = \bar{a}b + a\bar{b} + ab$

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

No it won't ring because there is no battery


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

yes it would ring because the battery is working

Your Name: _____

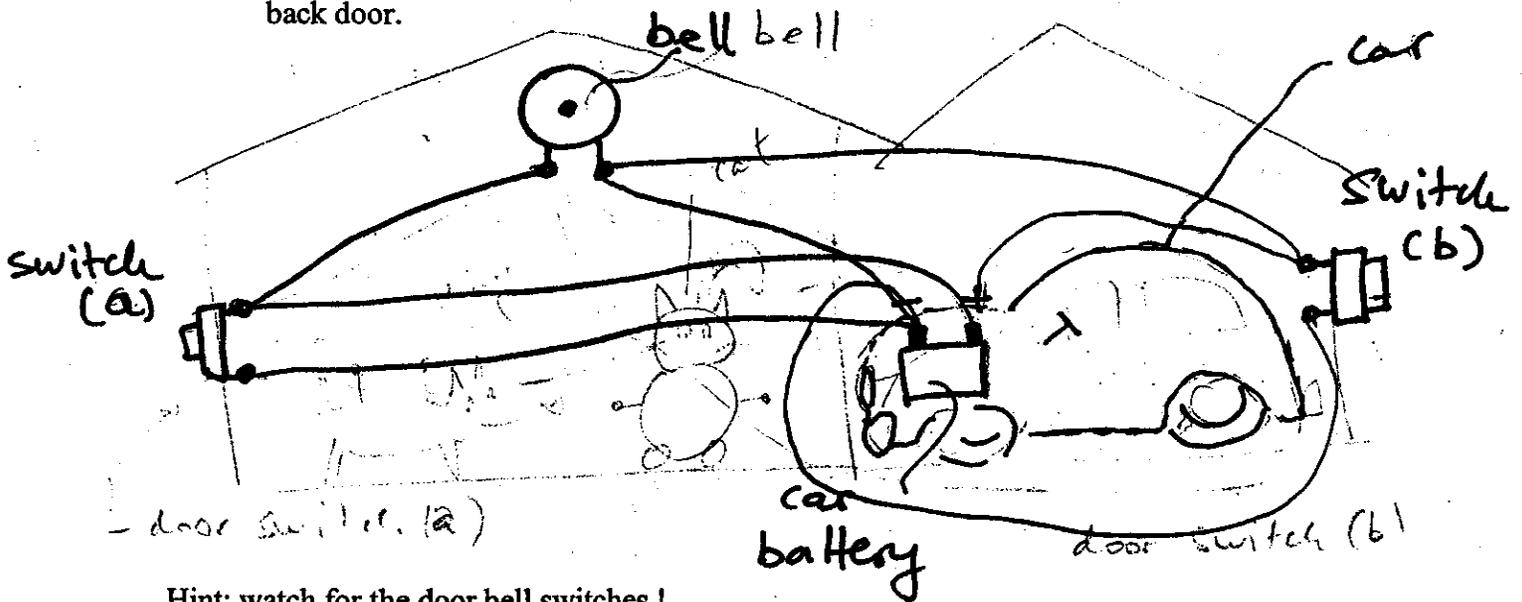Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a + b$$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring? *NO because there is no power for the door bell.*

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring? *Yes because there is a flow of power connected to the door bell.*

Your Name: _____

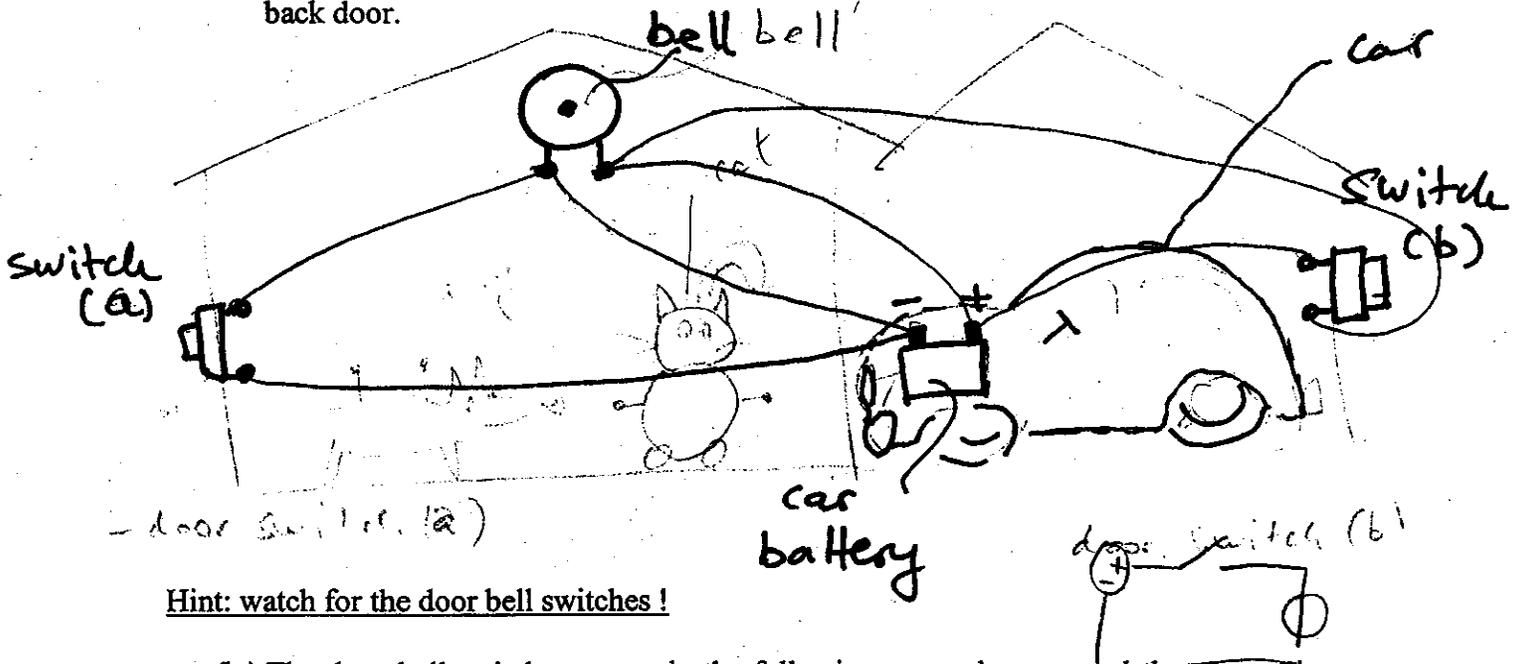Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)
 $= (a + b)$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

NO, BEN HAS HIS CAR @ WORK


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

YES, IF ENOUGH VOLTAGE TO POWER BELL W/ ALARM ON.

Your Name: _____

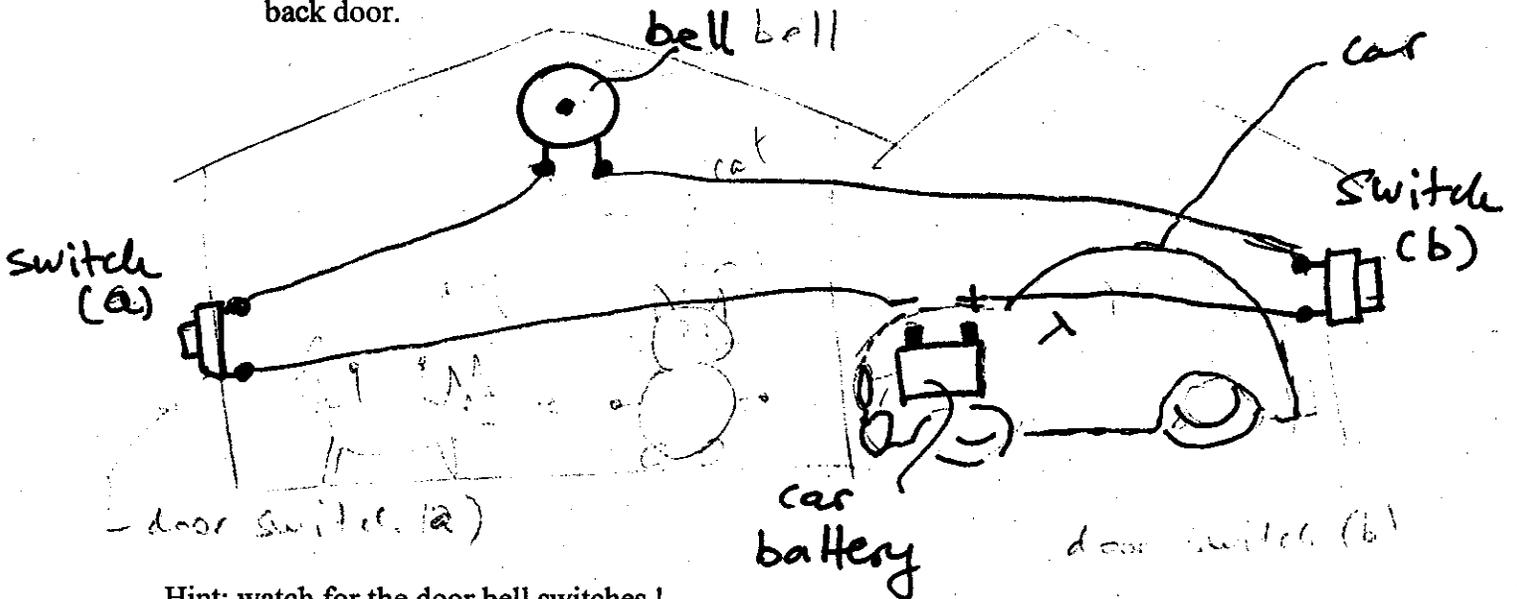Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$f = a + b$

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring? *Not without a battery*

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring? *no*

Your Name: _____

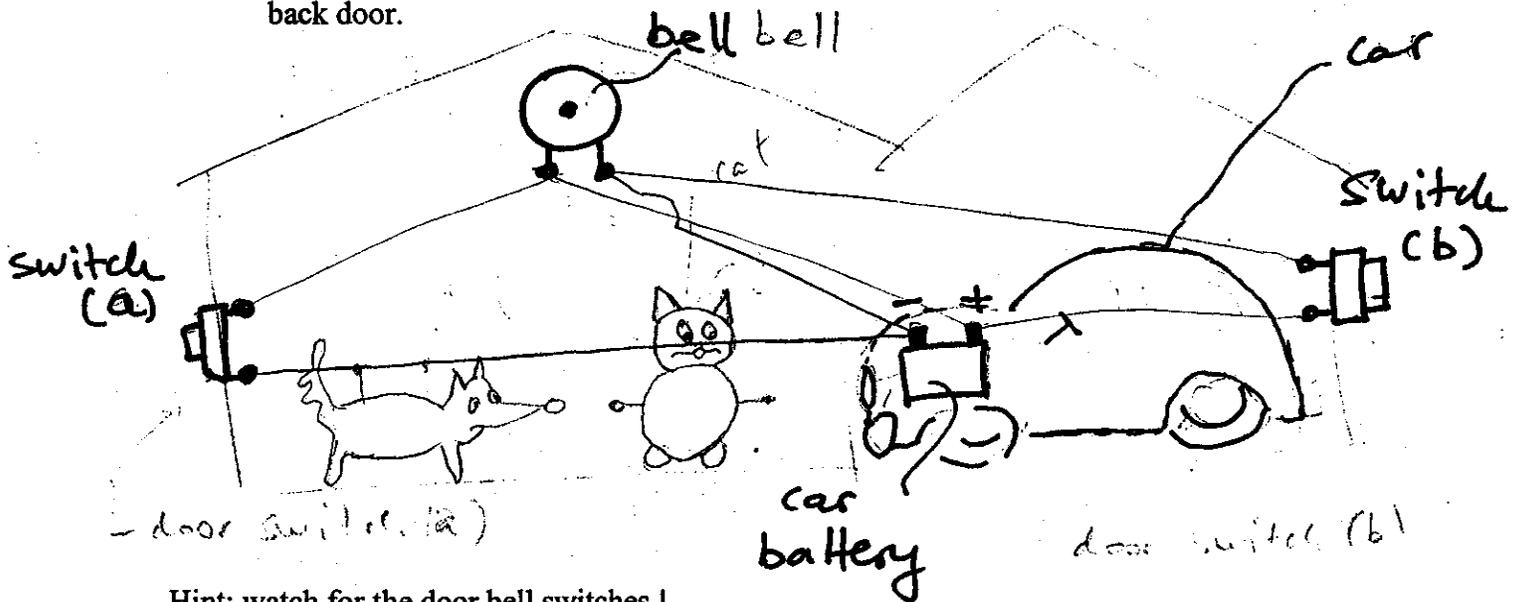Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell swithes a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$) $a + b$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ? NO

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ? NO

Your Name: _____

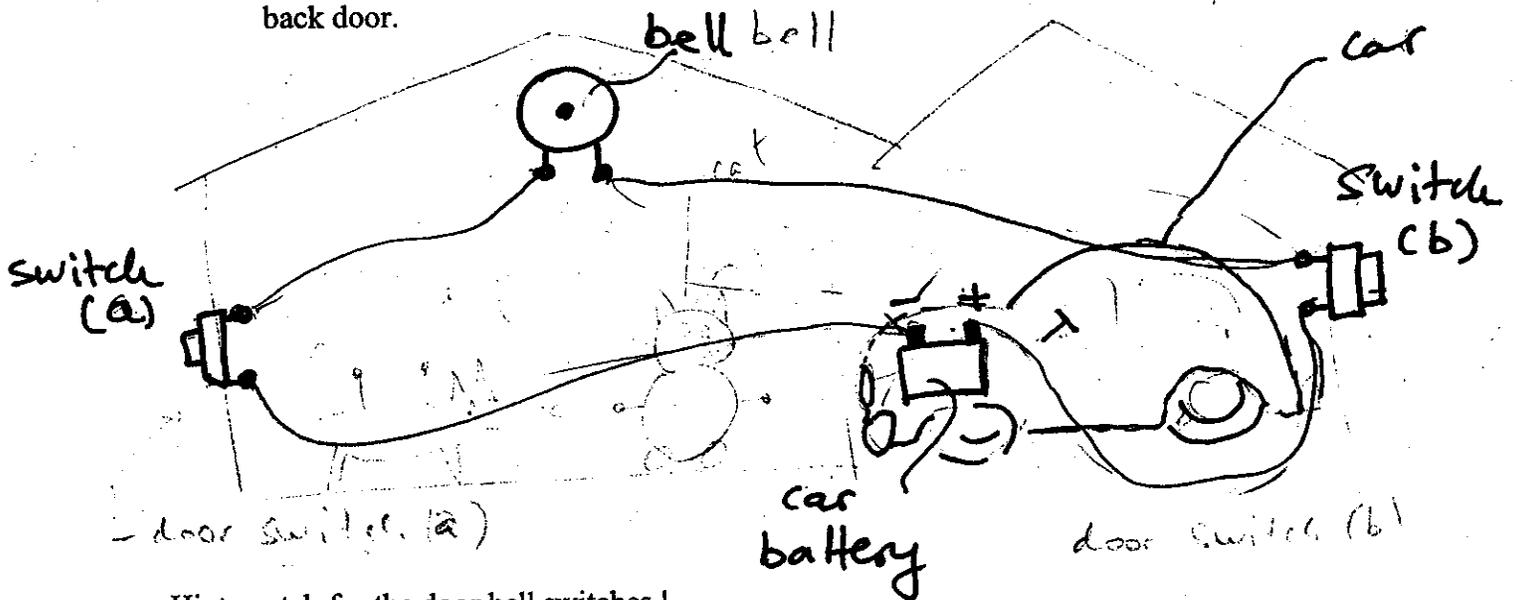Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f(a,b) = a \bar{b}$$

(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring ?

yes


(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring ?

NO

Your Name: _____

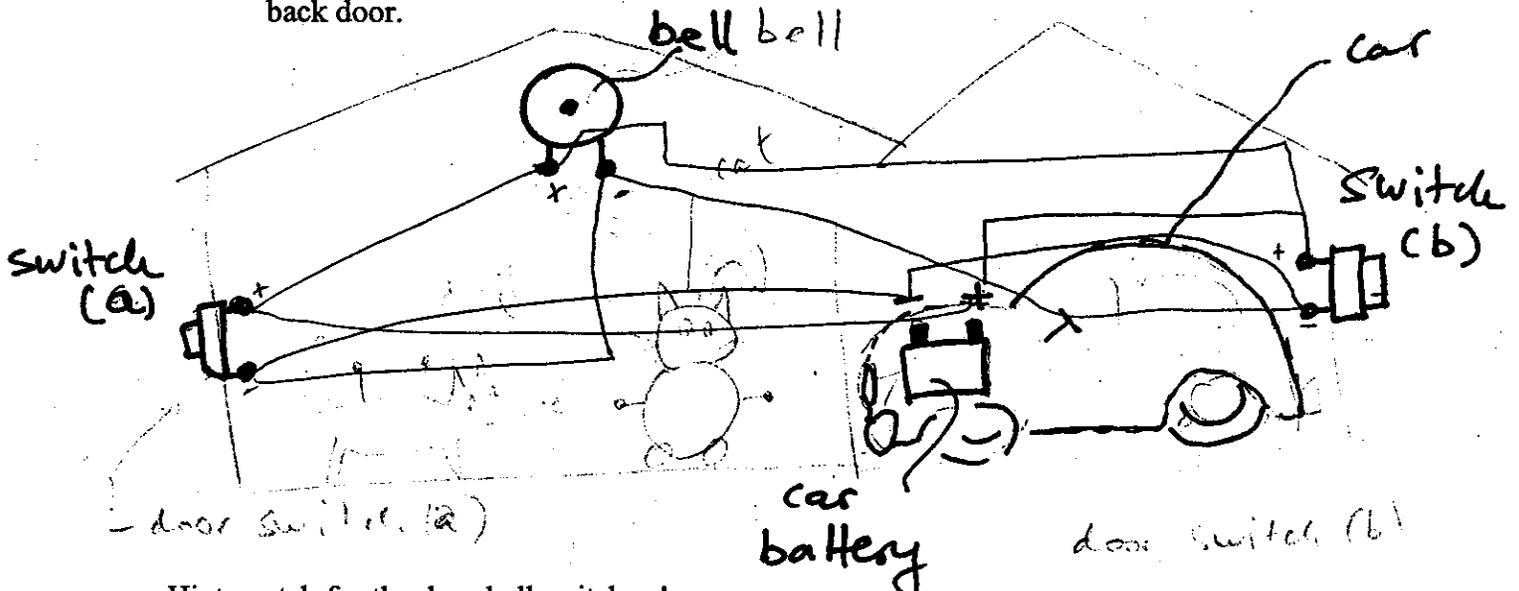Problem #1: Ben is an engineer working in the Silicon Valley start-up company. He is very energy consciencious. In order to save on his electricity bill he wants to use his car battery to power his door bell.

(a.) Finish the wiring diagram so that the bell can be activated from both: front and back door.



Hint: watch for the door bell switches !

(b.) The door bell switch operates in the following way: when pressed the contact is ON. When released - there is no contact (it is OFF). What is the logical expression for the door bell as a function of the two door bell switches a and b ?

i.e. $f(a,b) = ?$ (assume that door bell rings when $f=1$)

$$f = a + b$$


(c.) Ben has gone to work in his car. He is now sitting at a shareholders meeting of his company in San Jose. The mailman came to his back door to deliver his dividend check and he is pressing the door switch. Would the bell ring?
 Yes, NO, The car is gone

(d.) Ben is sleeping. The cat accidentally jumped on the top of his car and scared the dog. The dog started barking and this triggered Ben's car alarm. Would the door bell ring?
 Yes, because battery would be triggered also.

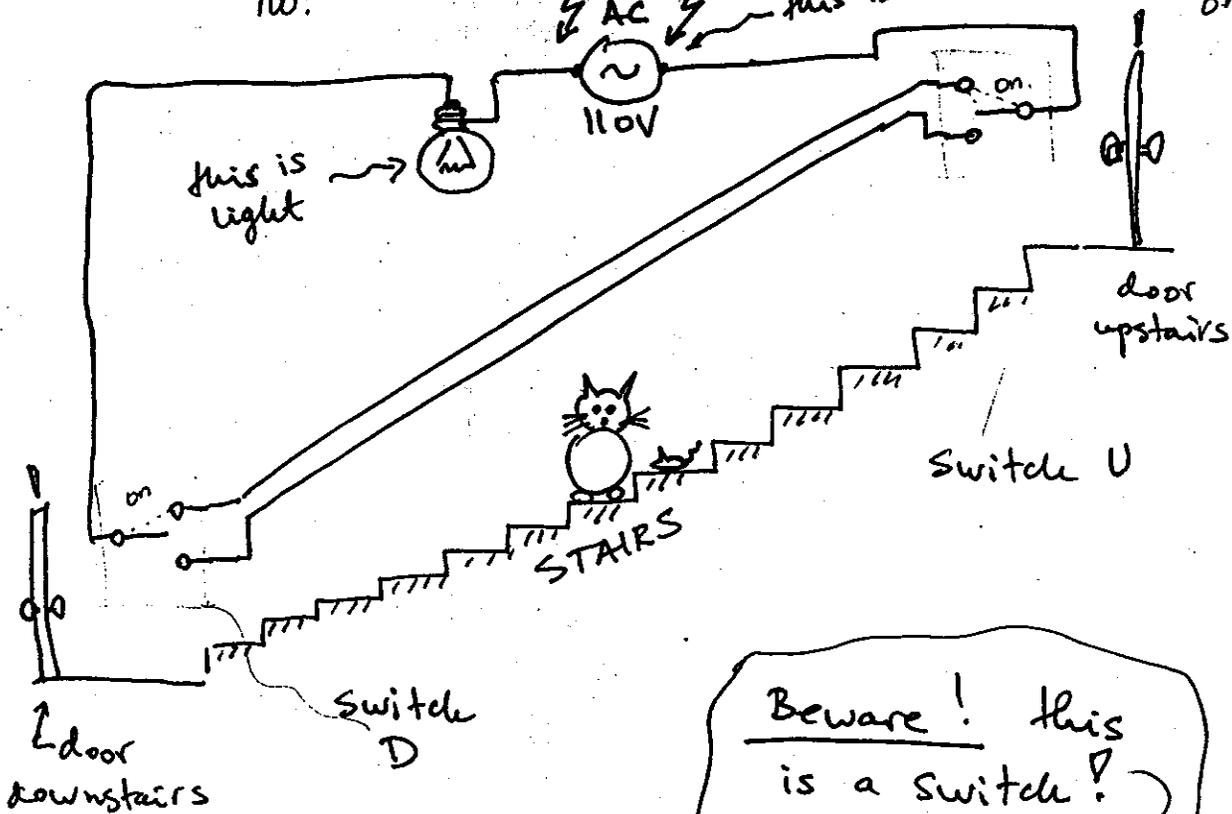Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

- (a.) I.e. $L=f(U,D)$. Write this expression and explain! ~~if~~ if either D is a 1 or U is a 1 then the light will be turned on.
 $L = D + U$
 (b.) could this expression be minimized further?
 NO.




Beware! this is a switch!

with two positions
Hint it can be only in one position.

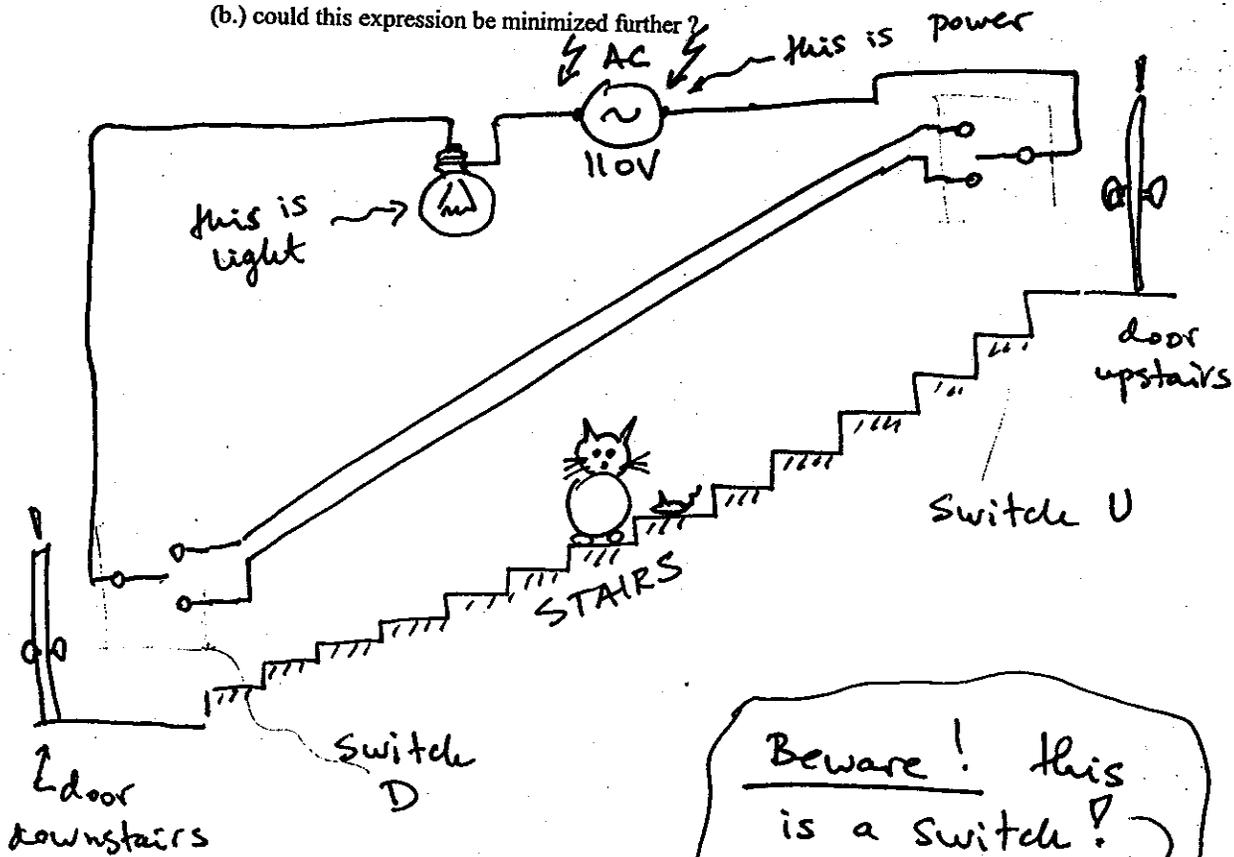Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs). If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?


(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



$$L \neq f(u, D) = 1$$

Beware! this is a switch!

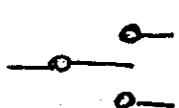


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

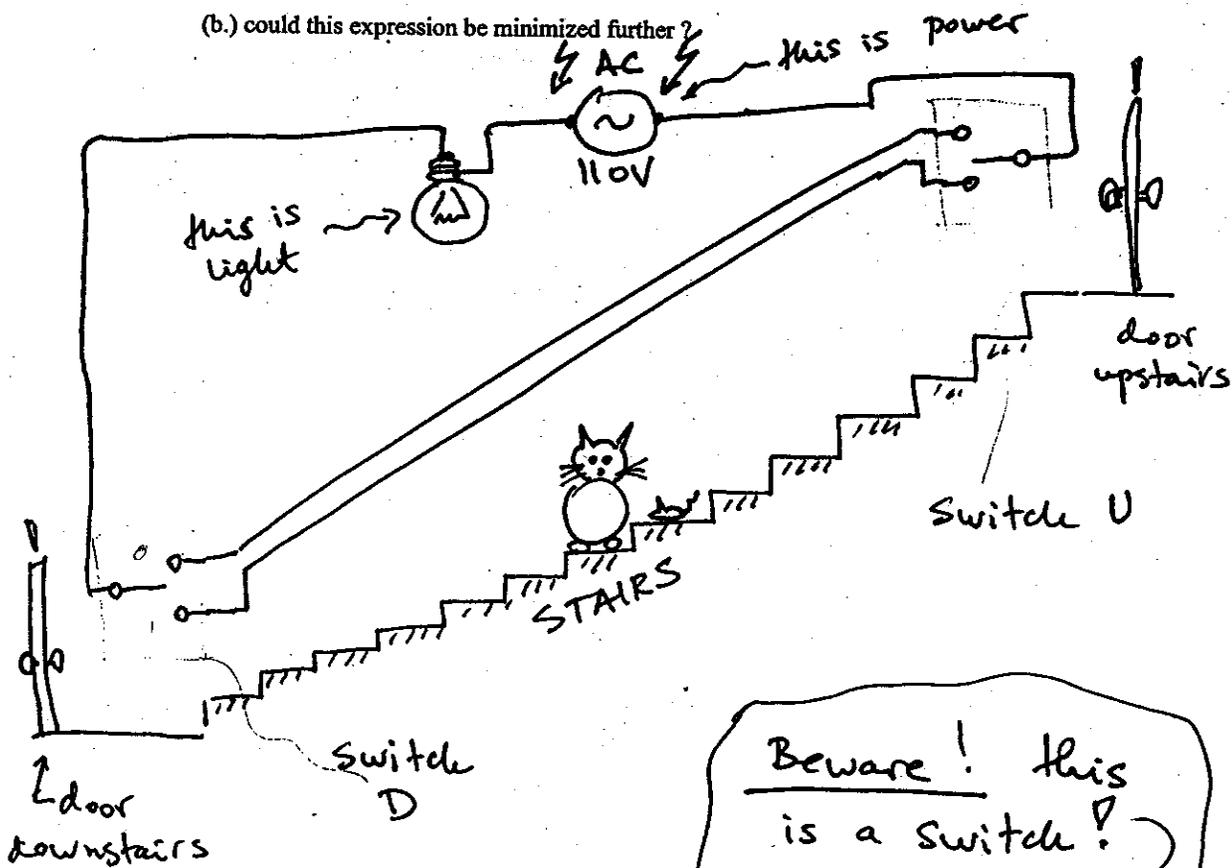(b.) could this expression be minimized further?



a) $\bar{D}U + D\bar{U}$

b) yes

Beware! this is a switch!


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).


If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

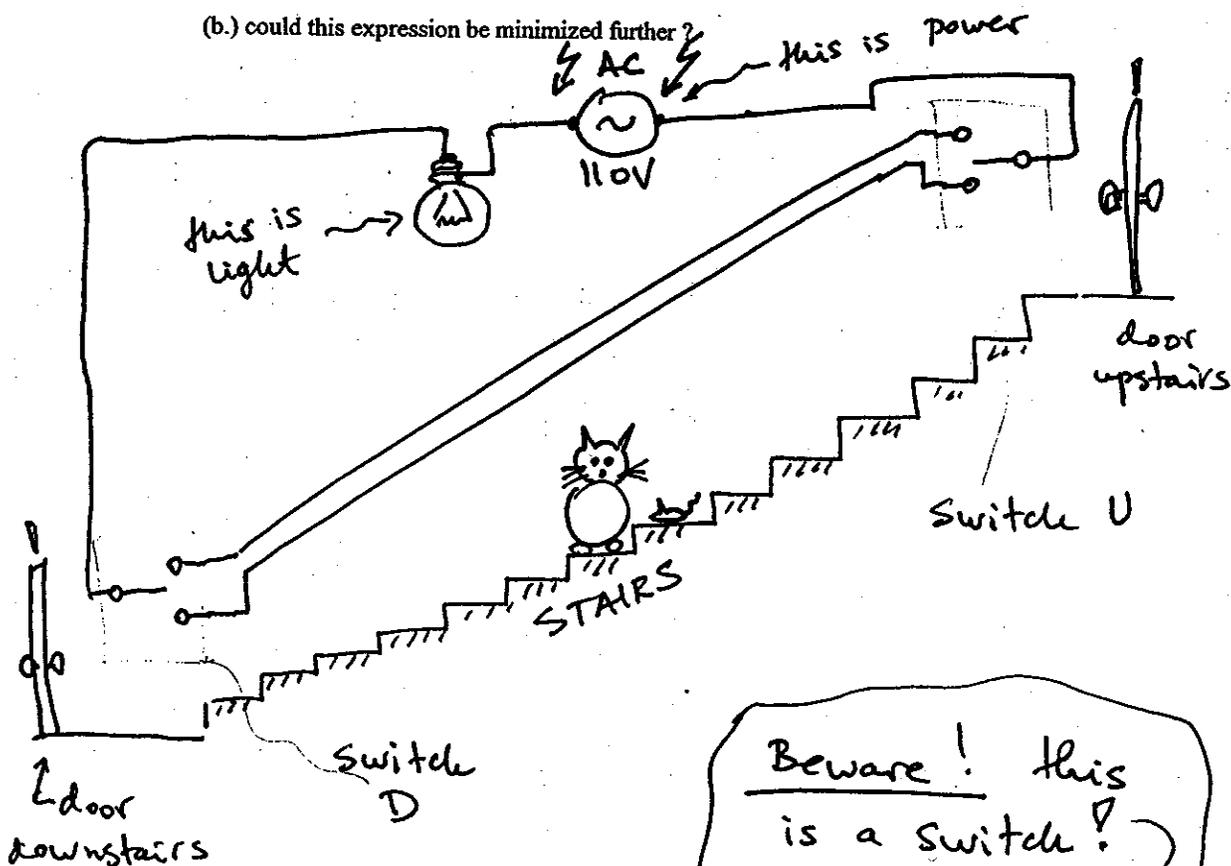(b.) could this expression be minimized further?



Beware! this is a switch!

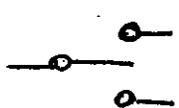


with two positions

Hint it can be only in one position.

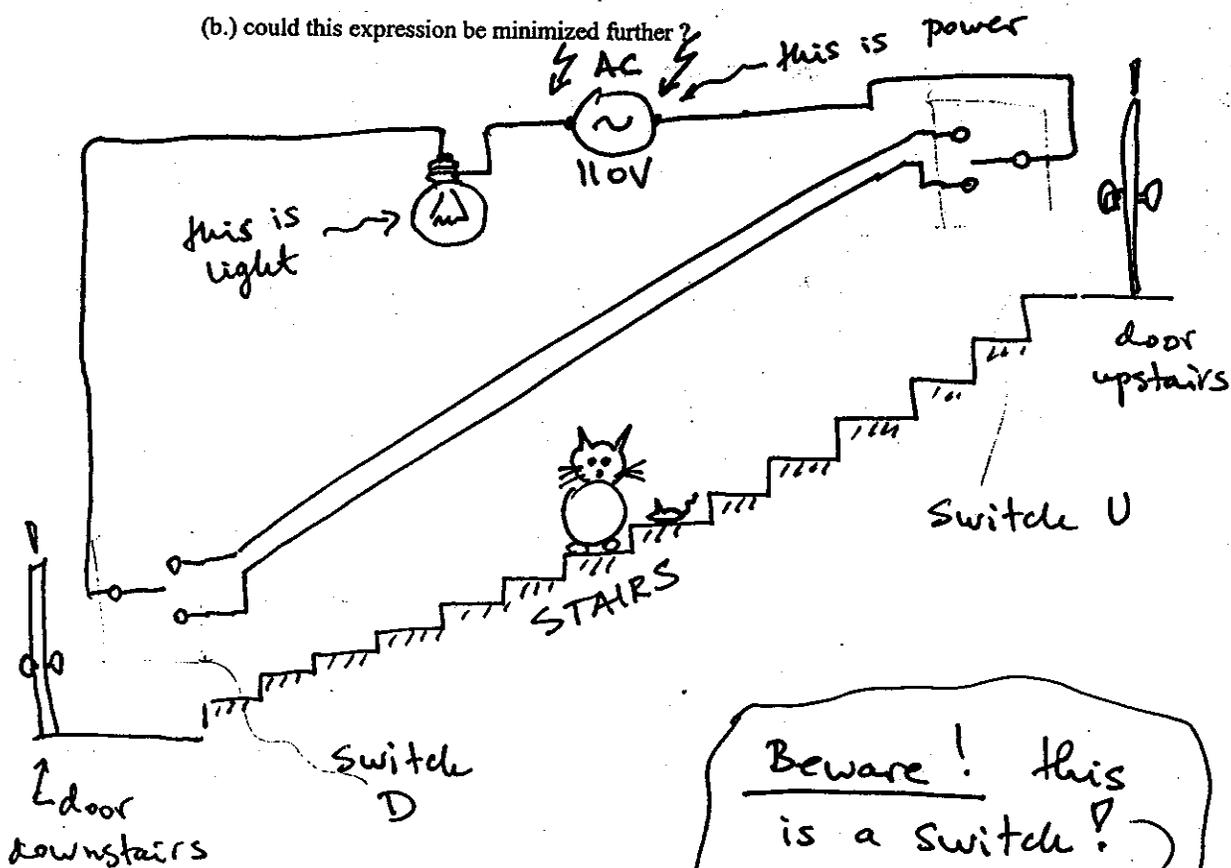Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs). If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?




Beware! this is a switch!

With two positions
Hint it can be only in one position.

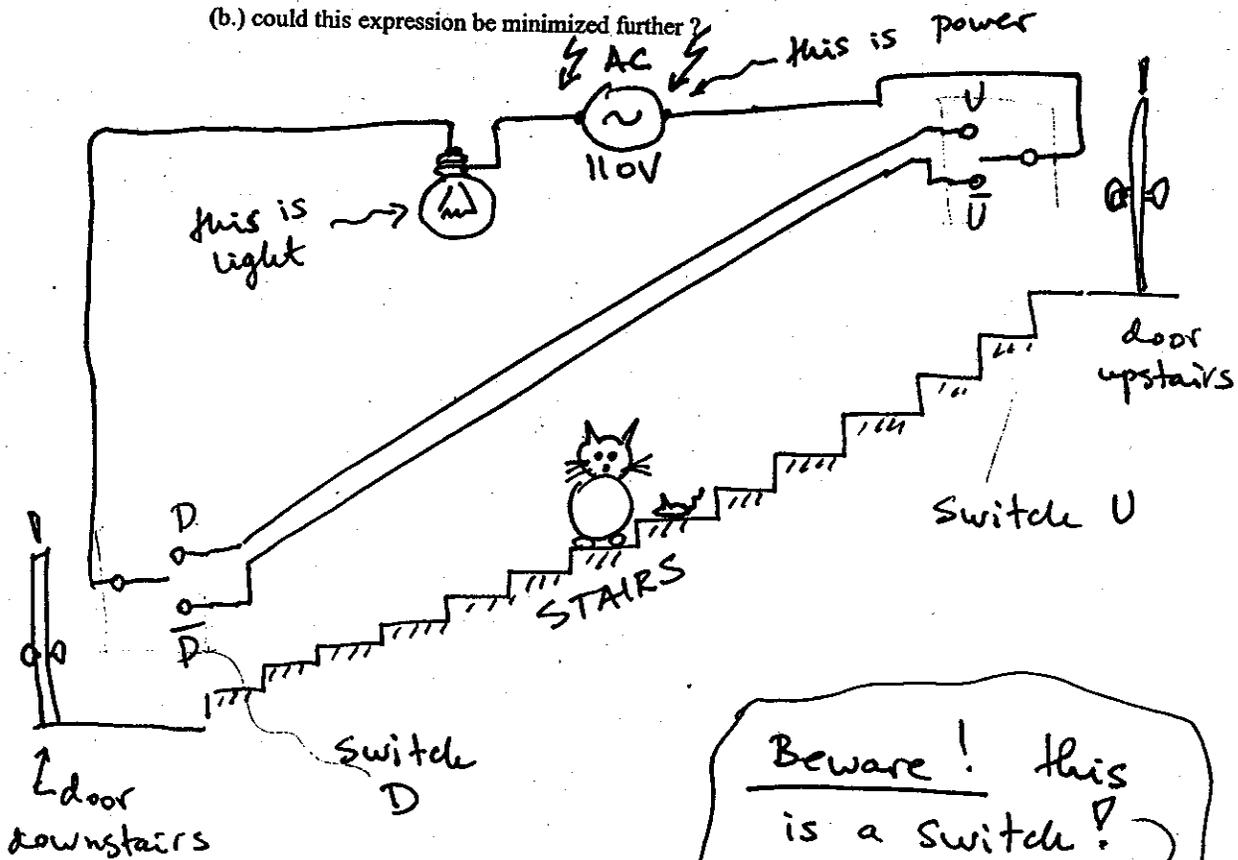Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



a) $L = f(U, D)$
 $= (U \cdot D) + (\bar{U} \bar{D})$

2 DIFFERENT COMBINATIONS
 OF SWITCHES TO HAVE
 LIGHT ON

Beware! this
 is a switch!

with two positions
Hint it can be only
 in one position.

b) $L = f(U, D)$
 $= UD + \bar{U}\bar{D}$

CAN'T BE MINIMIZED.
 FURTHER!

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).


If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

$$\bar{U}D + U\bar{D}$$

SAME AS PROB. #1

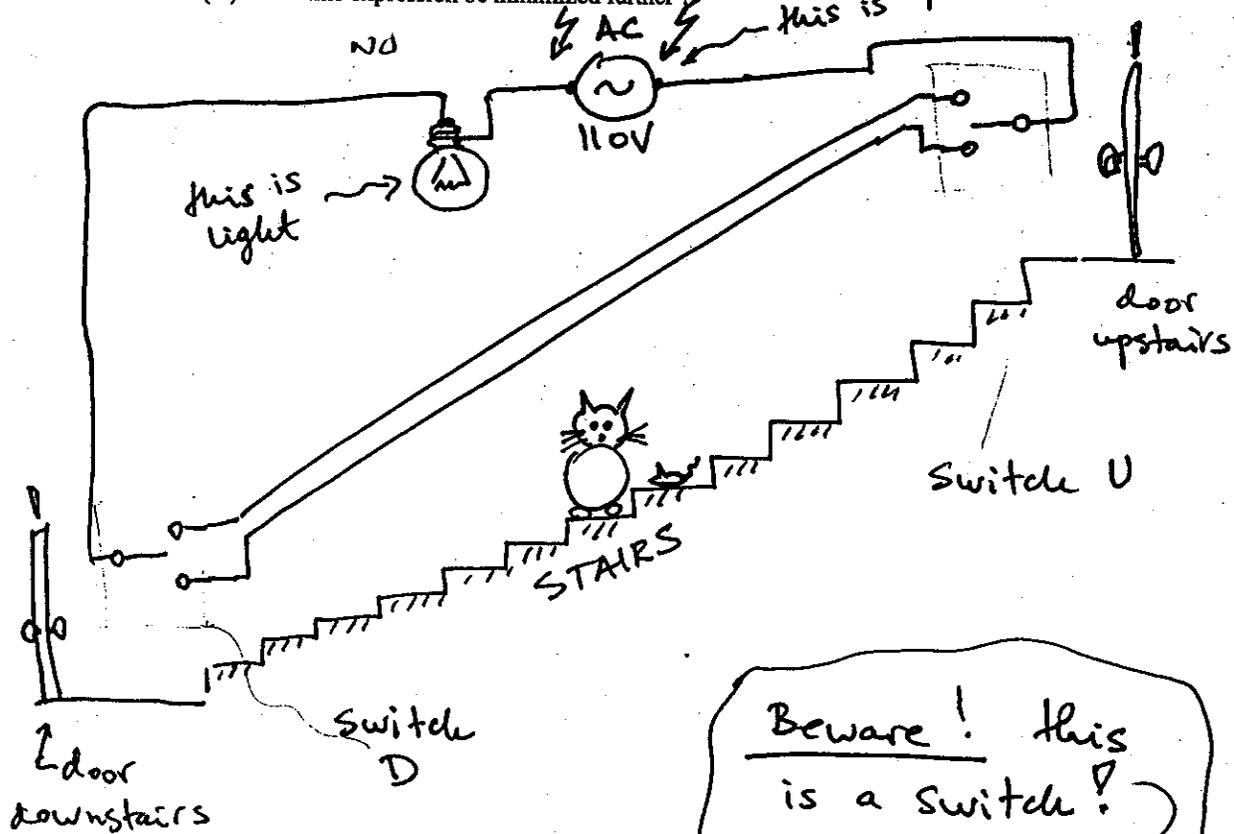(b.) could this expression be minimized further?



Beware! this is a switch!


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

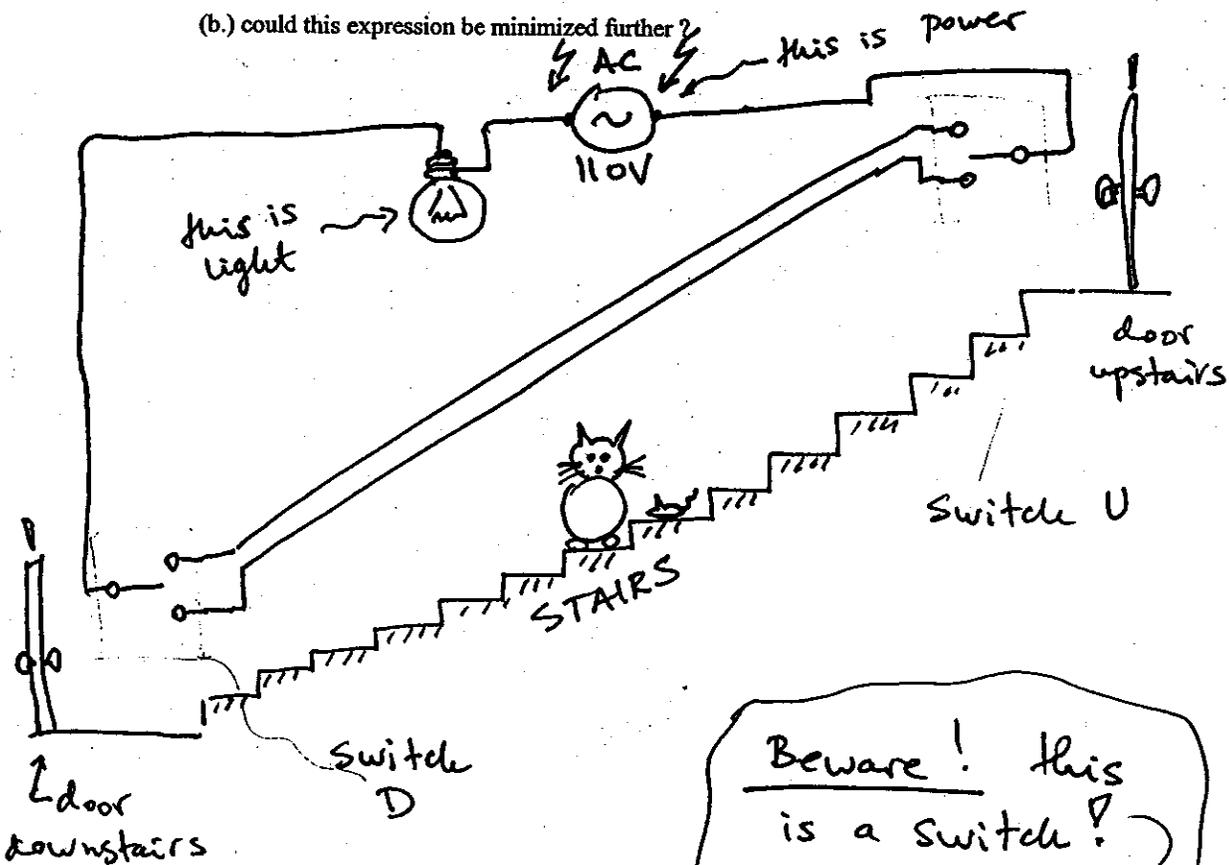(b.) could this expression be minimized further?



Beware! this is a switch!


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) i.e. $L=f(U,D)$. Write this expression and explain!

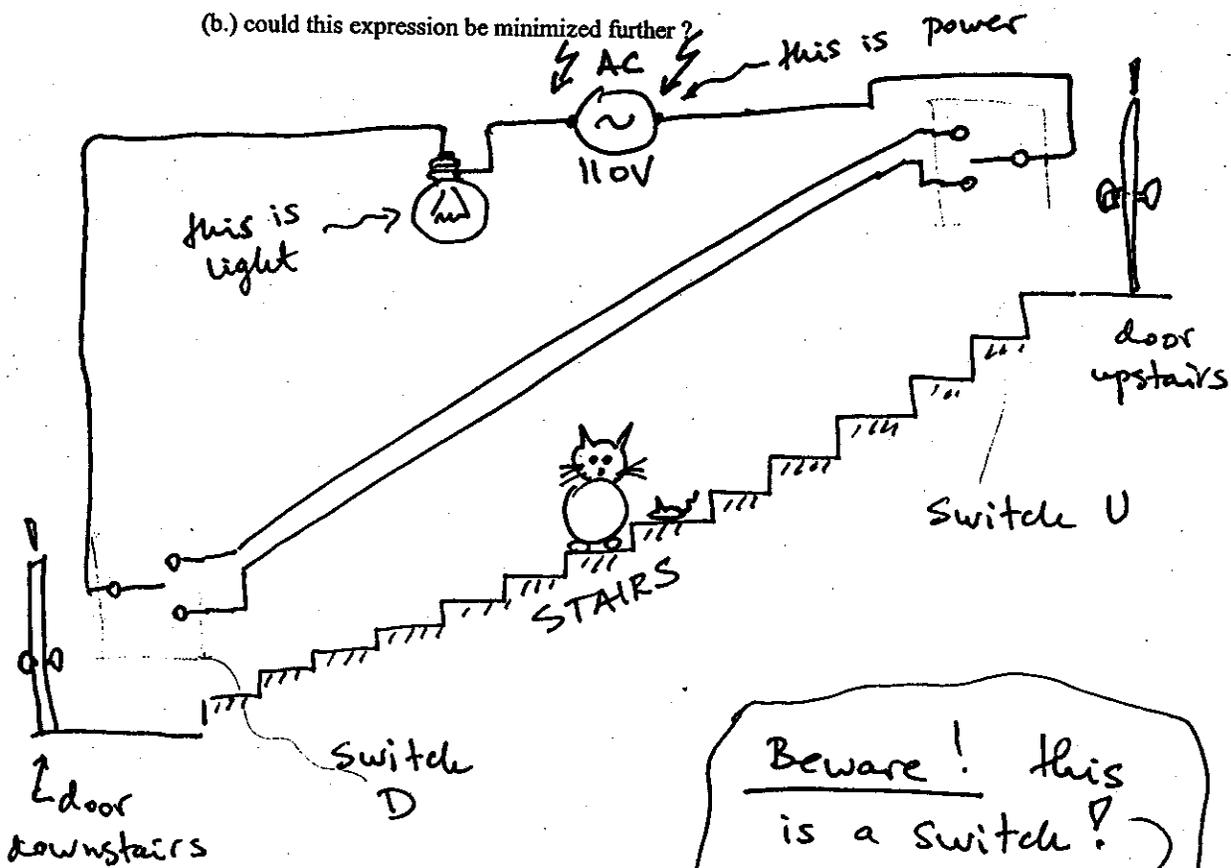(b.) could this expression be minimized further?



a). $F = UD + \bar{U}\bar{D}$
 the light is on only when you turn on one switch.

b). No, it could not be min. further

Beware! this is a switch!

 with two positions
Hint it can be only in one position.


Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs). If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) $L = \overline{U}U + \overline{U}D + UD$
 could this expression be minimized further? *yes*

D	U	L
0	0	0
0	1	1
1	0	1
1	1	1

D	U	L
0	0	0
0	1	1
1	0	1
1	1	1

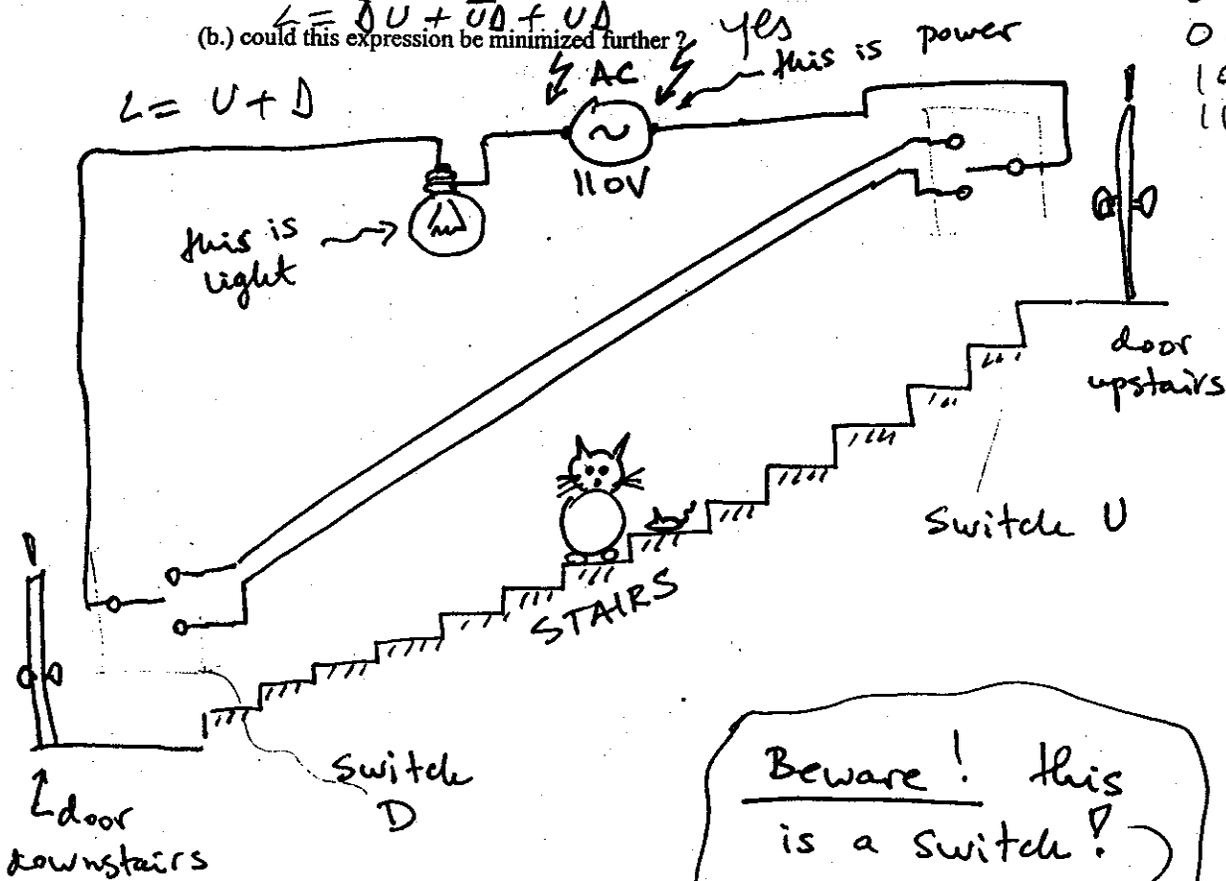

Beware! this is a switch!


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

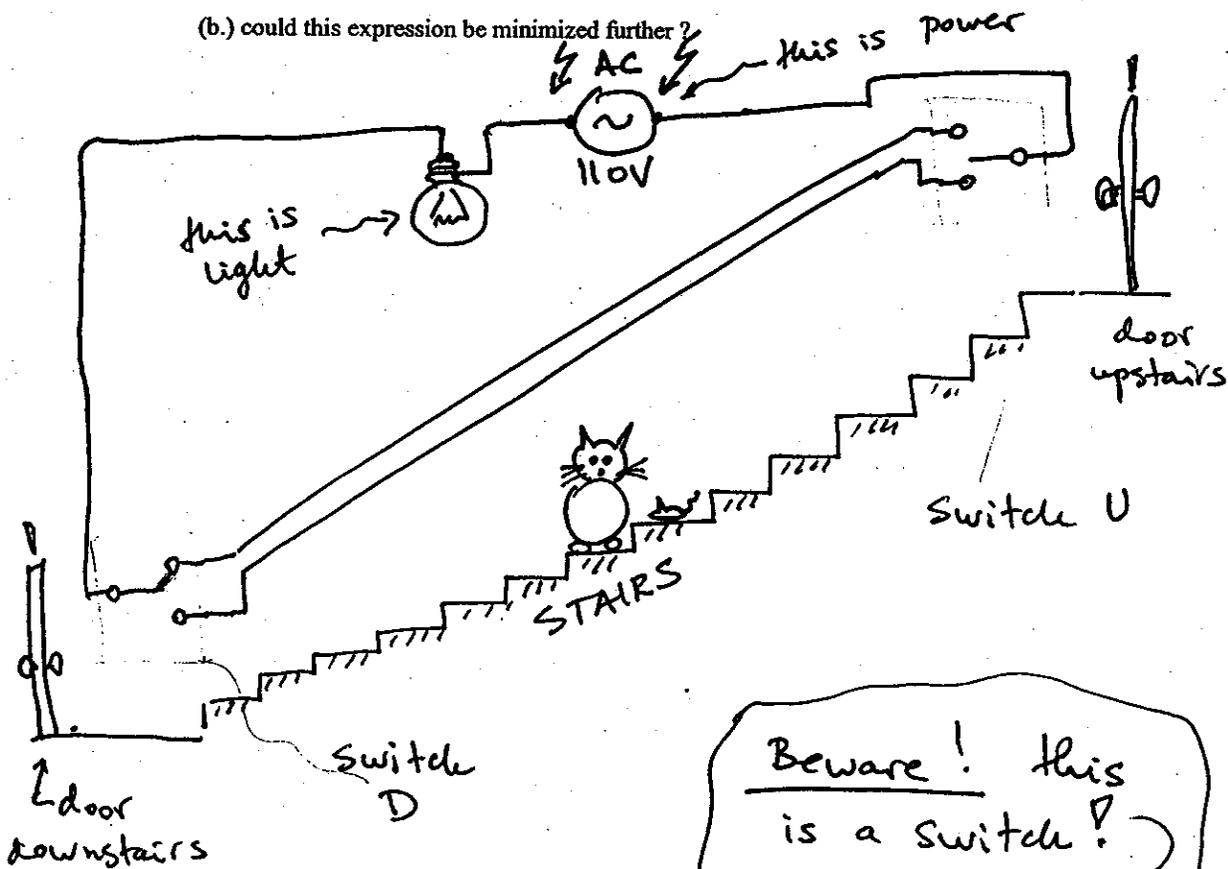(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

$$\bar{F} = \bar{D} + \bar{U}$$

$$F = \overline{\bar{D} + \bar{U}}$$

$$= \bar{\bar{D}} \cdot \bar{\bar{U}}$$

$$\bar{F} = \bar{D}U + D\bar{U}$$

$$F = \overline{\bar{D}U + D\bar{U}} = \overline{\bar{D}U} \cdot \overline{D\bar{U}}$$

$$F = (D + \bar{U}) (\bar{D} + U)$$


$$F = \bar{D}U + U\bar{D}$$

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).


If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain! $= f(u, d) = u + d$

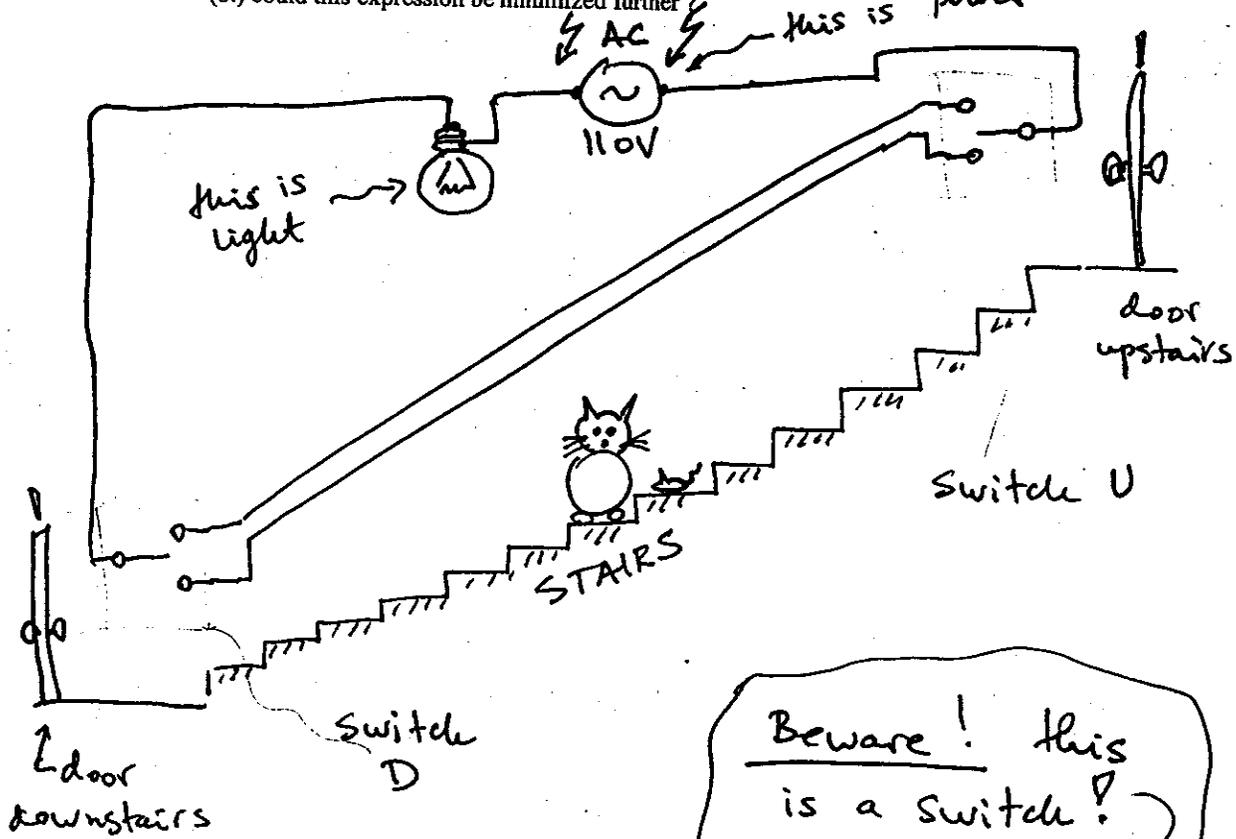(b.) could this expression be minimized further?



NO
 b) There's NO expression
 to be minimized
 further

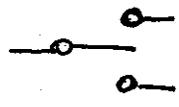
Beware! this
 is a switch!

 with two positions
Hint it can be only
 in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain! a) $L = f(U, D) = U + D \Rightarrow$ The light is on if either U is on OR D is on.

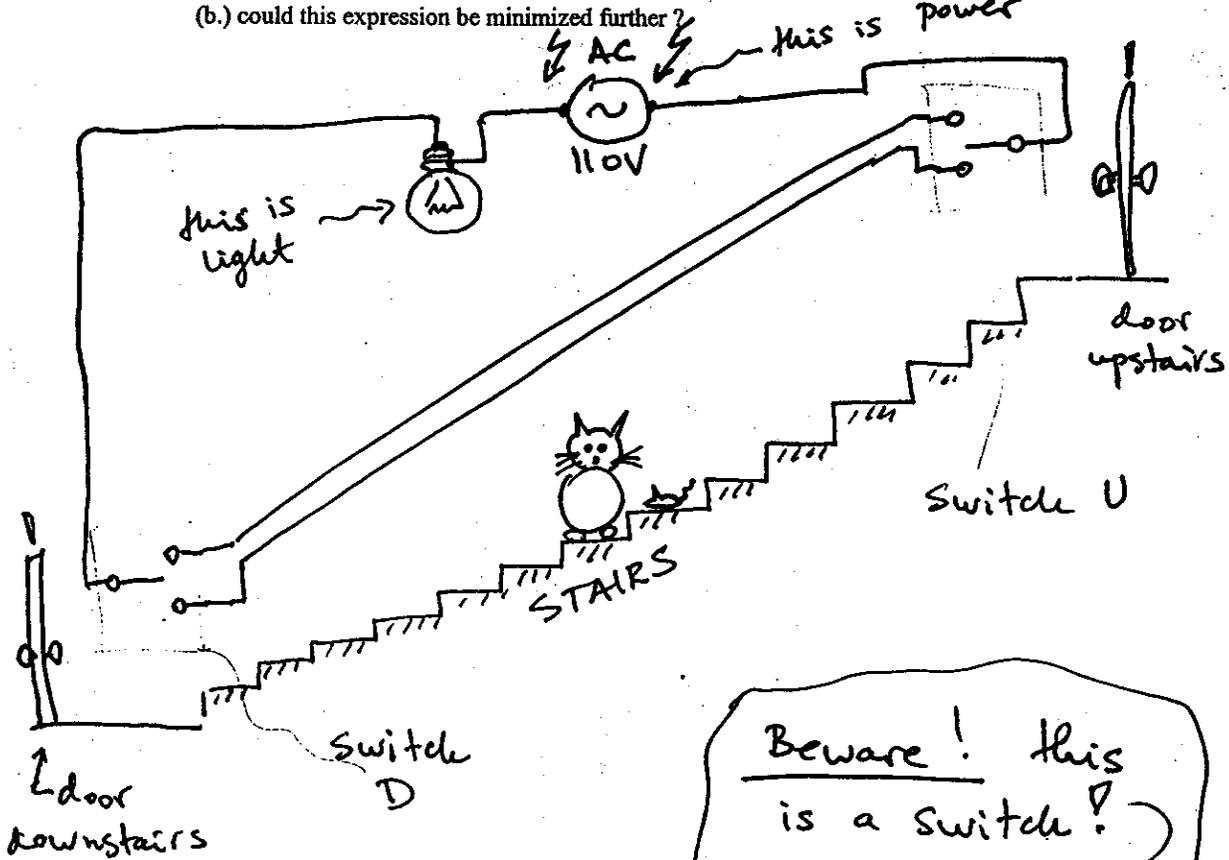(b.) could this expression be minimized further? ^{this is power}



b) No further simplification.

Beware! this is a switch!


with two positions
Hint it can be only in one position.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. - (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

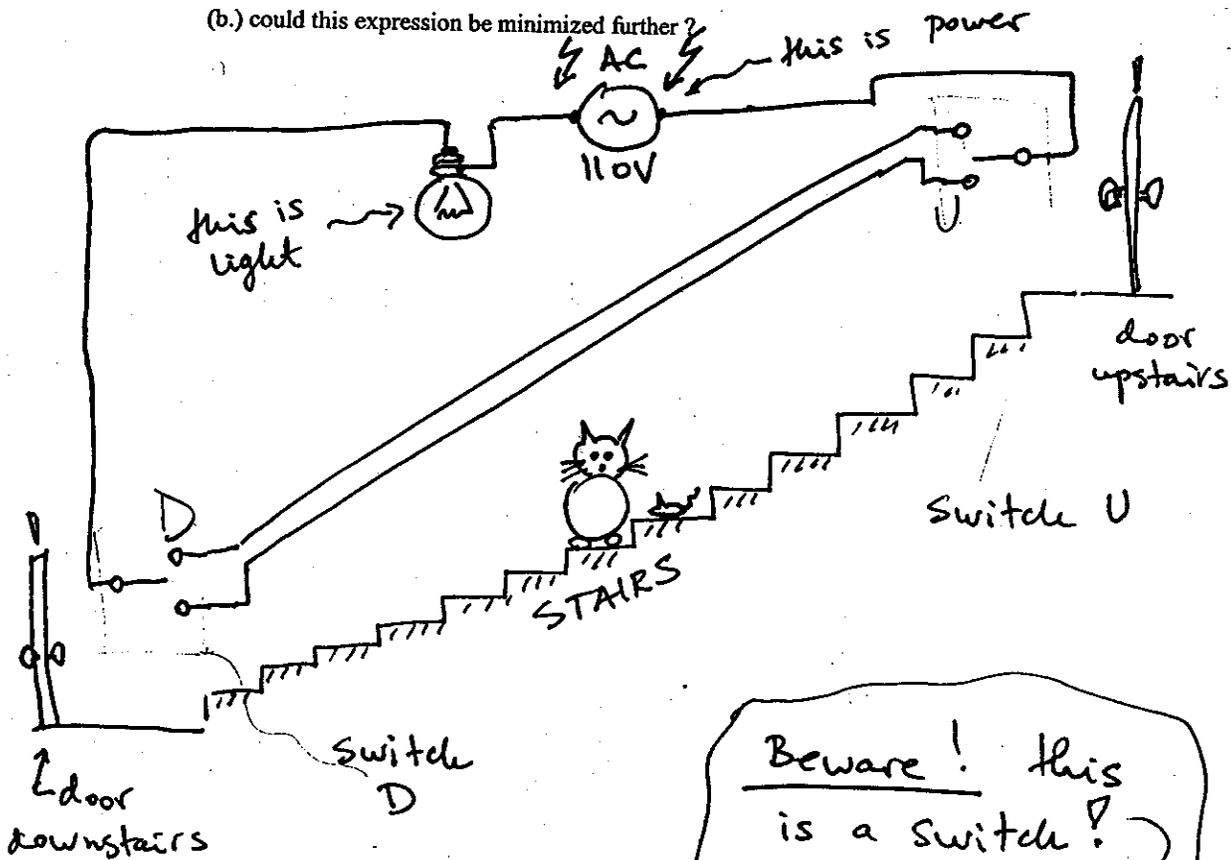(b.) could this expression be minimized further?



a) $L = \bar{D} + \bar{U}D$

one must be in the UP position while one is in the down position at all times to complete the circuit.

Beware! this is a switch!

with two positions
Hint it can be only in one position.


b) No, it can't be

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?

D	U	(F=1 for on)
00		
01		
10		
11		

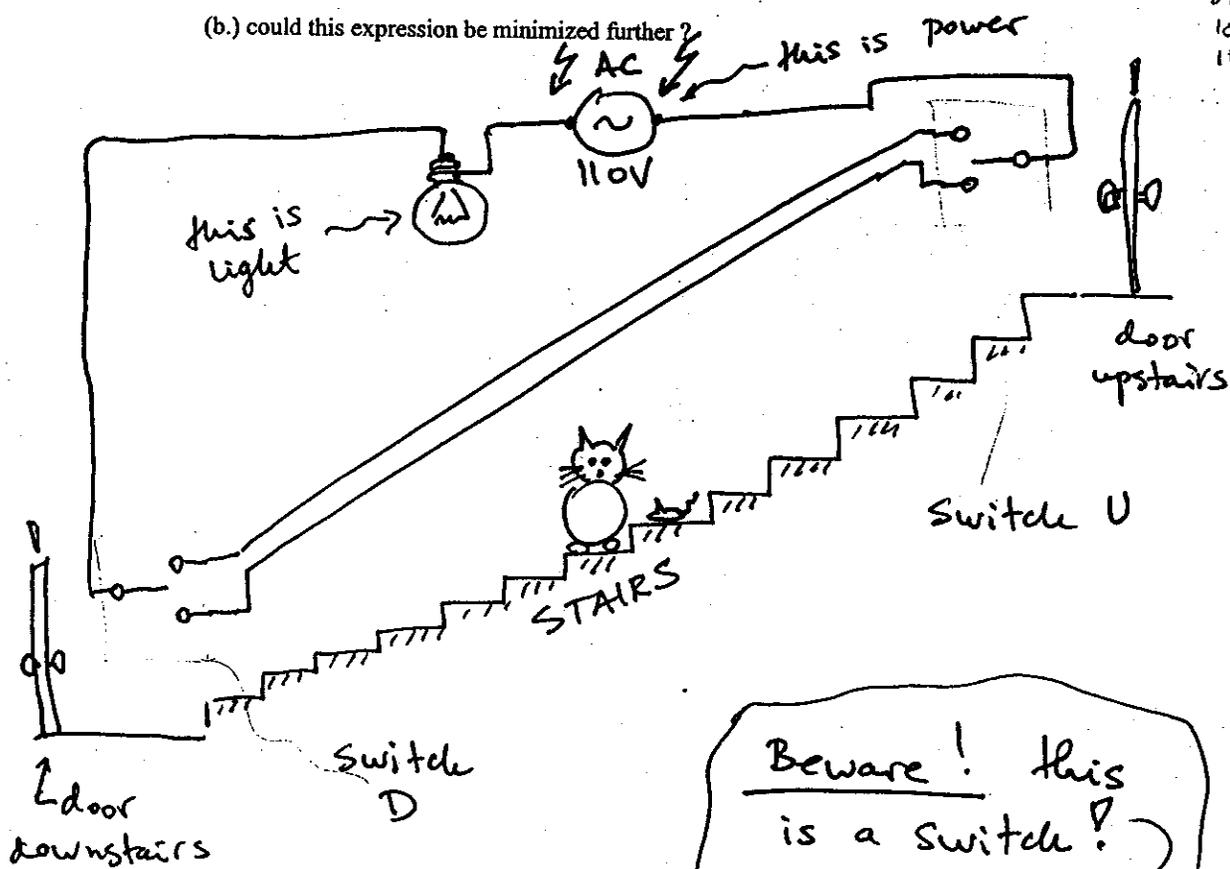

Beware! this is a switch!


with two positions
Hint it can be only in one position.

$$f = \bar{0}d + \bar{1}u + u\bar{d} +$$

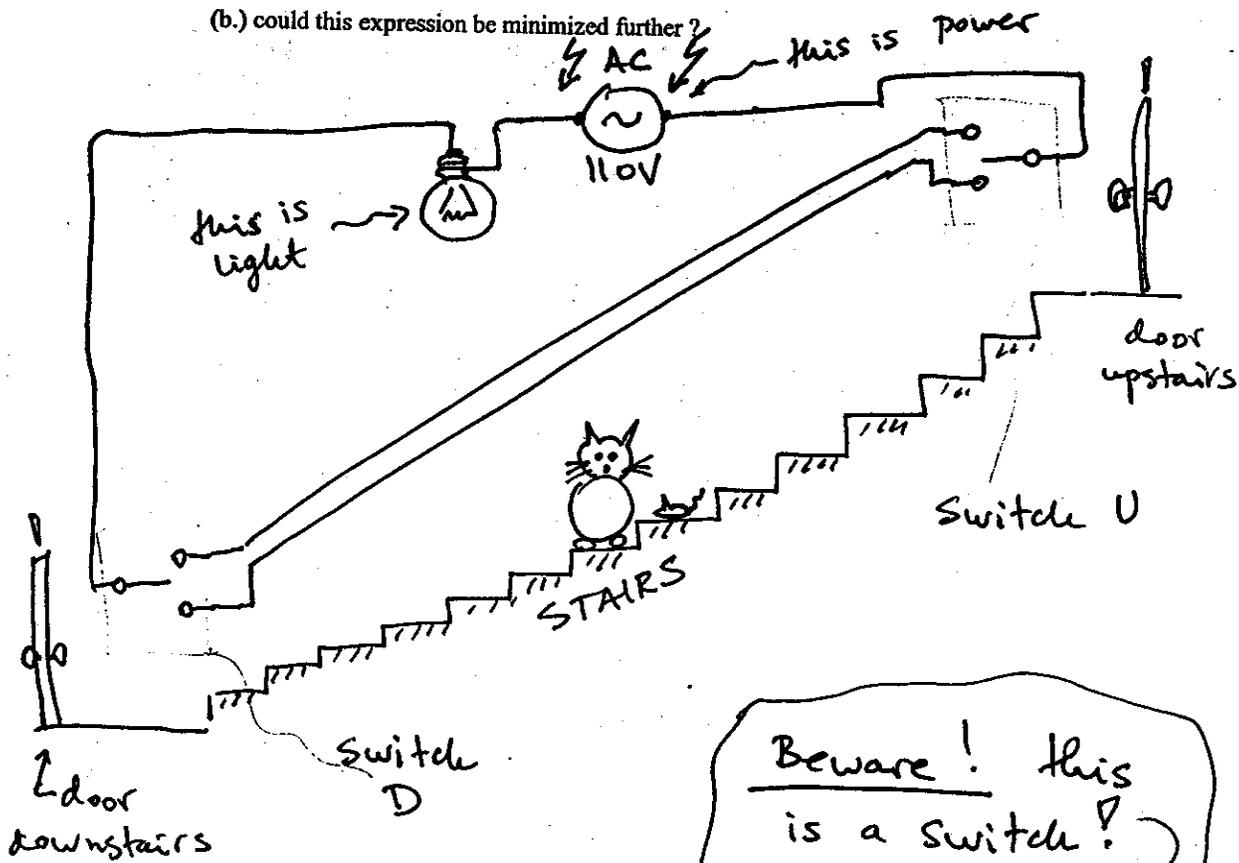Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs). If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.


Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain! $F = UD + \bar{U}\bar{D}$

(b.) could this expression be minimized further?

no

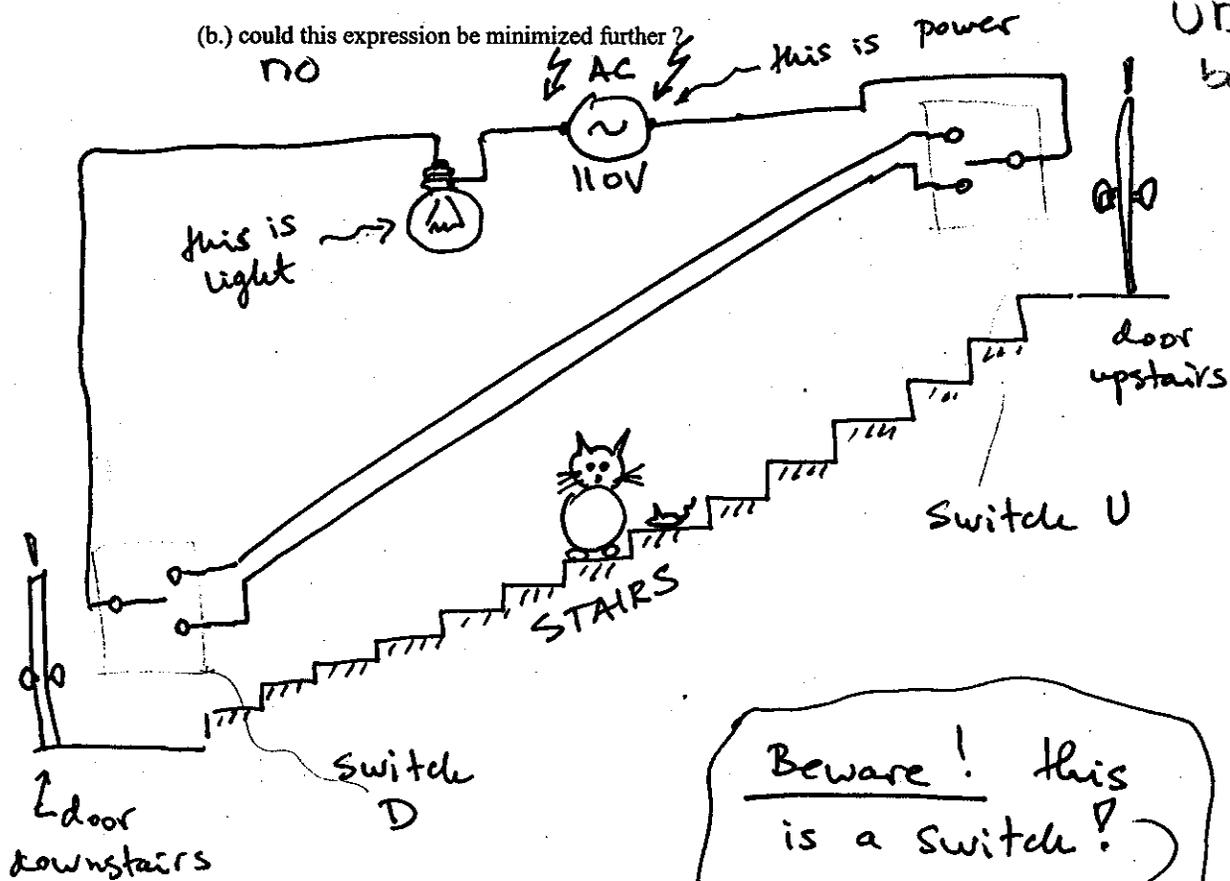UD means both on
 $\bar{U}\bar{D}$ means both off




Beware! this is a switch!

with two positions
Hint it can be only in one position.

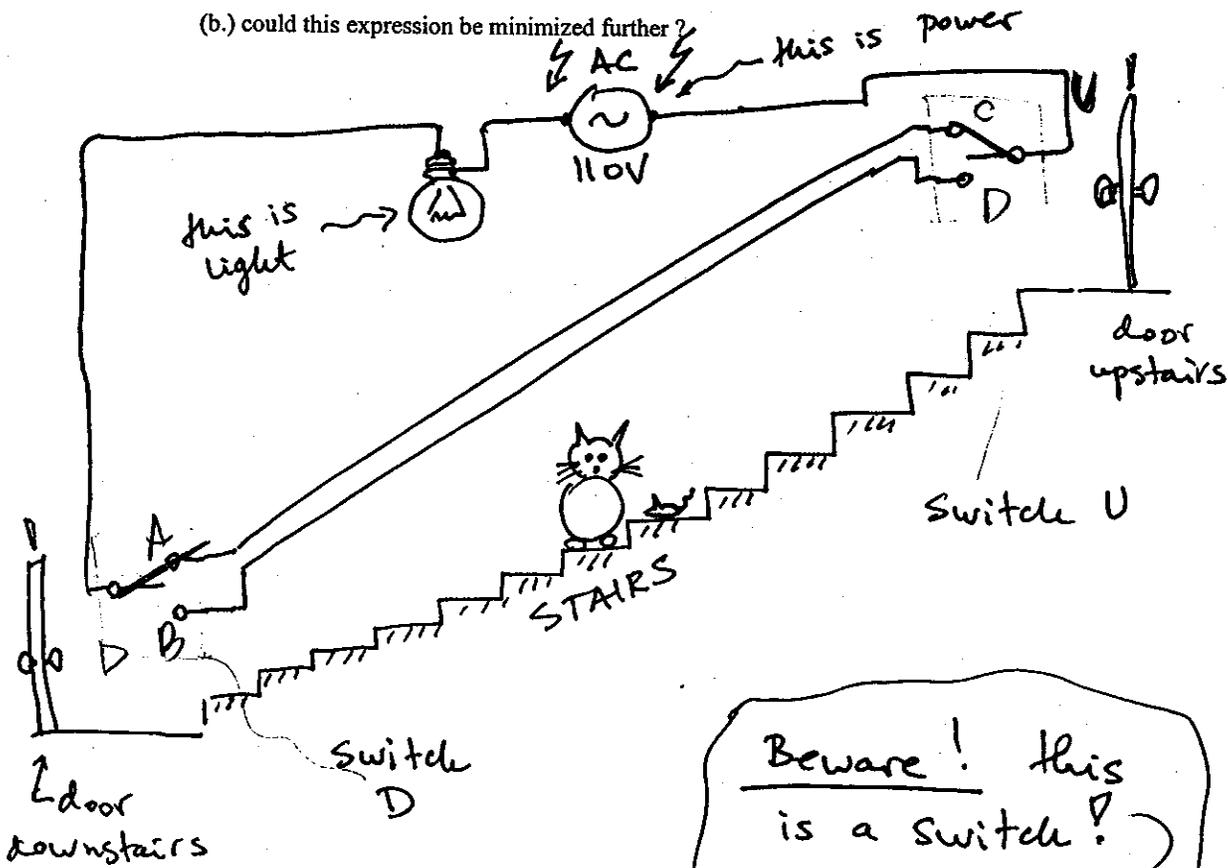Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

A) $F(a,b,c,d) = (AC) + (BD)$



b) cannot be minimized

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

D	U	L
0	0	0
0	1	0
1	0	0
1	1	1

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

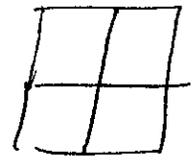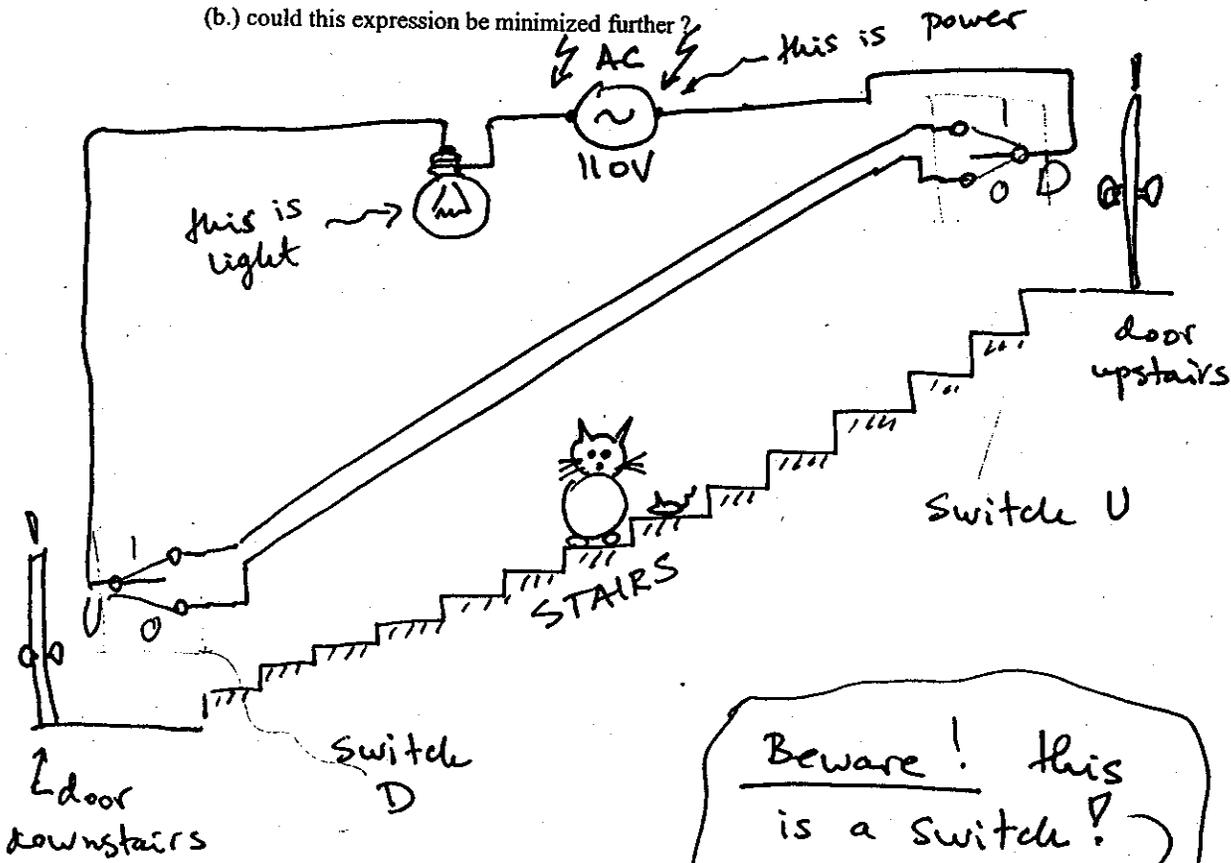(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

light on if U and D is on
 light off iff U or D off

$U_{on} = 1$
 $U_{off} = 0$
 $D_{on} = 1$
 $D_{off} = 0$

$\Rightarrow L = U \cdot D$

Truth table

D	U	L
0	0	0
0	1	0
1	0	0
1	1	1

b) It couldn't be minimize further

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?


(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?

$f(U,D) = UD' + U'D$

Yes this is an XOR
 AC 110V
 this is power
 ← 2 cases

U is on
 D is off
 U is off
 D is on

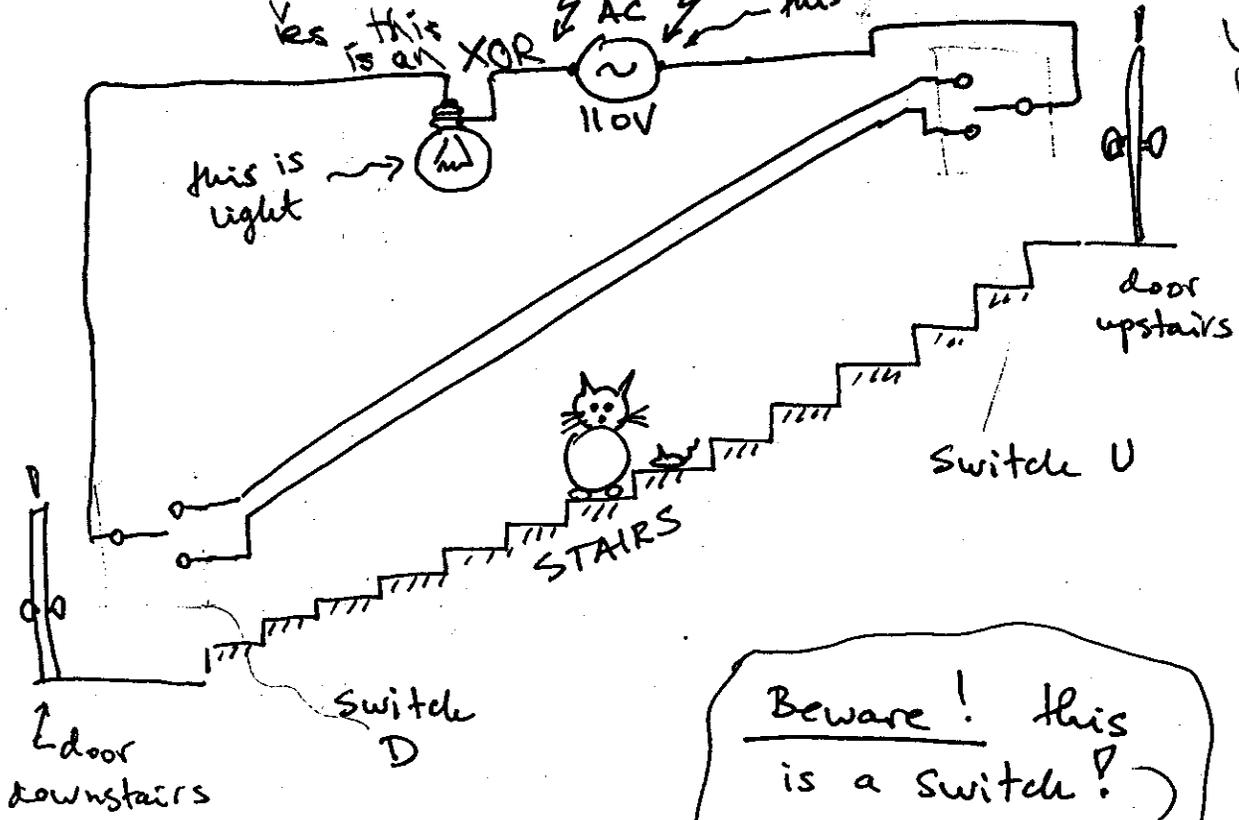


Beware! this is a switch!

with two positions
Hint it can be only in one position.

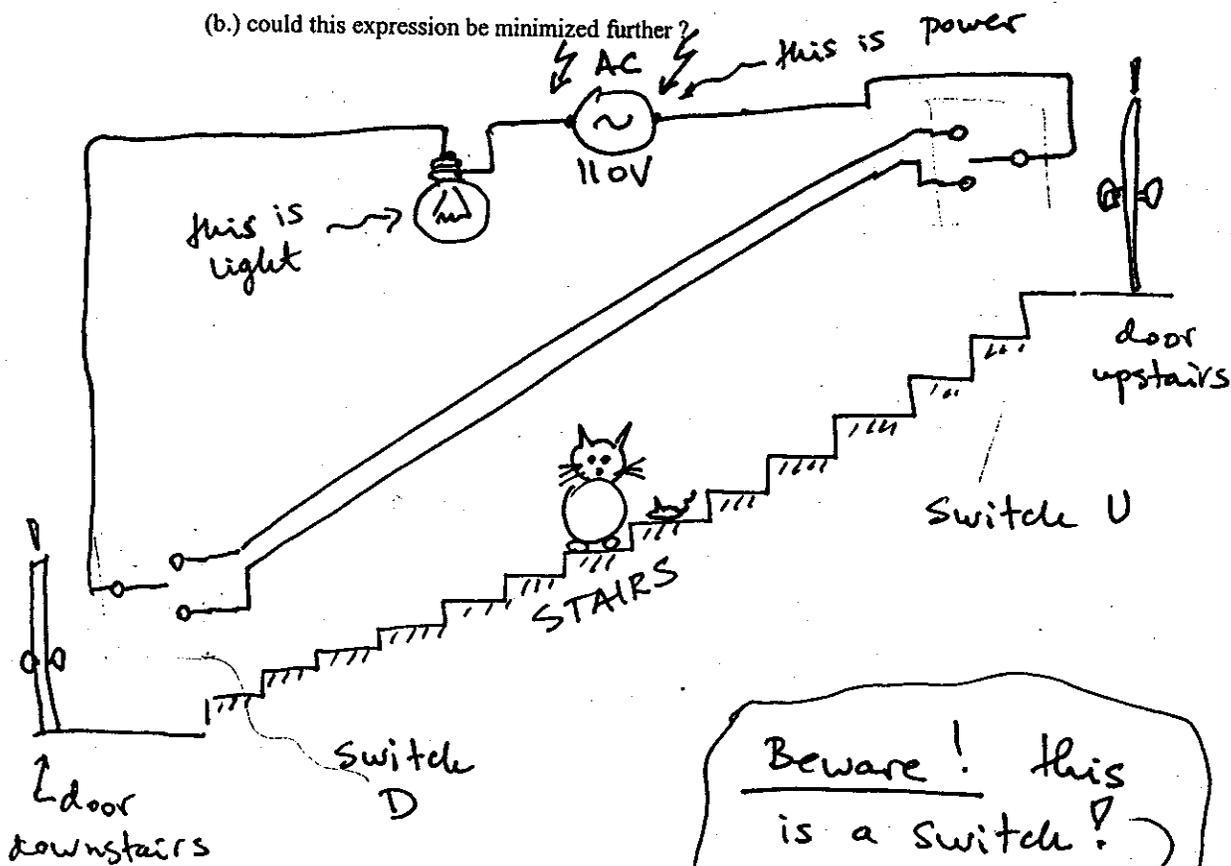Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!


with two positions
Hint it can be only in one position.

a) $L = f(U, D) = U\bar{D} + \bar{U}D + UD$

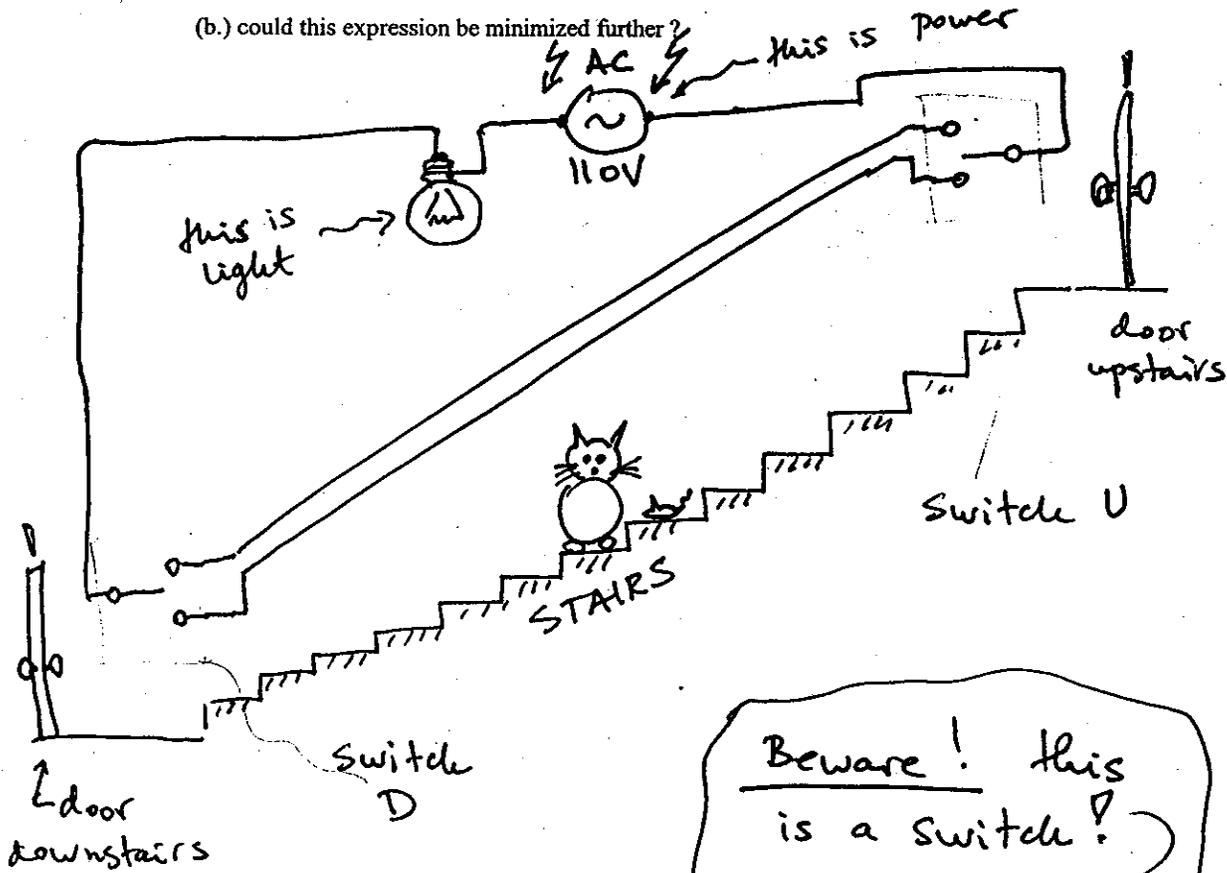Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

a) $L = f(U, D) =$


U	D	F
0	0	0
0	1	0
1	0	0
1	1	1

b) yes.

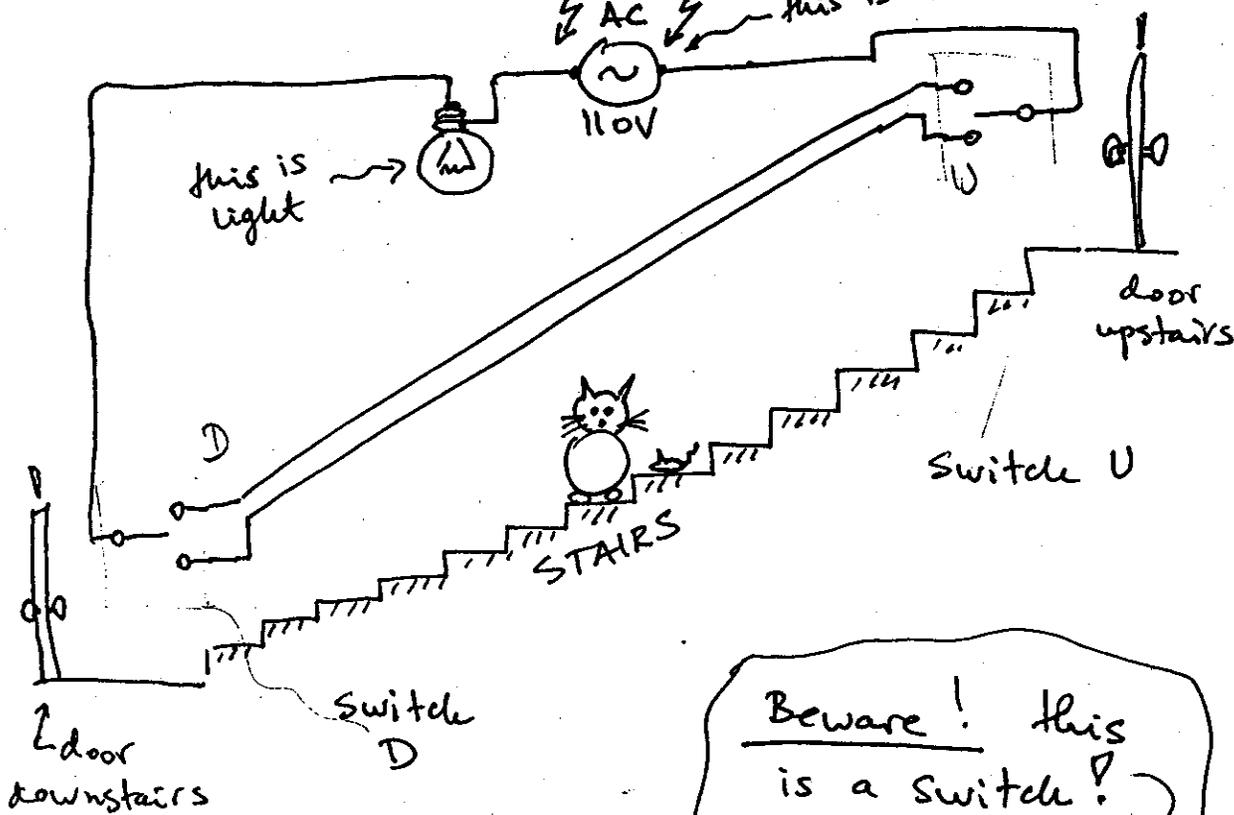Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain! $L = f(U,D) = U \cdot D$

(b.) could this expression be minimized further? NO! this is power




Beware! this is a switch!


with two positions
Hint it can be only in one position.

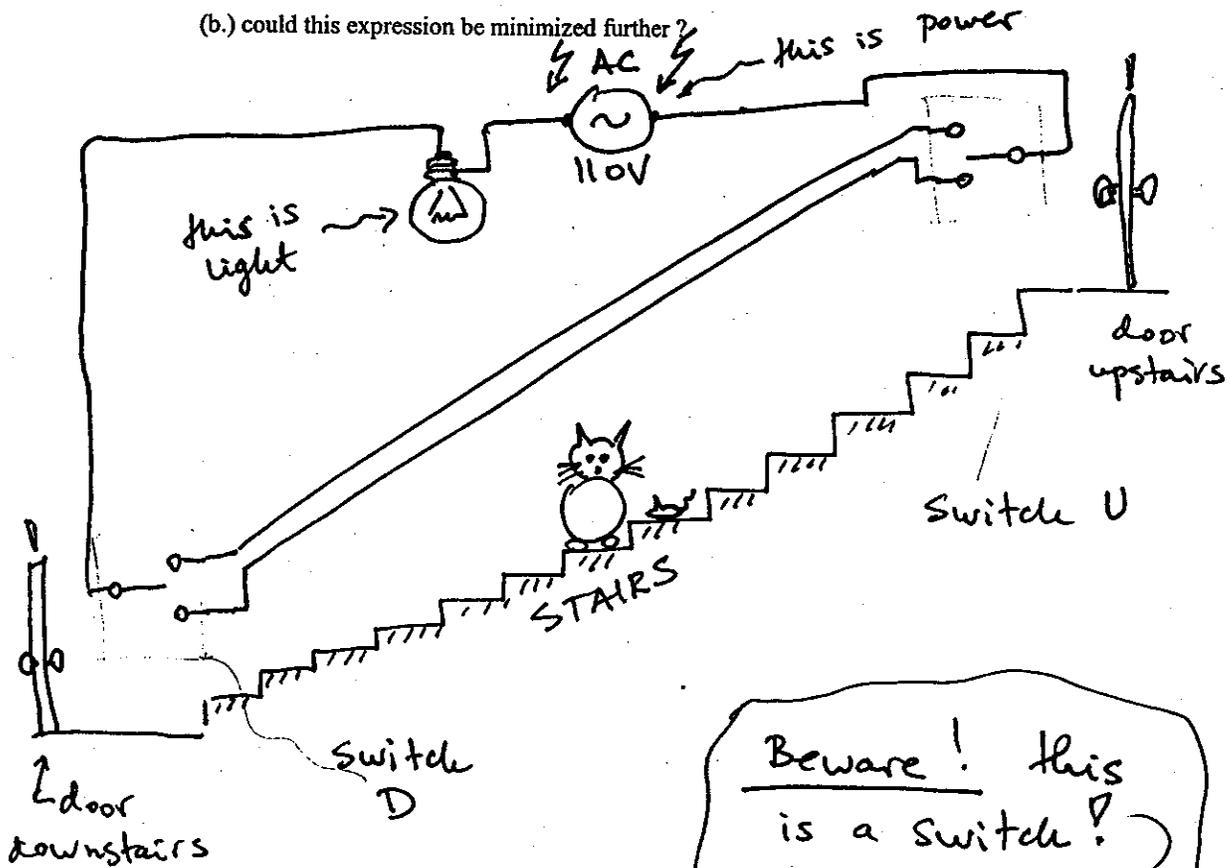Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



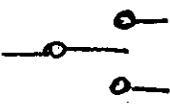Beware! this is a switch!

 with two positions
Hint it can be only in one position.

a.)

U	D	f
0	0	0 1
1	0	0
0	1	0
1	1	1

$$f(U,D) = \overline{(UD' + UD)} = (U'+D)(U+D')$$

b.) $f(U,D) = (U \oplus D)$ (exclusive or) complemented
 when both are in the same position (0 or 1) the light is on.

Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?


0 - OFF
 1 - ON

(a) i.e. $L=f(U,D)$. Write this expression and explain!

$L = U + D$ If $D=0$ (OFF) and $U=1$ (ON) then $L=1$ (ON).

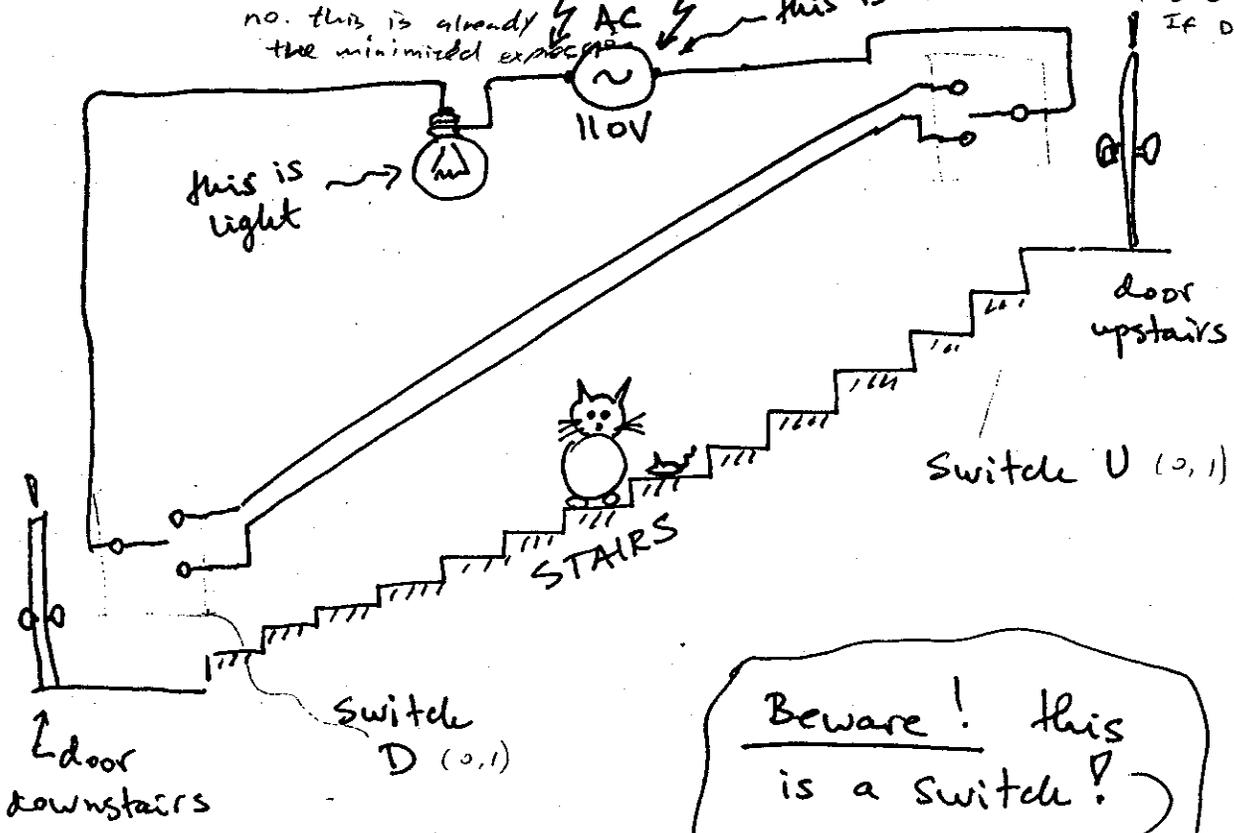(b) could this expression be minimized further?

no. this is already the minimized expression. AC this is power. If $D=1$ and $U=0$ then $L=1$. If $D=0$ and $U=0$ then $L=0$. If $D=1$ and $U=1$ then $L=1$.



Beware! this is a switch!


with two positions

Hint it can be only in one position.

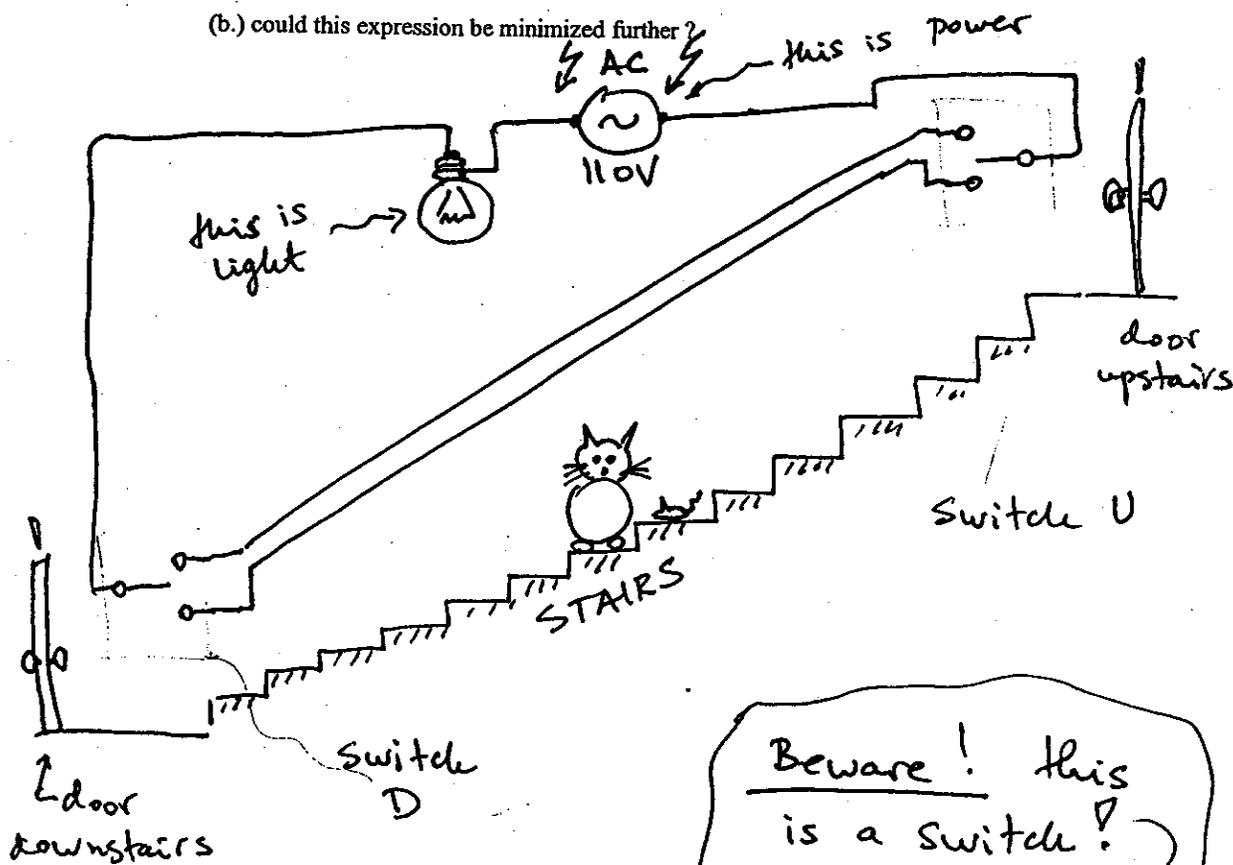Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

a)


Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).

If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

$L = \overline{D}U \oplus D\overline{U}$ because

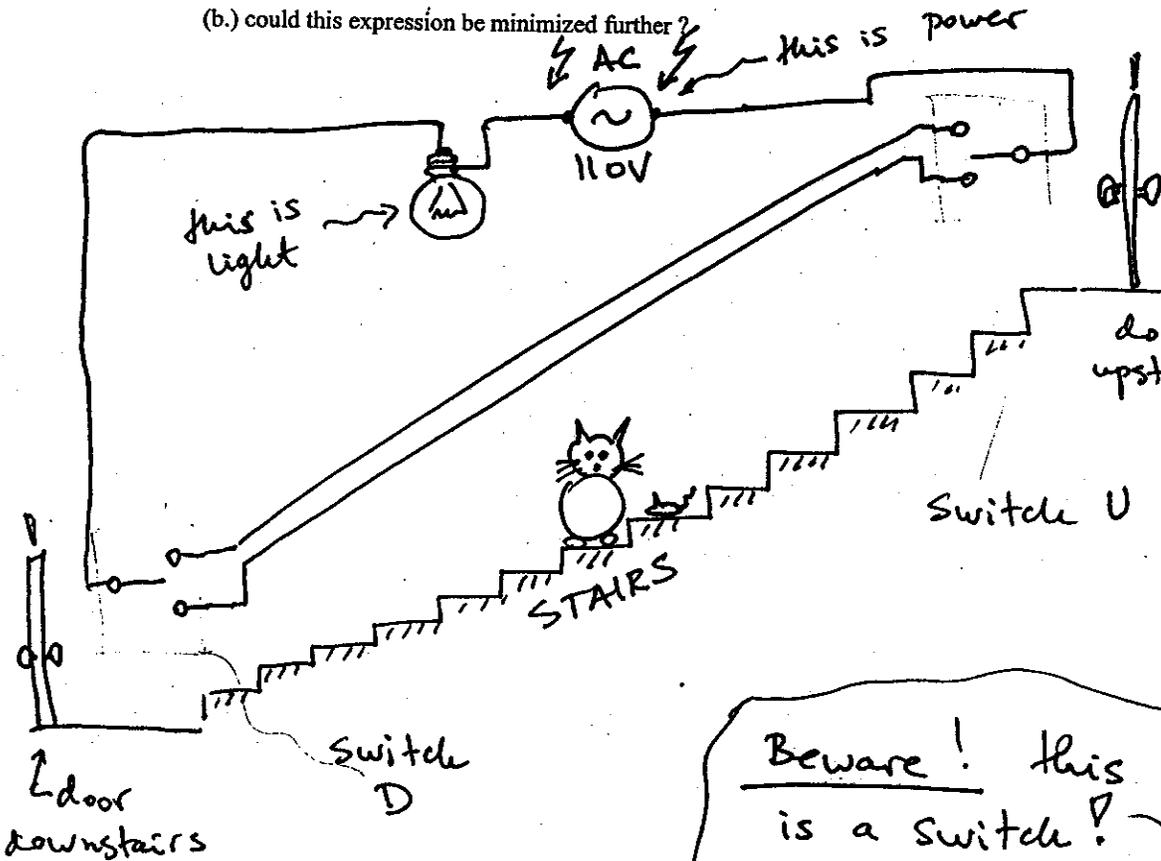(b.) could this expression be minimized further?



when you hit switch D, U will be off and vice versa but either one on (downstairs or upstairs), the light will be on. Either one switch off, the other will still be on, but the light off


Beware! this is a switch!

with two positions
Hint it can be only in one position.

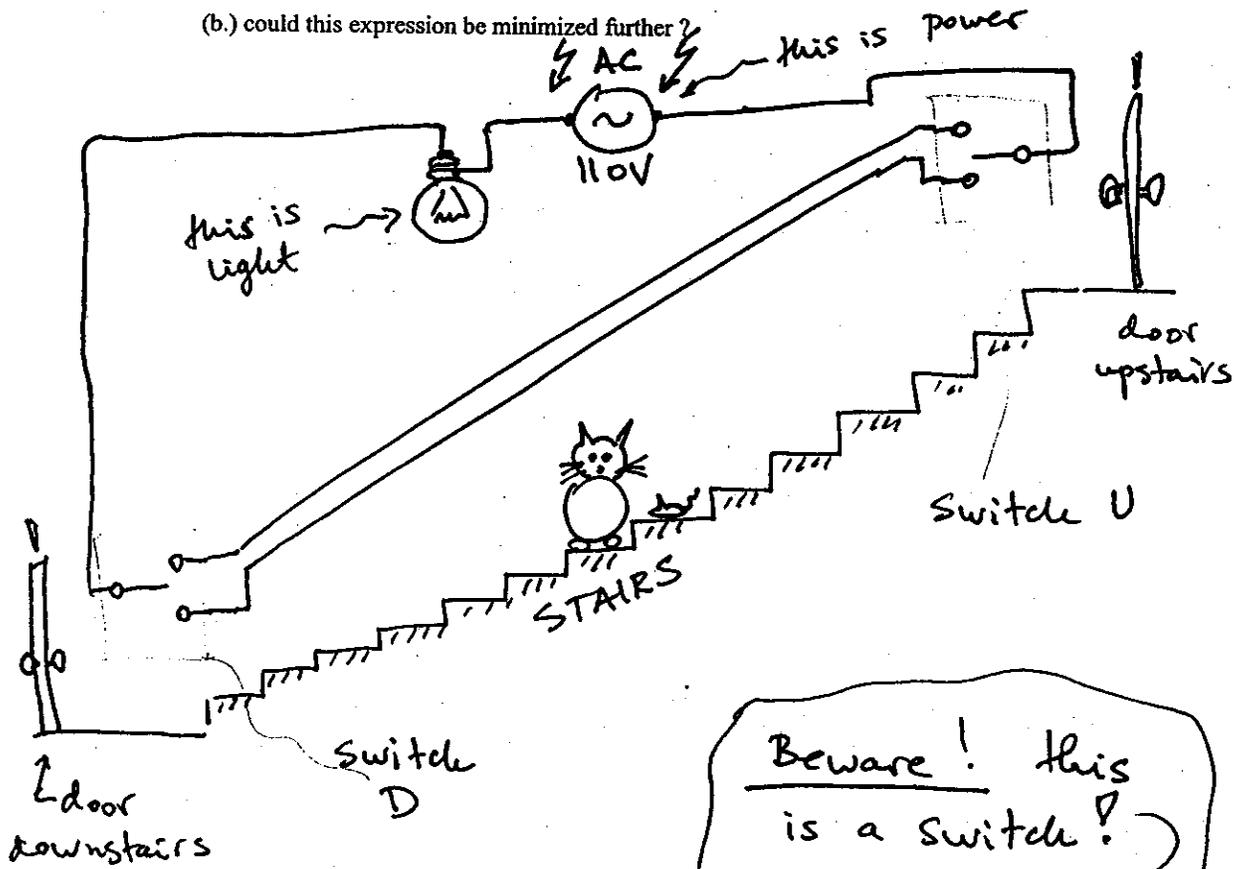Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs).
 If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



U	D	L
0	0	0
1	1	1

$L = UD$

Beware! this is a switch!


with two positions

Hint it can be only in one position.

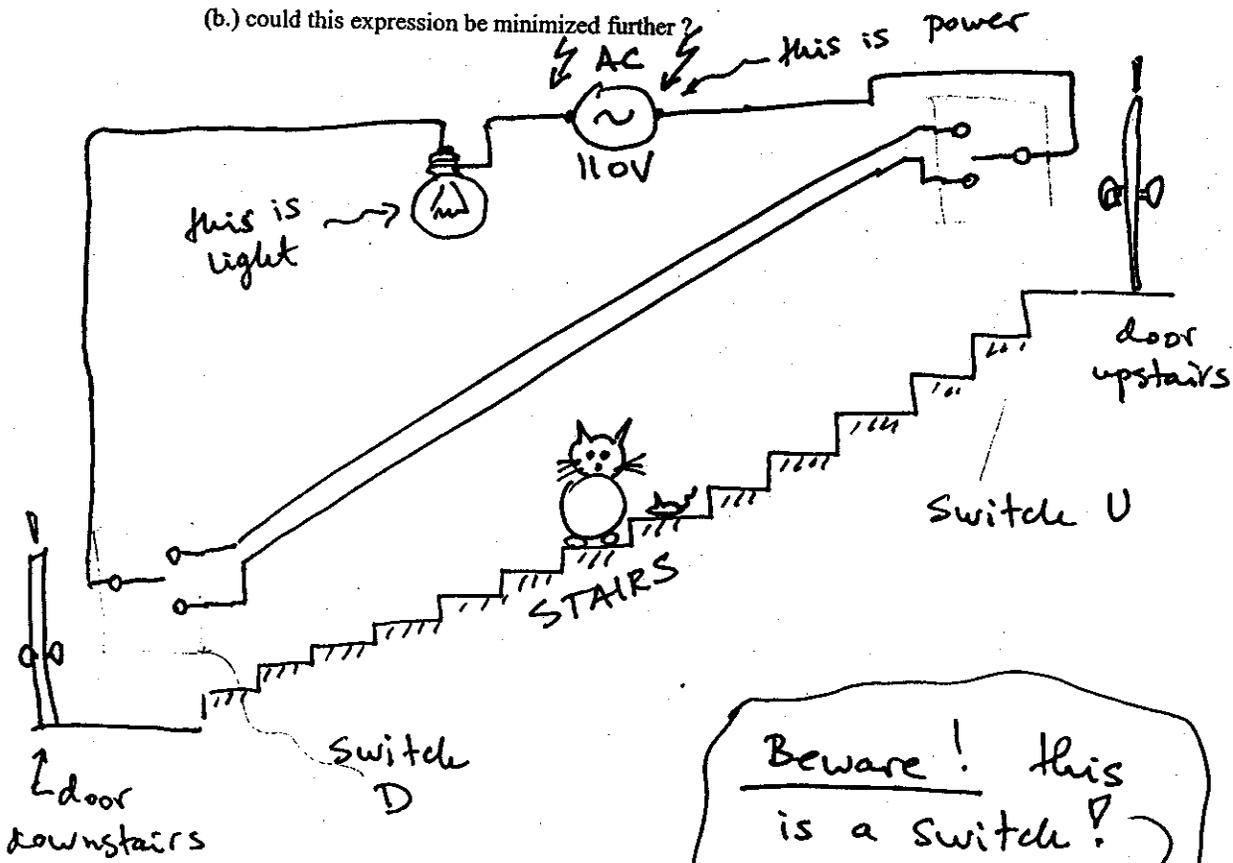Problem #2: Given is a famous staircase wiring diagram with the switch arrangement that can turn light OFF or ON on both sides of the stairs. (you do not need to go downstairs to turn the light OFF if you are exiting upstairs). If you designate the downstairs switch as D (which can have values 0, 1) and upstairs switch as U (0,1), what is the logic function (logic expression) for the light being ON?

(a.) I.e. $L=f(U,D)$. Write this expression and explain!

(b.) could this expression be minimized further?



Beware! this is a switch!

with two positions
Hint it can be only in one position.

$$L = f(U, D) = (UD' + DU')$$

$\underbrace{\quad}_U \quad \underbrace{\quad}_D$

\Downarrow
 since U can be on when D is off &
 D is on when U is off;

b.) $UD' + DU' \Rightarrow$ NO, can't be minimize further.