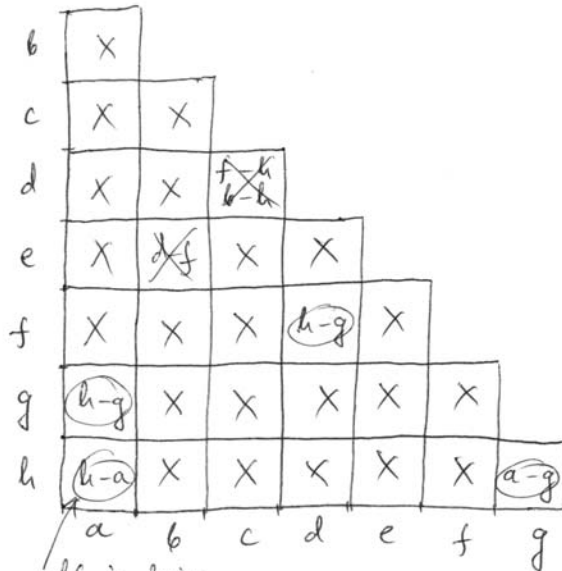


PROBLEM No.1 (15 points)

Reduce the following state table to a minimum number of states:

Present State S_n	Next State		Output Z	
	S_{n+1}		X=0	X=1
	X=0	X=1		
a	h	c	1	0
b	c	d	0	1
c	h	b	0	0
d	f	h	0	0
e	c	f	0	1
f	f	g	0	0
g	g	c	1	0
h	a	c	1	0

- [10] Write the resulting state table. Determine the equivalent states - show them !
- [3] Draw the resulting state diagram with all states, transitions and outputs !
- [2] Mark the transitions that are producing $Z=1$ as an output on the state diagram (circle them !)



equivalent states:

$$\begin{aligned}
 a &\equiv g \equiv h \\
 d &\equiv f \\
 e &\equiv b
 \end{aligned}$$


self-implying
Prof. V. G. Oklobdzija

(extra space for Problem 1)

new table:

S _n	S _{n+1}		z	
	X=0	X=1	X=0	X=1
a	a	c	1	0
b	c	d	0	1
c	a	b	0	0
d	d	a	0	0


state diagram:

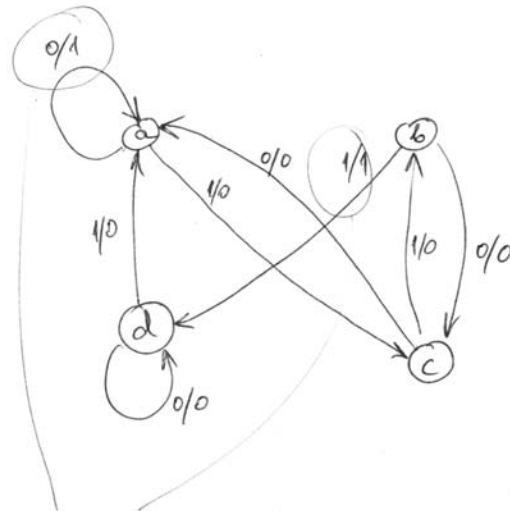


these transitions produce $z=1$

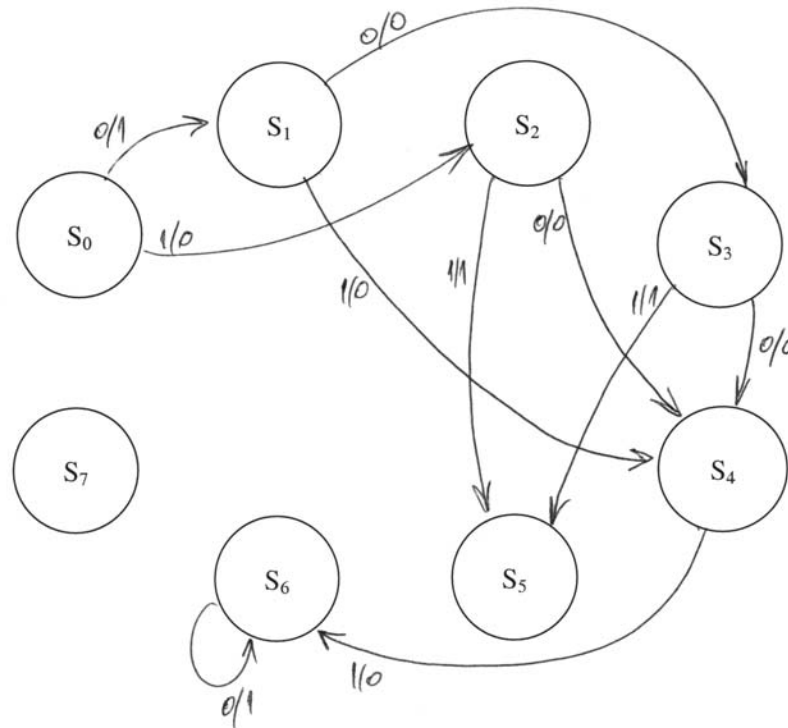Problem 2.

correction: There is also a transition from S5 to S0 for X/Z = 0/0 and 1/0. Also, there is a transition from S4 to S5 for X/Z = 0/1.



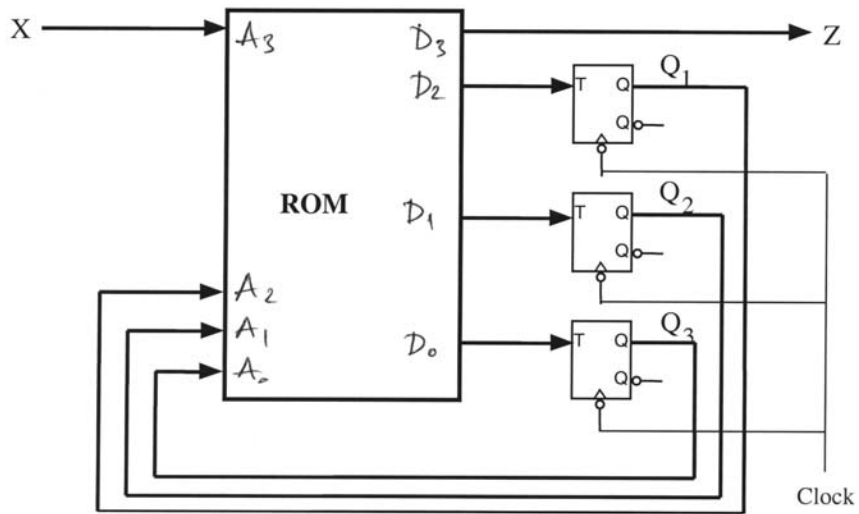- Mealy FSM
- problems :
 - S₆ - can't get out from S₆
 - S₇ - after power-up ⇒ undefined transition




D1

Address A3 A2 A1 A0	Content of ROM D3 D2 D1 D0	next state
0000	1 0 0 1	001
0001	0 0 1 0	011
0010	0 1 1 0	100
0011	0 1 1 1	100
0100	1 0 0 1	101
0101	0 1 0 1	000
0110	1 0 0 0	110
0111	X X X X	XXX
1000	0 0 1 0	010
1001	0 1 0 1	100
1010	1 1 1 1	101
1011	1 1 1 0	101
1100	0 0 1 0	110
1101	0 1 0 1	000
1110	X X X X	xxx
1111	X X X X	xxx

$X \ Q_1 \ Q_2 \ Q_3 \quad Z \ T_1 \ T_2 \ T_3 \quad Q_1^+ \ Q_2^+ \ Q_3^+$

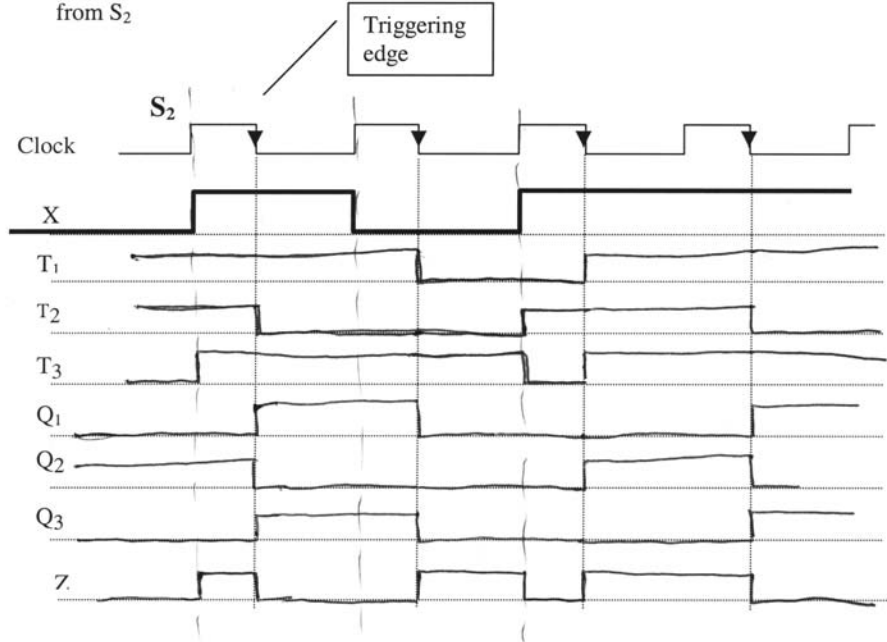c) [15] Draw a timing diagram for the change of the first four states starting from S_2



d) Suppose the ROM in part a) is to be replaced by a PLA:

- [6] Write **minimal form** equations for the inputs to the T flip-flops, called respectively T_1 , T_2 and T_3 ?
- [2] Write an equation for the output Z that can be realized as part of the PLA.

XQ_1		Q_2Q_3	00	01	11	10
	00		0	0	0	0
	01		0	1	1	1
	11		1	X	X	1
	10		1	0	X	1

$$\Rightarrow T_1 = \bar{Q}_1 Q_2 + Q_1 Q_3 + X Q_3$$

XQ_1		Q_2Q_3	00	01	11	10
	00		0	0	1	1
	01		1	0	0	0
	11		1	X	X	1
	10		1	0	X	1

$$T_2 = \bar{Q}_1 Q_2 + X \bar{Q}_3 + \bar{X} \bar{Q}_1 Q_3$$


XQ_1		Q_2Q_3	00	01	11	10
	00		1	1	0	0
	01		0	1	1	1
	11		1	X	X	0
	10		0	0	X	1

$$T_3 = Q_1 Q_3 + \bar{X} \bar{Q}_2 \bar{Q}_3 + X Q_2 \bar{Q}_3 + X \bar{Q}_2 Q_3 + \bar{X} Q_2 Q_3$$

XQ_1		Q_2Q_3	00	01	11	10
	00		1	1	0	0
	01		0	0	0	0
	11		0	X	X	1
	10		0	1	X	1

$$Z = Q_1 Q_2 + X Q_2 + \bar{X} \bar{Q}_2 \bar{Q}_3$$

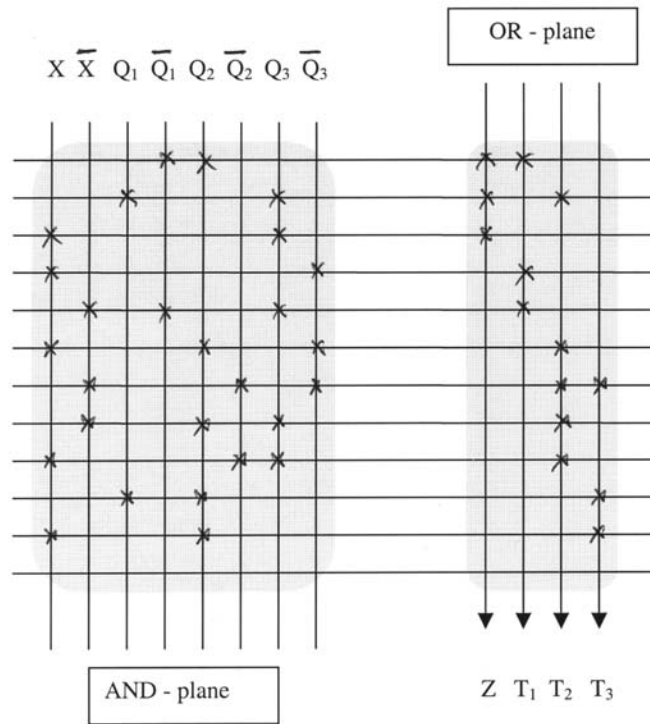
e) [3] Complete the "stick-diagram" PLA representation of the part d).



correction: In the last row of the table (for $G_i = A_i = B_i = 1$), G_{i+1} should be 1 instead of 0.

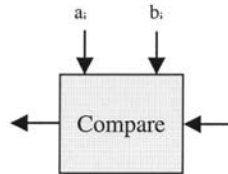
PROBLEM No. 3 (15 points)

Design an iterative network for comparing two unsigned binary numbers. These numbers are designated as: $a = a_n \dots a_0$, $b = b_n \dots b_0$. The comparator checks if $a > b$! A typical cell for the comparator is shown:



Note that there is a signal propagating between the cells. What is the function of that signal? How would you use it?

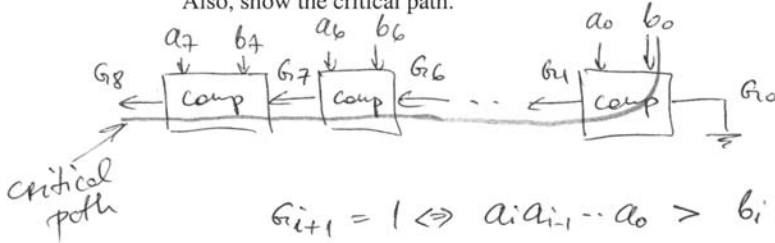(a.) [5] Draw a schematic of a comparator comparing two 8-bit words using these cells. Explain how it works and connect any signals that need to be connected. Also, show the critical path.




(b.) [10] Derive the logic inside this cell and write equations for this logic. Show the most efficient logic implementation for this comparator cell (a cell can be realized using one MUX and one logic gate).

G_i	A_i	B_i	G_{i+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$G_i A_i$	00	01	11	10
B_i 0	0	1	1	1
1	0	0	1	0

$\Rightarrow G_{i+1} = G_i A_i + G_i \bar{B}_i + A_i \bar{B}_i$

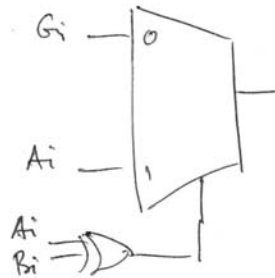

Problem 4.

(extra space for Problem 4)

A B C	$J_A K_A$	$J_B K_B$	$J_C K_C$	$A^+ B^+ C^+$
0 0 0	1 0	1 0	1 1	1 1 1
0 0 1	0 1	0 1	1 1	0 0 0
0 1 0	1 1	1 0	0 0	1 1 0
0 1 1	0 0	0 1	0 0	0 0 1
1 0 0	1 0	1 0	1 0	1 1 1
1 0 1	0 1	1 1	1 0	0 1 1
1 1 0	1 1	1 0	1 0	0 1 1
1 1 1	0 0	1 1	1 0	1 0 1

AB

C	00	01	11	10
0	1	1	0	1
1	0	0	1	0

$$A^+ = \bar{A}\bar{C} + \bar{B}\bar{C} + ABC$$

AB


C	00	01	11	10
0	1	1	1	1
1	0	0	0	1

$$B^+ = \bar{C} + AB$$

AB

C	00	01	11	10
0	1	0	1	1
1	0	1	1	1

$$C^+ = A + \bar{B}\bar{C} + BC$$

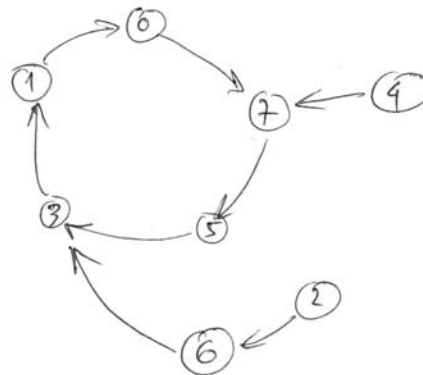

→ self-starting