

Problem 1 (20 points)

Using algebraic manipulations (without using Karnaugh maps) prove that:

$$\begin{aligned}
 F &= (\overline{A+B+D})(\overline{A+B+D})(B+C+D)(A+\overline{C})(A+\overline{C}+D) = \overline{A}\overline{C}D + A\overline{C}\overline{D} + B\overline{C}\overline{D} \\
 &= (\overline{A} + \overline{D})(B+C+D)(A+\overline{C}) = \\
 &= (\overline{A} + \overline{D})(A + \overline{C})(B+C+D) = \\
 &= (\overline{A}\overline{C} + A\overline{D} + \overline{D}\overline{C})(B+C+D) = \\
 &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{C}D + \overline{A}B\overline{D} + A\overline{C}\overline{D} + B\overline{C}\overline{D} = \\
 &= \overline{A}\overline{C}D + A\overline{C}\overline{D} + B\overline{C}\overline{D}
 \end{aligned}$$



Problem 2 (25 points)

Realize the given function $F = F(A,B,C,D)$:

		D			
		┌───┐		└───┘	
		1	1		1
		0	1	3	2
A	┌───┐	8	9	11	10
	└───┘			1	
	12	13	15	14	
	└───┘				
		1	1	1	
		4	5	7	6
		C			
		┌───┐		└───┘	

a) using one 8:1 MUX with control inputs A, C and D

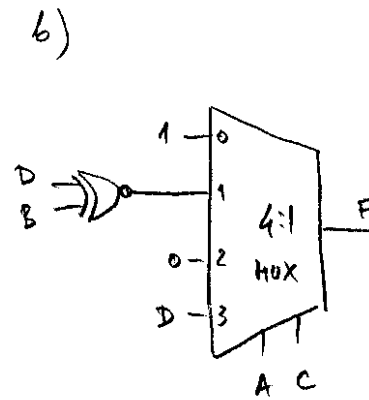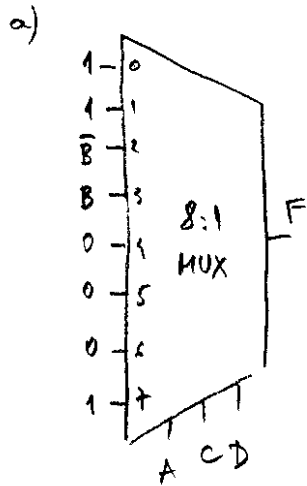b) using one 4:1 MUX. Select the control inputs to minimize the number of added gates.




Problem 3 (30 points)

Show that:

$$F = ABD + BCD + ABC + ABD \text{ reduces to } F = BCD + AD + ABC$$

You can use **Karnaugh map** (if you wish) – however you are allowed to use only **product of sums** (i.e. you can only minimize them using zeros).

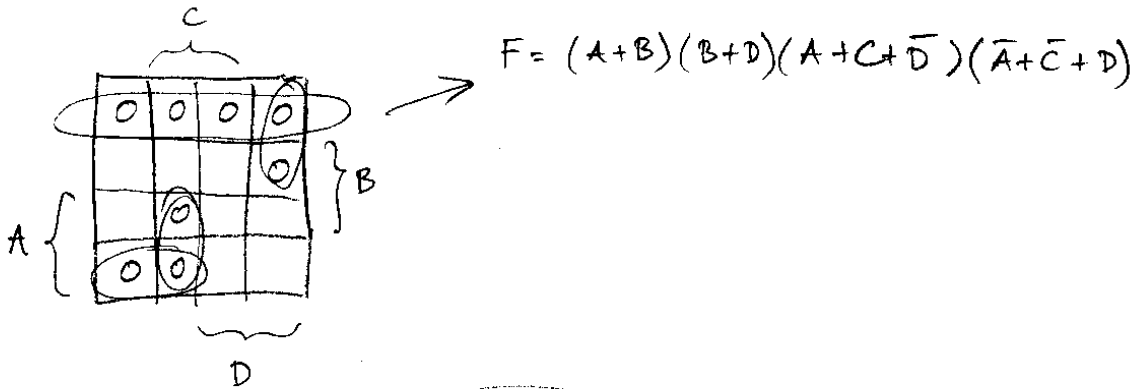List the **essential prime implicants** for this expression.



$$F = (A+B)(B+D)(A+C+\bar{D})(\bar{A}+\bar{C}+D)$$

$$\begin{aligned} F &= (AD+B)(\bar{A}\bar{C} + \bar{A}\bar{D} + A\bar{C} + \bar{C}\bar{D} + AD + CD) = \\ &= (AD+B)(\bar{A}(C+D) + A(\bar{C}+D)) = \\ &= \bar{A}B(C+\bar{D}) + AD(\bar{C}+D) + AB(\bar{C}+D) = \\ &= \bar{A}BC + \bar{A}B\bar{D} + AD + \cancel{ABD} + \underline{AB\bar{C}} \\ &= \bar{A}BC + AD + B\bar{C}\bar{D} \end{aligned}$$

EPI : AD