

Solutions for Homework # 4

8.A	ABCD	X_1	X_2	X_3	X_4	X_5	X_6	X_7
	0000	1	1	1	1	1	1	0
	0001	0	1	1	0	0	0	0
	0010	1	1	0	1	1	0	1
	0011	1	1	1	1	0	0	1
	0100	0	1	1	0	0	1	1
	0101	1	0	1	1	0	1	1
	0110	0	0	1	1	1	1	1
	0111	1	1	1	0	0	0	0
	1000	1	1	1	1	1	1	1
	1001	1	1	1	0	0	1	1

$$X_1 = B'D' + BD + A + CD = \underline{B'D'} + \underline{BC'D} + A + \underline{CD} \text{ (used in circuit)}$$

$$X_2 = B'D' + BD + A + B'C$$

$$X_2 = B' + \underline{CD'} + \underline{CD}$$

$$X_3 = C' + D + B$$

$$X_4 = \underline{B'D'} + \underline{B'C} + \underline{BC'D} + \underline{CD'}$$

$$X_5 = \underline{B'D'} + \underline{CD'}$$

$$X_6 = \underline{CD'} + \underline{BC'} + BD' + A$$

$$X_7 = \underline{B'C} + \underline{BC'} + A + \underline{CD'} \text{ (used in circuit)}$$

$$X_7 = B'C + BC' + A + BD'$$

This solution uses 15 gates and 41 gate inputs.

Students are allowed to use a maximum of 18 gates.

8.A, continued

X_1

		A B		
C D	00	01	11	10
00	1		X	1
01		1	X	1
11	1	1	X	X
10	1		X	X

$$X_1 = B'D' + BC'D + A + CD$$

X_2

		A B		
C D	00	01	11	10
00	1	1	X	1
01	1		X	1
11	1	1	X	X
10	1		X	X

$$X_2 = B' + CD' + CD$$

X_3

		A B		
C D	00	01	11	10
00	1	1	X	1
01	1	1	X	1
11	1	1	X	X
10		1	X	X

$$X_3 = C' + D + B$$

X_4

		A B		
C D	00	01	11	10
00	1		X	1
01		1	X	
11	1		X	X
10	1	1	X	X

$$X_4 = B'D' + B'C + BC'D + CD'$$

X_5

		A B		
C D	00	01	11	10
00	1		X	1
01			X	
11			X	X
10	1	1	X	X

$$X_5 = B'D' + CD'$$

X_6


		A B		
C D	00	01	11	10
00	1	1	X	1
01		1	X	1
11			X	X
10		1	X	X

$$X_6 = CD' + BC' + BD' + A$$

X_7

		A B		
C D	00	01	11	10
00		1	X	1
01		1	X	1
11	1		X	X
10	1	1	X	X

$$X_7 = B'C + BC' + A + BD'$$

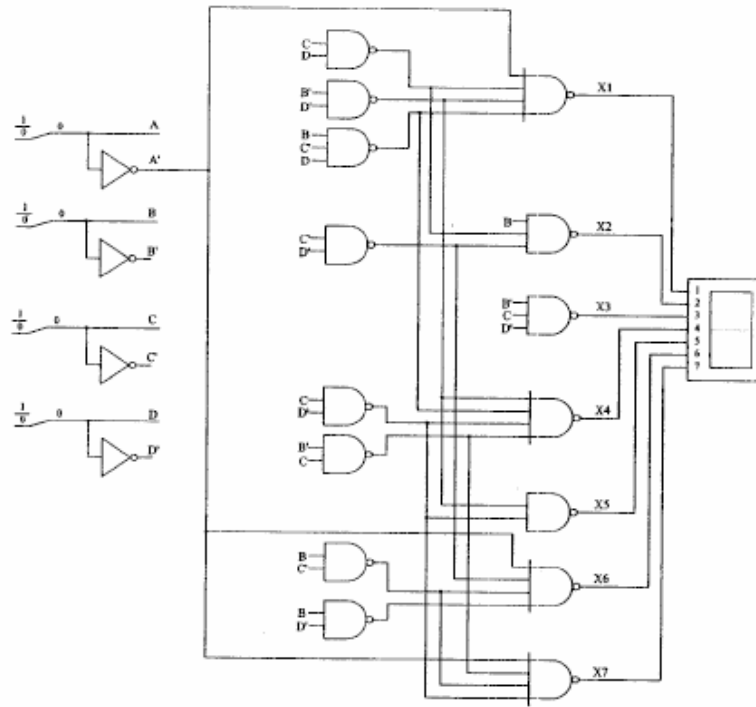

8.B

ABCD	X_1	X_2	X_3	X_4	X_5	X_6	X_7
0000	X	X	X	X	X	X	X
0001	X	X	X	X	X	X	X
0010	X	X	X	X	X	X	X
0011	1	1	1	1	1	1	0
0100	0	1	1	0	0	0	0
0101	1	1	0	1	1	0	1
0110	1	1	1	1	0	0	1
0111	0	1	1	0	0	1	1
1000	1	0	1	1	0	1	1
1001	1	0	1	1	1	1	1
1010	1	1	1	0	0	0	0
1011	1	1	1	1	1	1	1
1100	1	1	1	1	0	1	1

$$X_1 = B' + \underline{C'D} + C D' + A$$

$$X_2 = C + B$$

$$X_3 = D' + C + A \text{ (used in circuit)}$$

$$X_3 = D' + C + B'$$

$$X_4 = \underline{C'D} + \underline{B'D} + B C D' + \underline{A C'} \text{ (used in circuit)}$$

$$X_4 = C'D + A' C D' + B' D + A C'$$

$$X_5 = \underline{C'D} + \underline{B'D}$$


$$X_6 = C D + \underline{A C'}$$

$$X_7 = A D + B C + \underline{C'D} + \underline{A C'} \text{ (used in circuit)}$$

$$X_7 = A D + B C + A C' + B D$$

This solution uses 15 gates and 38 gate inputs.

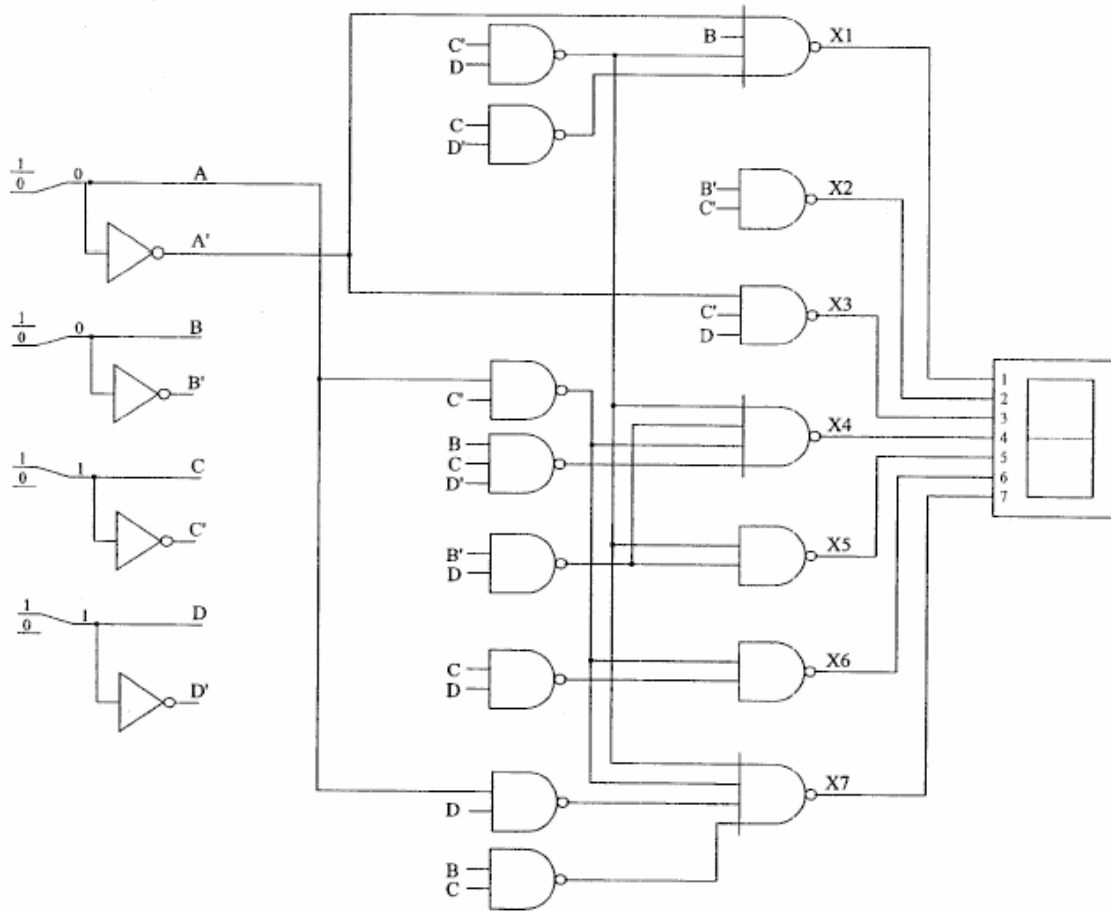Students are allowed to use a maximum of 16 gates.



8.0

ABCD	X ₁	X ₂	X ₃	X ₄	X ₅	X ₆	X ₇
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	0	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1

$$X_1 = (A + B + C + D') (B' + D) = (A + B + C + D') (B' + C' + D) (B' + C + D)$$

$$X_2 = (B' + C + D') (B' + C' + D)$$

$$X_3 = (B + C' + D)$$

$$X_4 = (B + C + D') (B' + C + D) (B' + C' + D')$$

$$X_5 = D' (B' + C) = D' (B' + C + D)$$


$$X_6 = (A + B + D') (B + C') (C' + D')$$

$$X_7 = (A + B + C) (B' + C' + D')$$


This solution uses 18 gates and 48 gate inputs.

Students are allowed to use a maximum of 19 gates.


8.O, continued

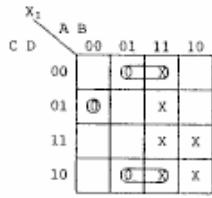

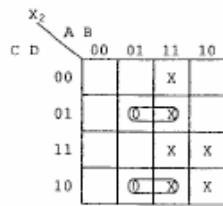
$$X_1 = (A + B + C + D)(B' + C + D)(B' + C' + D)$$




$$X_2 = (B' + C + D')(B' + C' + D)$$

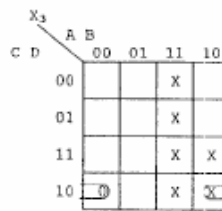


$$X_3 = (B + C' + D)$$

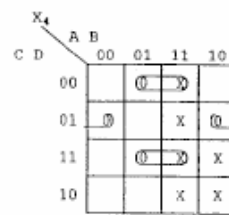

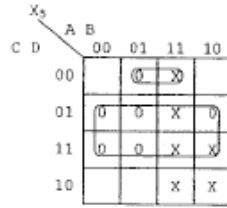
$$X_4 = (B' + C' + D')(B' + C + D)(B + C + D)$$



$$X_5 = (D')(B' + C + D)$$

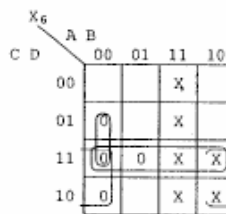


$$X_6 = (C' + D')(B + C)(A + B + D')$$

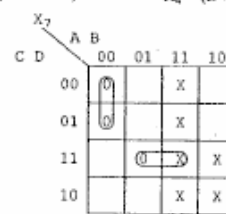


$$X_7 = (B' + C' + D')(A + B + C)$$

To save one gate, use:

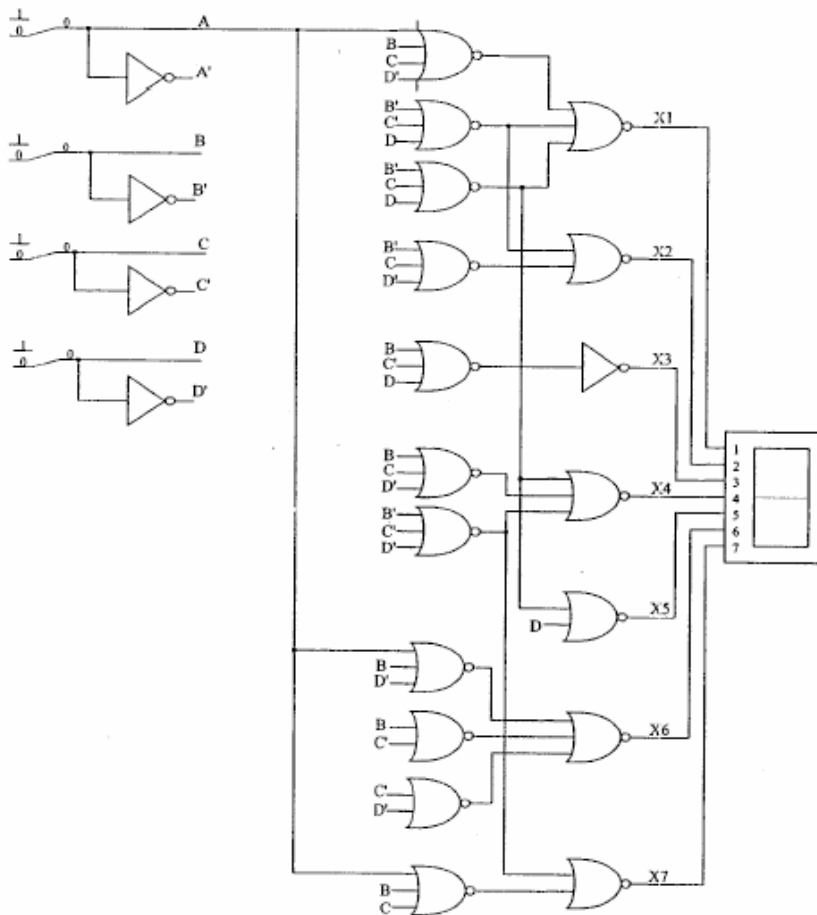
$$X_6 = (B' + C' + D')(B + C')(A + B + D')$$




9.1 (a)

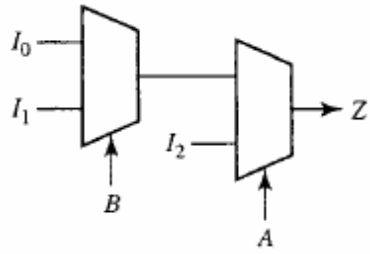


(b)

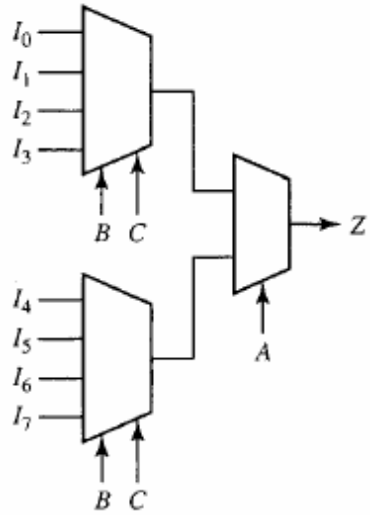


(c)

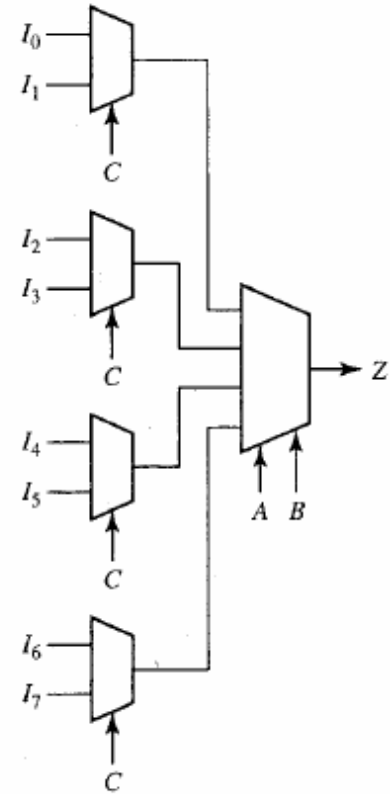


9.2

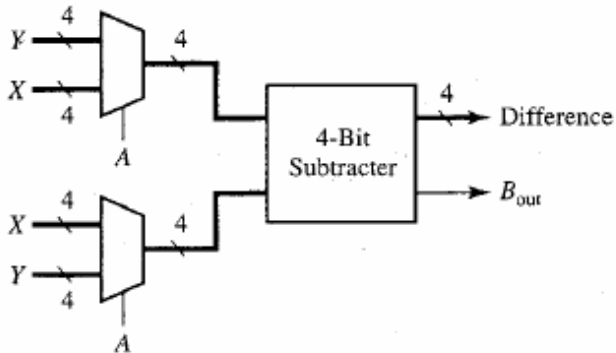


9.4 (a)

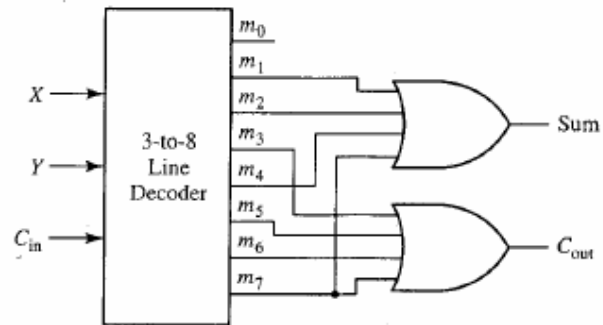

(b)

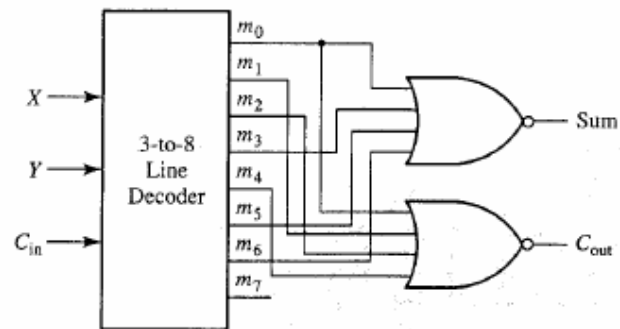


9.8 (a)

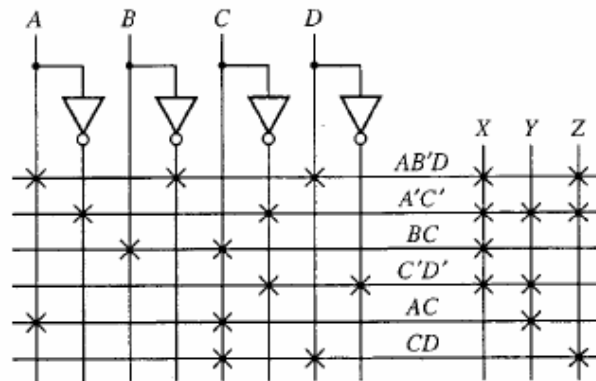

(b) Truth Table for the ROM

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	1	1	1
0	1	0	1	1	1	1
0	1	1	0	1	0	0
0	1	1	1	1	0	1
1	0	0	0	1	1	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	0	0	0
1	1	1	0	1	1	0
1	1	1	1	1	1	1

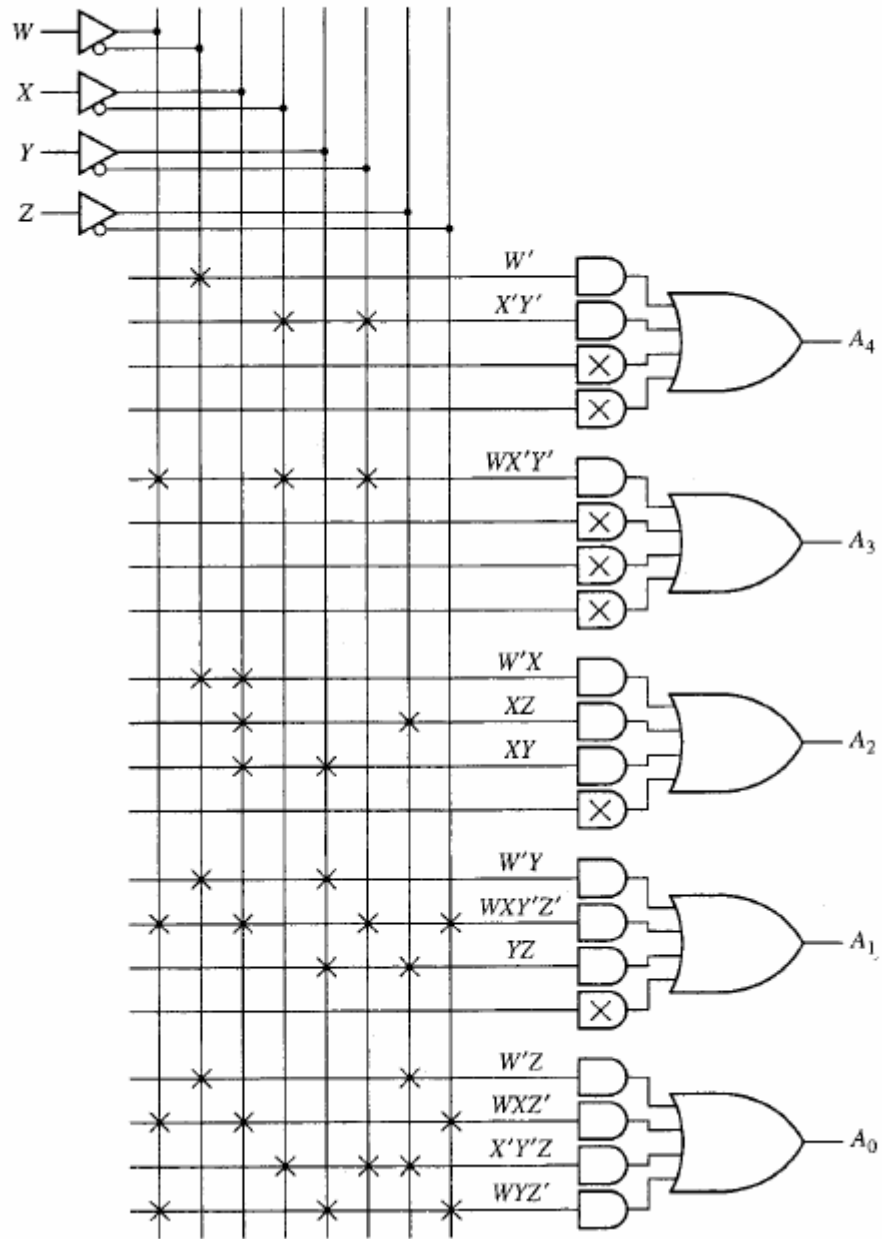9.10 (a) $A_4 = W' + X'Y'$ $A_3 = WX'Y'$ $A_2 = W'X + XZ + XY$
 $A_1 = W'Y + WXY'Z' + YZ$ $A_0 = W'Z + WXZ' + X'Y'Z + WYZ'$



(b)

W	X	Y	Z	A ₄	A ₃	A ₂	A ₁	A ₀
0	-	-	-	1	0	0	0	0
-	0	0	-	1	0	0	0	0
1	0	0	-	0	1	0	0	0
0	1	-	-	0	0	1	0	0
-	1	-	1	0	0	1	0	0
-	1	1	-	0	0	1	0	0
0	-	1	-	0	0	0	1	0
1	1	0	0	0	0	0	1	0
-	-	1	1	0	0	0	1	0
0	-	-	1	0	0	0	0	1
1	1	-	0	0	0	0	0	1
-	0	0	1	0	0	0	0	1
1	-	1	0	0	0	0	0	1

9.25 (a)


C D		A B			
		00	01	11	10
00	⊙	1	1	1	
01	1	1	⊙	⊙	
11	⊙	0	0	⊙	
10	1	1	1	1	

$$F_1 = (A + B + C + D)(A' + C + D')(C' + D')$$

9.25 (a)
(contd)

C D		A B			
		00	01	11	10
00	⊙	1	1	1	
01	⊙	0	⊙	⊙	
11	⊙	0	1	1	
10	1	1	1	1	
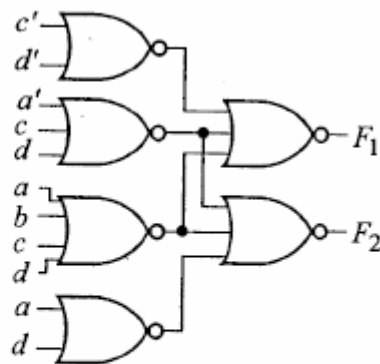
$$F_2 = (A + B + C + D)(A' + C + D')(A + D')$$



Alternate solution:

$$F_1 = (a + b + c + d)(a + c' + d')(a' + d')$$

$$F_2 = (a + b + c + d)(a + b' + d')(c + d')$$

9.25 (b)

	a	b	c	d	F_1	F_2
(cd')	-	-	1	0	1	1
(bd')	-	1	-	0	1	1
(ad')	1	-	-	0	1	1
(ac)	1	-	1	-	0	1
$(a'c'd)$	0	-	0	1	1	0

