


Solutions for Homework # 7

13.2 Notice that this is a shift register. At each falling clock edge, Q_3 takes on the value Q_2 had right before the clock edge, Q_2 takes on the value Q_1 had right before the clock edge, and Q_1 takes on the value X had right before the clock edge. For example, if the initial state is 000 and the input sequence is $X = 1100$, the state sequence is = 100, 110, 011, 001, and the output sequence is $Z = (0)0011$. Z is always Q_3 , which does not depend on the present value of X . So it's a Moore machine. See FLD p. 653 for the state graph.

13.3 (a) $A^+ = AK'_A + A'J_A = A(B' + X) + A'(BX' + B'X)$
 $B^+ = B'J_B + BK'_B = AB'X + B(A' + X')$
 $Z = AB$

		X			
		0	1	0	1
A B	00	0	1	0	0
	01	1	0	1	1
	11	0	1	1	0
	10	1	1	0	1

Present State AB	Next State (A ⁺ B ⁺)		Z
	X=0	X=1	
00	00	10	0
01	11	01	0
11	01	10	1
10	10	11	0

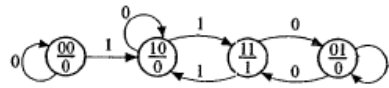

13.3 (b) $X = 0 1 1 0 0$
 $AB = 00 00 10 11 01 11$
 $Z = (0) 0 0 1 0 1$

13.3 (c) See FLD p. 653 for solution.

13.7 (a) Notice that Z depends on the input X, so this is a Mealy machine.

$Q_1^+ = J_1Q_1' + K_1'Q_1 = XQ_1'Q_2 + X'Q_1$
 $Q_2^+ = J_2Q_2' + K_2'Q_2 = XQ_1'Q_2' + X'Q_2$
 $Z = Q_2 \oplus X = XQ_2' + X'Q_2$


State	Present State	Next State (Q_1^+, Q_2^+)		Z	
	Q_1Q_2	X=0	X=1	X=0	X=1
S_0	00	00	01	0	1
S_1	01	01	10	1	0
S_2	11	11	00	1	0
S_3	10	10	00	0	1

		X			
		0	1	0	1
Q1 Q2	00	0	0	0	1
	01	0	1	1	0
	11	1	0	1	0
	10	1	0	0	1


Q1⁺ Q2⁺ Z

Alternate solution: Swap states S_2 and S_3 .

13.7 (a)
(contd)

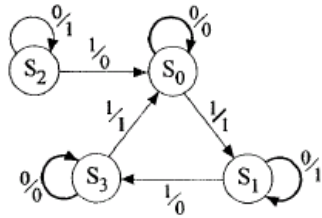

13.7 (b)

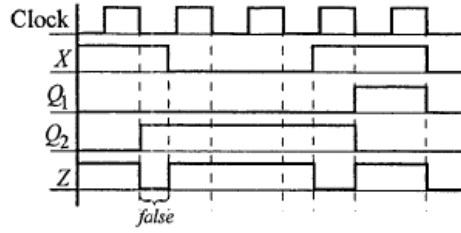

13.8 (a) Notice that Z does not depend on this input X, so this is a Moore machine.

$$Q_1^+ = X_1 X_2 Q_1 + Q_1 Q_2 + X_1 Q_2$$

$$Q_2^+ = Q_1'(X_1 + X_2) + Q_2(X_1' + X_2') = X_1 Q_1' + X_2 Q_1' + X_1' Q_2 + X_2' Q_2$$

$$Z = Q_1 Q_2'$$

Q1 Q2		X1 X2			
		00	01	11	10
00	0	0	0	0	0
01	0	0	1	1	1
11	1	1	1	1	1
10	0	0	1	0	0

Q_1^+


Q1 Q2		X1 X2			
		00	01	11	10
00	0	1	1	1	1
01	1	1	1	1	1
11	1	1	0	1	1
10	0	0	0	0	0

Q_2^+


Q2		Q1	
		0	1
0	0	1	
1	0	0	

Z

State	Present State Q_1, Q_2	Next State X_1, X_2				Z
		00	01	11	10	
S_0	00	00	01	01	01	0
S_1	01	01	01	11	11	0
S_2	11	11	11	10	11	0
S_3	10	00	00	10	00	1

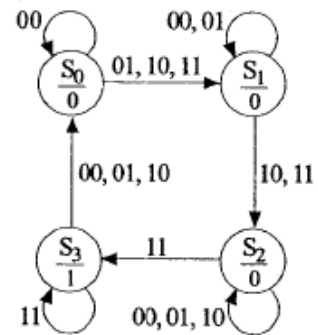


13.8 (b)

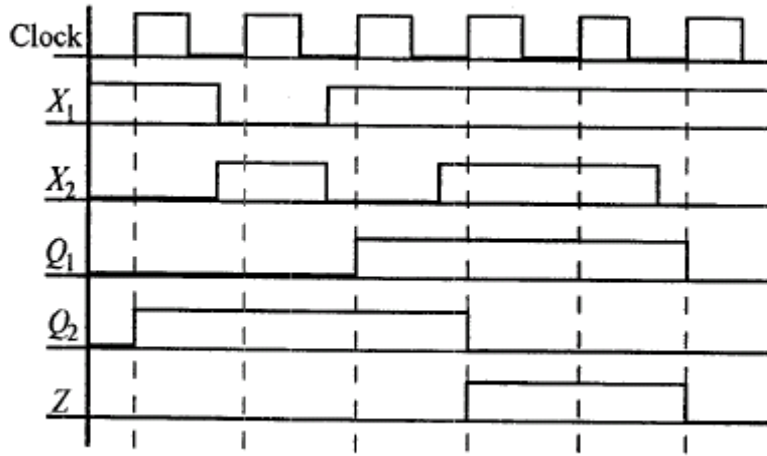


Correct output: $Z = 0, 0, 0, 1, 1, 0$

14.17 There are two identical parts: one with an output of 0 and one with an output of 1.

State	Meaning
S_1, S_4	Previous input was 0
S_2, S_5	Previous inputs were 01
S_3, S_0	Previous input was 1 / Reset (S_0)

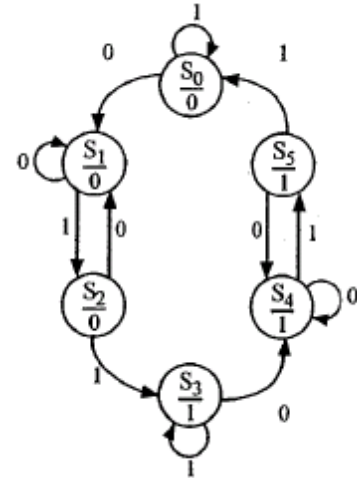

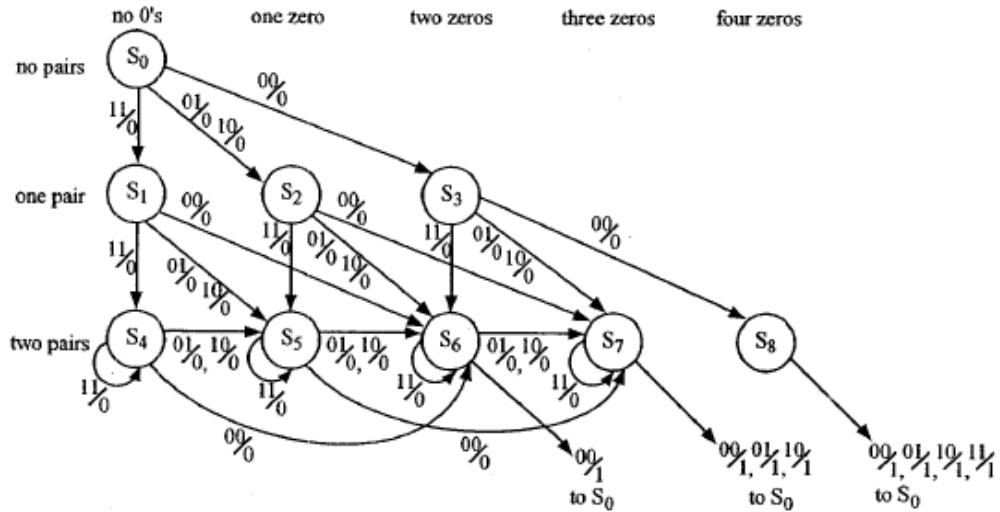14.19 This is another problem similar to 14.10. Plot the number of 0's horizontally and the number of pairs vertically:



Pairs	0's	Present State	Next State				Z_1, Z_2			
			00	01	10	11	00	01	10	11
0	0	S_0	S_3	S_2	S_2	S_1	0	0	0	0
1	0	S_1	S_6	S_5	S_5	S_4	0	0	0	0
1	1	S_2	S_7	S_6	S_6	S_5	0	0	0	0
1	2	S_3	S_8	S_7	S_7	S_6	0	0	0	0
2	0	S_4	S_6	S_5	S_5	S_4	0	0	0	0
2	1	S_5	S_7	S_6	S_6	S_5	0	0	0	0
2	2	S_6	S_0	S_7	S_7	S_6	1	0	0	0
2	3	S_7	S_0	S_0	S_0	S_7	1	1	1	0
2	4	S_8	S_0	S_0	S_0	S_0	1	1	1	1

Note: There is a seven-state solution.

14.23 Example: $X = 001100110101$

$Z = 001110111101$

Note: Overlapping sequences are allowed.

State	Meaning
S_0	No sequence
S_1	0
S_2	00
S_3	001
S_4	0011

State	Next State		Z	
	X=0	X=1	X=0	X=1
S_0	S_1	S_0	0	1
S_1	S_2	S_0	0	1
S_2	S_2	S_3	0	1
S_3	S_1	S_4	0	1
S_4	S_1	S_0	1	1

