

if-then else : 2-1 mux

```
mux: process (A, B, Select)
begin
  if (select='1') then
    Z <= A;
  else
    Z <= B;
  end if;
end process;
```

Conditional signal assignment

2-1 Mux

```
Z <= A when (Select='1')  
    else B;
```

Concurrent statement - I.e. outside process.

Case statement: 2-1 Mux

```
mux: process
```

```
begin
```

```
  case Select is
```

```
    when '0' => Z <= B;
```

```
    when '1' => Z <= A;
```

```
    when others => Z <= '-'; -- cover all cases
```

```
  end case;
```

```
end process;
```

Priority Encoder using if-then- elsif

```
Z <= E;    -- default
if (SELECT_D = '1') then      Z <= D;
elsif (SELECT_C = '1') then   Z <= C;
elsif (SELECT_B = '1') then   Z <= B;
elsif (SELECT_A = '1') then   Z <= A;
end if;
```

Decoder using case statement

```
case_value := A & B & C; -- concatenate bits
CASE case_value IS
    WHEN "000" => Z <= "00000001";
    WHEN "001" => Z <= "00000010";
    ...
    WHEN others => Z <= "00000000";
END CASE;
```

Case statements

- Truth table can be directly translated into CASE statement. (I.e. hex to 7-segment)
- State transition table can also be implemented using CASE statement.
- Synthesized as combinational logic (unless incompletely specified.)

Case vs. If-then-elsif

- Case statement generates hardware with more parallelism.
- If-then-elsif has built-in priority; Can require lots of logic for low-priority conditions.
- If conditions are mutually exclusive, use case statement to simplify logic.

Inferred Latch (undesirable!)

```
process (A, Select)
begin
  if (Select='1') then
    Z <= A;
  end if;
end process;
```


Preventing Latch Inference

- If-statements and case statements must be completely specified or VHDL compiler infers latches.
- A default assignment must be made so that an assignment occurs for all conditions.
- #1 synthesis problem for Xilinx - although simulation will work, the final hardware most likely will NOT work!

D-FF Simulation Model

```
process (CLK) begin
```

```
  if CLK='1' then
```

```
    Q <= D;
```

```
  end if;
```

```
end process;
```

- Incomplete sensitivity list
- What will be synthesized??

D flip-flop

```
DFF : process
```

```
begin
```

```
    wait until clk'event and clk='1';
```

```
    Q <= D;
```

```
end process;
```

D flip-flop with Asynch Reset

```
process (clk, reset, D)
begin
  if (reset='1') then
    Q <= '0';
  elsif (clk'event and clk='1') then
    Q <= D;
  end if;
end process;
```

D-FF with async reset and enable

```
process (clk, reset, D, enable) begin
  if (reset='1') then
    Q <= '0';
  elseif (clk'event and clk='1') then
    if (enable='1') then
      Q <= D;
    end if;
  end if;
end process;
```

D-FF with Synch Reset

```
process begin
    wait until clk'event and clk='1';
    if (reset='1') then
        Q <= '0';
    else
        Q <= D;
    end if;
end process;
```

Synthesis Guidelines

- Avoid inferring latches.
- Don't specify time delays.
- Avoid incomplete sensitivity lists.
- Don't specify initial values in entity, signal or variable declarations.
- Use basic constructs and behavioral code.
- Use `std_logic` and `std_logic_vector` types.

Synthesis Guidelines (cont.)

- A process must have a sensitivity list or one or more wait statements.
- All paths through process code must be balanced. I.e. if one path has a wait statement, all paths must have a wait statement.

IEEE-1164 Standard Logic

- ('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-')
- accurately models hardware.
- std_logic replaces type bit
- std_logic_vector replace bit_vector
- Recommended for simulation and synthesis
- Special operator overloading functions and resolution functions.

Using IEEE-1164

Library IEEE;

use IEEE.std_logic_1164.all;

use IEEE.std_logic_unsigned.all;

- Library source code available on our system.
- Can add std_logic vectors, model tri-state buffers, etc.

How will this code be synthesized?

```
process
begin
    wait until clk'event and clk='1';
    synch_in <= asynch_in;
    stage_out <= synch_in;
end process;
```

Variables

- Local to a process.
- Instantaneously updated - no delta delay.
- Useful for algorithmic description which needs to generate/use intermediate values.
(I.e. inside for loop)
- Contrast: signals are global to process only
- Signals are *scheduled*, not updated instantly.

Parity generator using variable

```
process (WORD)          -- bit_vector(0 to 4)
variable ODD : bit;
begin
    ODD := '0';
    for I in 0 to 4 loop
        ODD := ODD xor WORD(I);
    end loop;
    PARITY <= ODD;
end process;
```

Summary

- Know how to use *basic constructs* to produce predictable, reliable synthesis results.
- Know how to avoid inferring latches!
- Signals are *scheduled*; Variables update instantly.
- Model state machines using *separate processes* for state registers and for next-state combinational logic.