Ex: Build a multi-level NOR

Key: ends in AND

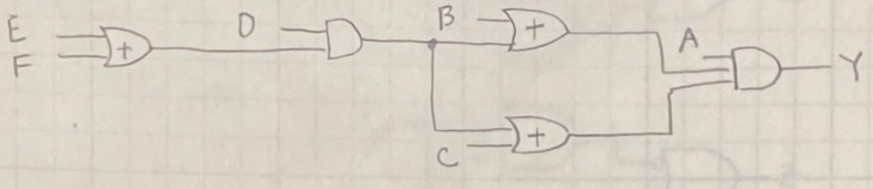

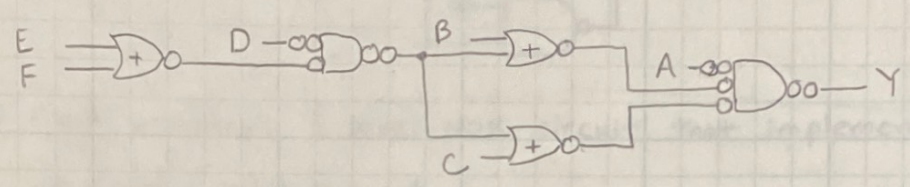

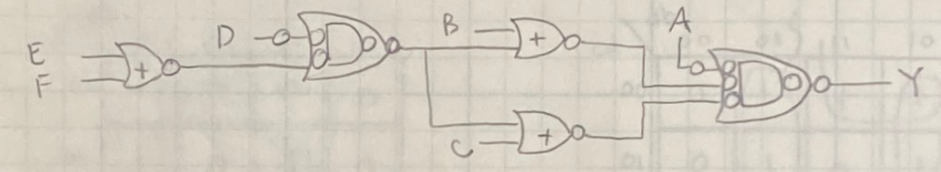

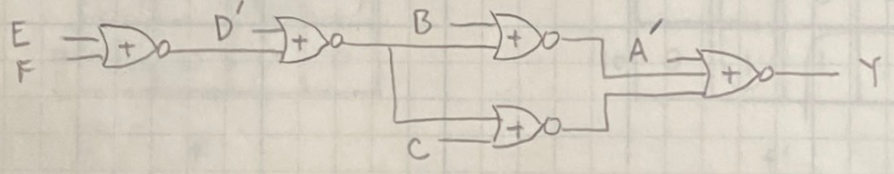

Note entering signals: not inverted; inverted; not inverted; inverted